


Unit - 2

Laplace transform:-

↳ to convert time domain eqⁿ to frequency domain

$$x(t) \xrightarrow{\text{L.T.}} X(s)$$

$$s = \sigma + j\omega$$

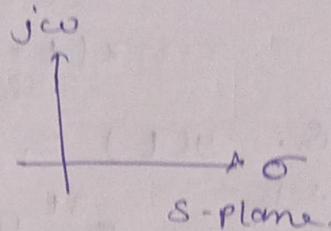

$$X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$

where,

$\sigma \rightarrow$ damping factor
 $\omega \rightarrow$ frequency

Advantages:-

- a) Any differential or integral eqⁿ in time domain is transformed into a linear eqⁿ if solved in s-domain and hence calculation becomes easier.


Q. Find Laplace transform of

$$x(t) = e^{at} u(t)$$

Sol:-

$$X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$
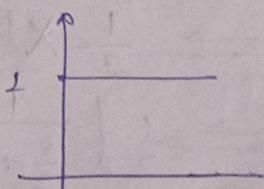
$$= \int_{-\infty}^{\infty} e^{at} \cdot u(t) \cdot e^{-st} dt$$



$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$

∴

$$X(s) = \int_0^{\infty} e^{-(s+a)t} dt$$

$$= \frac{[e^{-(s+a)t}]_0^{\infty}}{-(s+a)} = \frac{-1}{(s+a)} \left[\frac{1}{e^{\infty}} - \frac{1}{e^0} \right]$$

$$X(s) = \frac{1}{s+a}$$

Properties of Laplace transform:-

1) Time shifting

$$x(t-t_0) \xrightarrow{\text{L.T.}} X(s) e^{-st_0}$$

$$x(t+t_0) \xrightarrow{\text{L.T.}} X(s) e^{st_0}$$

Q. $y(t) = e^{-3t} u(t-4)$

Sol:-

$$e^{-3t} u(t) = \frac{1}{s+3}$$

$$e^{-2t} u(t-4) \not\cong \left(\frac{1}{s+3}\right) e^{-4s}$$

$$e^{-3(t-4)} u(t-4) \cong \left(\frac{1}{s+3}\right) (e^{-4s})$$

$$e^{-3t} \cdot u(t-4) \cong \frac{e^{-4s} \cdot e^{-12}}{s+3}$$

$$y(t) \cong \frac{e^{-4(s+3)}}{s+3}$$

② Time scaling

$$x(at), a \neq 0 \xrightarrow{} \frac{1}{|a|} X\left(\frac{s}{a}\right)$$

Q. $\text{If } x(t) = e^{-3t} u(t) \text{ find L.T of } x(2t)$

Sol:- $x(t) = e^{-3t} u(t) \cong \frac{1}{s+3}$

$$x(2t) = e^{-3(2t)} u(2t) \cong \frac{1}{2} X\left(\frac{s}{2}\right)$$

$$\cong \frac{1}{2} \left(\frac{1}{\frac{s}{2} + 3} \right)$$

$$\cong \frac{1}{2} \left(\frac{2}{s+6} \right)$$

$$e^{-6t} u(2t) \cong \frac{1}{s+6}$$

$u(2t) = u(t)$ as it always have value 1.

$$e^{-6t} u(t) \cong \frac{1}{s+6}$$

3) Frequency shifting :-

$$e^{-at} \cdot x(t) \Leftrightarrow X(s+a)$$

Q. If $x(t) = e^{-2t} u(t)$ find L.T of $e^{-4t} x(t)$

Sol:- $e^{-2t} u(t) \Leftrightarrow \frac{1}{s+2} = X(s)$

$$e^{-4t} \cdot x(t) \Leftrightarrow \frac{1}{(s+4)+2} = \frac{1}{s+6}$$

4) Differentiation in frequency.

$$t^n x(t) \Leftrightarrow (-1)^n \frac{d^n X(s)}{ds^n}$$

Q. $y(t) = t e^{-at} u(t)$ find its L.T.

Sol:- $t \cdot x(t) = t e^{-at} \cdot u(t) \Leftrightarrow X(s) = \frac{1}{s+a}$

$$\begin{aligned} t \cdot e^{-at} \cdot u(t) &\Leftrightarrow (-1)' \frac{d}{ds} \left(\frac{1}{s+a} \right) \\ &\Leftrightarrow - \left[-\frac{1}{(s+a)^2} \right] \\ &\Leftrightarrow \frac{1}{(s+a)^2} \end{aligned}$$

5) Integration in frequency.

$$\frac{x(t)}{t} \Leftrightarrow \int_s^{\infty} X(s) ds$$

Q. $f(t) = \frac{(1-e^t)}{t} \cdot u(t)$ find its L.T.

Sol:- let $x(t) = (1-e^t) u(t)$

$$X(s) = \frac{1}{s} - \frac{1}{s+1}$$

$$f(t) = \frac{x(t)}{t} \Leftrightarrow F(s) = \int_s^{\infty} X(s) ds$$

$$\begin{aligned}
 f(s) &= \int_s^{\infty} \left(\frac{1}{s} - \frac{1}{s-1} \right) ds \\
 &= \left[\log s - \log(s-1) \right]_s^{\infty} \\
 f(s) &= \left[\log \left(\frac{s}{s-1} \right) \right]_s^{\infty} \\
 &= \log \left[\lim_{s \rightarrow \infty} \left(\frac{s}{s-1} \right) \right] - \log \left(\frac{s}{s-1} \right) \\
 &= \log \left[\lim_{s \rightarrow \infty} \frac{1}{1 - \frac{1}{s}} \right] - \log \left(\frac{s}{s-1} \right) \\
 &= \log(1) - \log \left(\frac{s}{s-1} \right) \\
 &= -\log \left(\frac{s}{s-1} \right) \\
 &= \log \left(\frac{s-1}{s} \right)
 \end{aligned}$$

b) Differentiation in Time.

$$\frac{d^n x(t)}{dt^n} \rightleftharpoons s^n X(s) - s^{n-1} x(0^-) + s^{n-2} x'(0^-) - s^{n-3} x''(0^-) + \dots$$

Q. where, $x(0^-) = x(t) \Big|_{t=0^-}$

$$x'(0^-) = \frac{dx(t)}{dt} \Big|_{t=0^-}$$

$$x''(0^-) = \frac{d^2}{dt^2} x(t) \Big|_{t=0^-}$$

Q. $\frac{d^2 x(t)}{dt^2} + 4 \frac{dx(t)}{dt} - 3 x(t) = 0$

where $x(0^-) = -3, x'(0^-) = 0$

find its LT.

Sol:

$$\begin{aligned}
 \underline{L\{T\}} &= s^2 X(s) - s x(0^-) - s^0 x'(0^-) + 4 \{ s X(s) - s^0 x(0^-) \} \\
 (s^2 X(s) + 3s - 0) + 4 s X(s) + 12 - 3 X(s) &= 0
 \end{aligned}$$

$$x(s) [s^2 + 4s - 3] = -(3s + 12)$$

$$x(s) = \frac{-(3s + 12)}{s^2 + 4s - 3}$$

Some important Laplace transform pairs? -

<u>x(t)</u>	<u>X(s)</u>
① $s(t)$	$\rightarrow \frac{1}{s}$
② $u(t)$ or $u(-t)$	$\rightarrow \frac{1}{s}$ or $\frac{1}{s}$
③ $e^{-at} u(t)$	$\rightarrow \frac{1}{s+a}$
4) $\sin \omega_0 t \cdot u(t)$	$\rightarrow \frac{\omega_0}{s^2 + \omega_0^2}$
5) $\cos \omega_0 t \cdot u(t)$	$\rightarrow \frac{s}{s^2 + \omega_0^2}$
6) $t^n u(t)$	$\rightarrow \frac{n!}{s^{n+1}}$
7) $x(t) = t u(t)$	$\rightarrow \frac{1}{s^2}$
8) $\sinh \omega_0 t \cdot u(t)$	$\rightarrow \frac{\omega_0}{s^2 - \omega_0^2}$
9) $\cosh \omega_0 t \cdot u(t)$	$\rightarrow \frac{s}{s^2 - \omega_0^2}$

Inverse Laplace transform? -

$$x(t) \xrightarrow{L.T} X(s)$$

$$X(s) \xrightarrow{I.L.T} x(t)$$

$$x(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$

$$x(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} x(s) e^{st} ds$$

Q. find I.L.T. for $X(s) = \frac{3}{(s+1)(s+2)^2}$

$$\text{Sol: } \frac{s+3}{(s+1)(s+2)^2} = \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

$$\text{If } s+1=0 \Rightarrow s=-1 \Rightarrow A = \frac{-1+3}{(-1+2)^2} = 2$$

$$\text{If } (s+2)^2=0 \Rightarrow s=-2 \Rightarrow C = \frac{-2+3}{-2+1} = -1$$

Let $s=0$

$$\frac{3}{(1)(2)^2} = \frac{A}{1} + \frac{B}{2} + \frac{C}{(2)^2}$$

$$\frac{3}{4} = \frac{2}{1} + \frac{B}{2} + \frac{1}{4} \Rightarrow B = \left(\frac{3}{4} + \frac{1}{4} - 2\right) 2 \\ = \frac{(6+1-8) \times 2}{4} = -\frac{1}{2}$$

$$= -2$$

$$X(s) = \frac{s+3}{(s+1)(s+2)^2} = \frac{2}{s+1} + \frac{2}{(s+2)} + \frac{(-1)}{(s+2)^2}$$

Q. $x(t) = 2[e^{-t}u(t)] - 2[e^{-2t}u(t)] - t^2 e^{-2t} u(t)$

Q. Consider following d.e. of a signal

$$x(t) \Rightarrow \frac{d^2x(t)}{dt^2} - 3 \frac{dx(t)}{dt} + 2x(t) = 0$$

with $x(0^-) = -1$ and $x'(0^-) = 0$ find $x(t)$.

Sol:-

$$\text{L.T. } \Rightarrow s^2 X(s) - s x(0^-) - s^0 x'(0^-) - 3 \{ s X(s) - s^0 x(0^-) \\ + 2 X(s) \} = 0$$

$$s^2 X(s) - s(-1) - 0 - 3 \{ s X(s) + 1 \} + 2 X(s) = 0$$

$$s^2 X(s) + s - 3s X(s) + 3 + 2 X(s) = 0$$

$$X(s) \{ s^2 - 3s + 2 \} = - (s+3)$$

$$x(s) = \frac{-(s-3)}{s^2 - 3s + 2} = \frac{-s+3}{(s-1)(s-2)}$$

$$\frac{-s+3}{(s-1)(s-2)} = \frac{A}{(s-1)} + \frac{B}{(s-2)}$$


Let $s=1$, then $A = \frac{-1+3}{1-2} = -2$

$s=2$ then $B = \frac{-2+3}{2-1} = 1$

$$x(s) = \frac{-2}{s-1} + \frac{1}{s-2}$$

I. L.T. $x(t) = -2(e^t \cdot u(t)) + e^{2t} u(t)$

⑦ convolution property :-

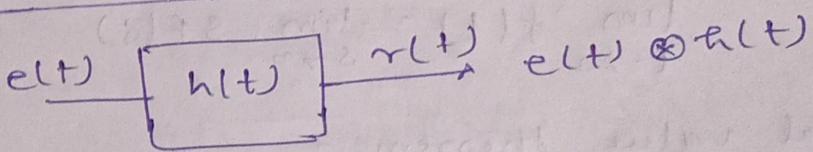

$$f_1(t) \rightarrow F_1(s)$$

$$f_2(t) \rightarrow F_2(s)$$

$$f_1(t) \otimes f_2(t) \rightarrow F_1(s) \cdot F_2(s)$$

Short cut for Region of convergence :-

Step-1:- compare σ with the real part of co-efficients of t in power of e

Step-2:- check if the signal is left sided or right sided and decide $<$ or $>$.

Ex: $e^{at} u(t)$ is left sided

since,

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

Illustrations :-

$$\textcircled{1} \quad f(t) = e^{(5+3j)t} u(-t-5)$$

left sided.

R.O.C. :- $\sigma < 5$

$$\textcircled{2} \quad f(t) = e^{3t} u(t) + e^{-2t} u(-t), \text{ find its R.O.C.}$$


Sol:-

$$\text{ROC I} \rightarrow \sigma > 3$$

$$\text{ROC II} \rightarrow \sigma < -2$$

No common ROC

so, L.T. does not exist.

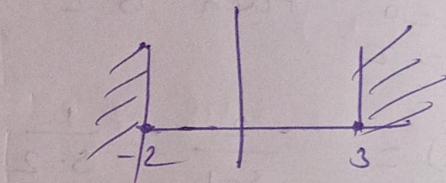

Initial value theorem :-


$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s F(s)$$

Final value theorem :-

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

Representation of circuit elements in s-domain :-


① Resistor

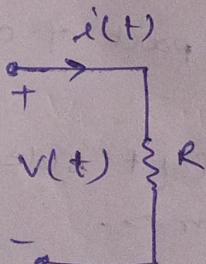

$$v(t) = i(t)R$$

$$V(s) = i(s)R$$

② Inductor :-


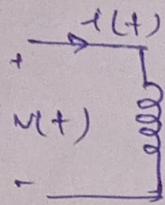


$$V(t) = L \frac{di(t)}{dt}$$


$$V(s) = L [sI(s) - s^0 i(0^-)] \\ = LS I(s) - L i(0^-)$$

$$I(s) = \frac{V(s)}{sL} + \frac{i(0^-)}{sX}$$
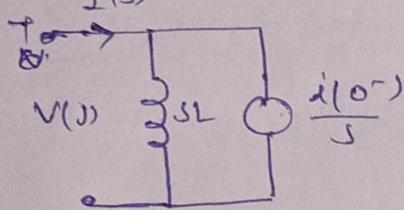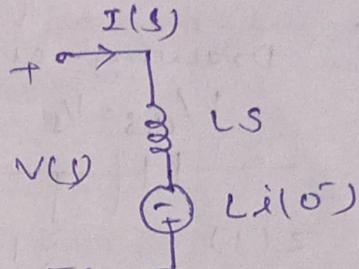
$$I(s) = \boxed{\frac{V(s)}{sL} + \frac{i(0^-)}{s}}$$




3) Capacitor :-

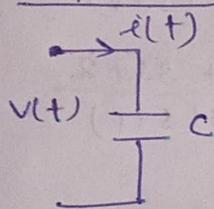


$$i(t) = C \frac{dV}{dt}$$

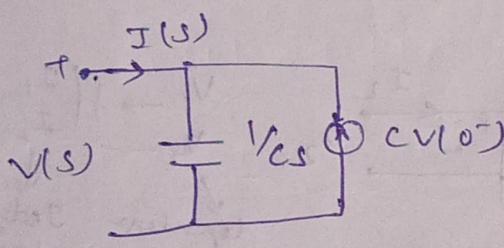
$$I(s) = C [sV(s) - s^0 V(0^-)] \\ = \frac{V(s)}{1/sC} - C V(0^-)$$



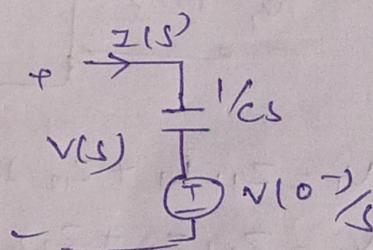
$$V(s) = \frac{I(s)}{Cs} + \frac{V(0^-)}{s}$$



Q. In the following circuit find $Z(s)$

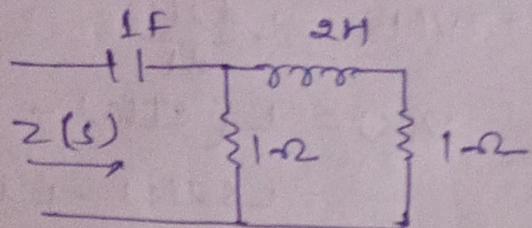

(sol:-) Drawing circuit in s-domain

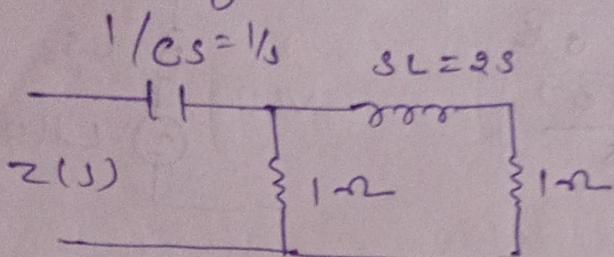


$$Z(s) = \frac{1}{s} + \left\{ 1 \parallel (2s+1) \right\}$$

$$= \frac{1}{s} + \frac{1 \times (2s+1)}{2s+1+1} = \frac{1}{s} + \frac{2s+1}{2(s+1)}$$

$$= \frac{2s+2+s(2s+1)}{2s(s+1)} = \frac{2s^2+3s+2}{2s(s+1)}$$

Two Port Network :-

1) Z-parameter

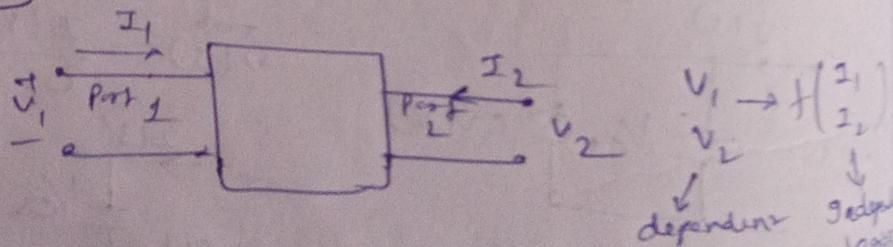

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \text{Open ckt. driving pt. input impedance}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad \text{Open ckt. reverse transfer impedance}$$

$$Z_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \quad \text{Open ckt. forward transfer impedance.}$$

$$Z_{22} = \frac{V_{22}}{I_2} \Big|_{I_1=0} \quad \text{open ckt. driving pt. output impedance.}$$

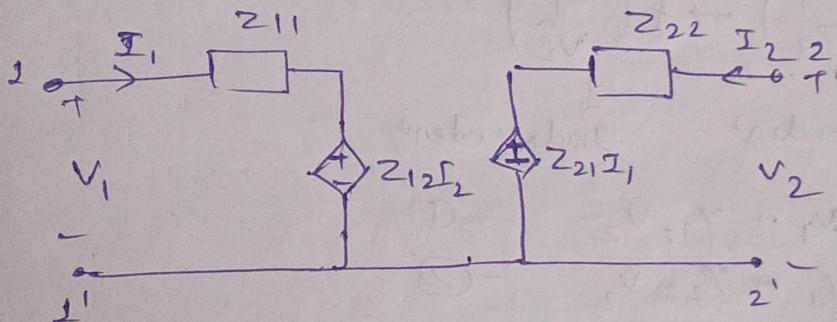Electrical equivalent circuit of Z-Parameter



Q. A two port is described by $V_1 = I_1 + 2V_2$
 $I_2 = -2I_1 + 0.4V_2$. find impedance parameters.

Sol:-

$$V_1 = I_1 + 2V_2 \quad \text{--- (1)}$$

$$I_2 = -2I_1 + 0.4V_2 \quad \text{--- (2)}$$

$$V_2 = \frac{2I_1}{0.4} + \frac{1}{0.4}I_2 \quad \text{--- (3)}$$

$$= 5I_1 + 2.5I_2 \quad \text{--- (4)}$$

put it in eqn (1)

$$V_1 = I_1 + 2(5I_1 + 2.5I_2)$$

$$= I_1 + 10I_1 + 5I_2$$

$$V_1 = 11I_1 + 5I_2 \quad \text{--- (5)}$$

Now,

$$V_1 = 11I_1 + 5I_2$$

$$V_2 = 5I_1 + 2 \cdot 5 I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 11 & 5 \\ 5 & 2 \cdot 5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[Z] = \begin{bmatrix} 11 & 5 \\ 5 & 2 \cdot 5 \end{bmatrix}$$

2.) γ -Parameter or Admittance Parameter

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \rightarrow f \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

↓ ↓
dependent independent

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- } \textcircled{1}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- } \textcircled{2}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[Y] = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$


$$Y_{11} = \frac{I_1}{V_1} \Big|_{\substack{V_2=0}} \quad \begin{array}{l} \text{short ckt driving point input} \\ \text{admittance} \end{array}$$

$$Y_{12} = \frac{I_2}{V_1} \Big|_{\substack{V_2=0}} \quad \begin{array}{l} \text{short ckt forward transfer} \\ \text{admittance} \end{array}$$

$$Y_{21} = \frac{I_1}{V_2} \Big|_{\substack{V_1=0}} \quad \begin{array}{l} \text{short ckt reverse transfer} \\ \text{admittance} \end{array}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \quad \text{short ckt. driving point admittance}$$

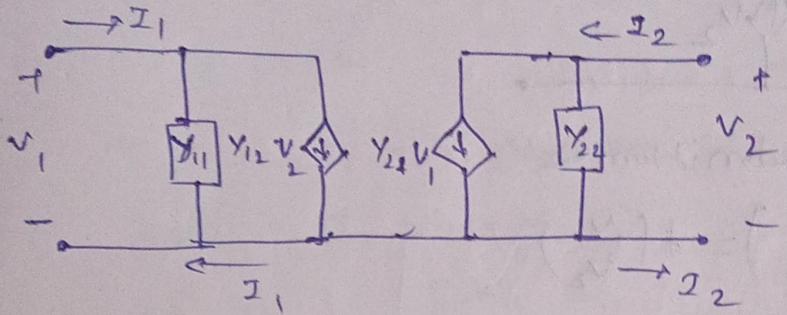Electrical equivalent circuit of Y-parameter.



Relation b/w Z and Y parameter :-

from Y-parameter.

$$[I] = [Y][V] \quad \text{--- (1)}$$

from Z-parameter

$$[V] = [Z][I] \quad \text{--- (2)}$$

$$[I] = [Z^{-1}][V] \quad \text{--- (3)}$$

from eqn (1) and (3)

$$[Y] = [Z^{-1}] \quad \text{or} \quad [Z] = [Y^{-1}]$$


$$[Z^{-1}] = \frac{\text{Adj } Z}{|Z|}$$

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$\text{adj } Z = \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$

$$Y_{11} = \frac{Z_{22}}{|Z|} + \frac{1}{Z_{11}} \quad Y_{12} = -\frac{Z_{12}}{|Z|}$$

$$Y_{21} = -\frac{Z_{21}}{|Z|} \quad Y_{22} = \frac{Z_{11}}{|Z|}$$

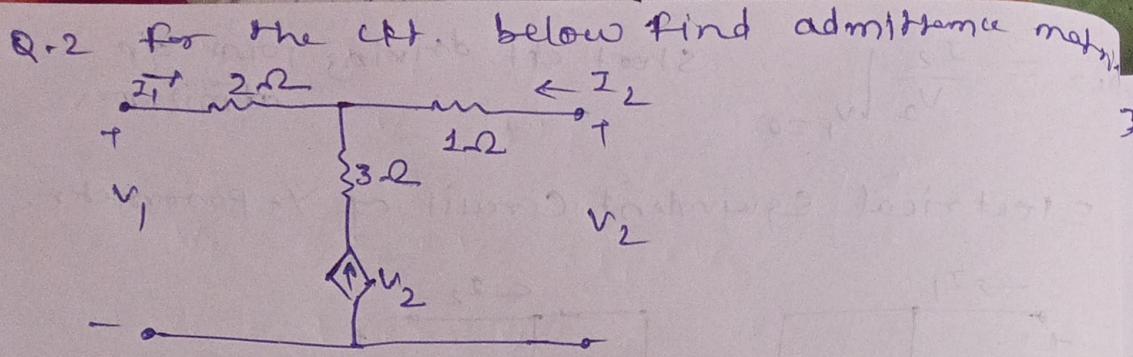

Sol:- For admittance,

$$\left(\frac{z_1}{z_2} \right) = f \left(\frac{v_1}{v_2} \right)$$

$$v_2 = -(I_1 + I_2) \quad \text{--- (1)}$$

Applying KVL in outer loop.

$$v_1 - 2z_1 + I_2 - v_2 = 0$$

$$v_1 = 2z_1 - I_2 + v_2$$

$$= 2z_1 - I_2 - I_1 - I_2$$

$$= I_1 - 2I_2 \quad \text{--- (2)}$$

$$v_1 = 2I_1 - 2I_2$$

$$v_2 = -I_1 - I_2$$

$$[z] = \begin{bmatrix} 1 & -2 \\ -1 & -1 \end{bmatrix}$$


$$\begin{aligned} |z| &= -1 - 2 \\ &= -3 \end{aligned}$$

$$[y] = [z^{-1}] = \frac{\text{adj } z}{|z|}$$

$$= -\frac{1}{3} \begin{bmatrix} -1 & 2 \\ 1 & 1 \end{bmatrix}$$

$$[y] = \begin{bmatrix} 1/3 & -2/3 \\ -1/3 & -1/3 \end{bmatrix}$$

3) h -parameter:

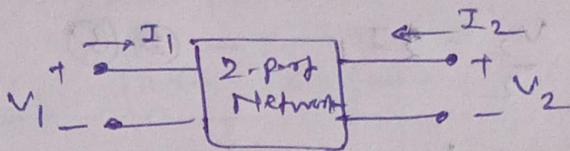

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = h \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$[H] = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \rightarrow h\text{-parameter matrix.}$$

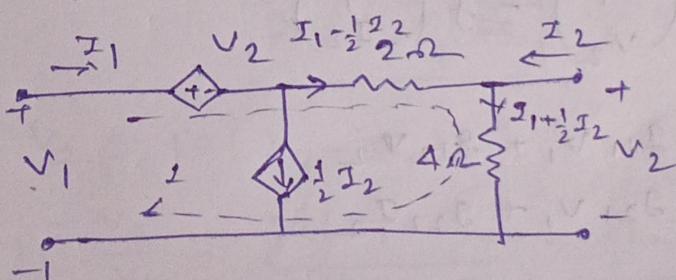Q. For the circuit show ^{find} the hybrid parameter matrix ($[h]$)



Sol:- Using supermesh concept, applying KVL

$$V_1 - V_2 - 2(I_1 - \frac{1}{2}I_2) - 4(I_1 + \frac{1}{2}I_2) = 0$$

$$-V_2 - 2I_1 - 4I_1 + I_2 - 2I_2 = 0$$

$$V_1 - V_2 - 6I_1 - I_2 = 0$$

$$V_1 = 6I_1 + I_2 + V_2 \quad \text{--- (1)}$$

$$V_2 = 4(I_1 + \frac{1}{2}I_2) \\ = 4I_1 + 2I_2 \quad \text{--- (2)}$$

Putting it in eq 1

$$V_1 = 6I_1 + I_2 + 4I_1 + 2I_2 \\ = 10I_1 + 3I_2$$

$$V_2 = 4I_1 + 2I_2$$

$$I_2 = \frac{V_2 - 4I_1}{2} \quad - \textcircled{3}$$


$$V_1 = 6I_1 + \frac{V_2 - 2I_1 + V_2}{2}$$

$$V_1 = 4I_1 + \frac{3}{2}V_2 \quad - \textcircled{4}$$

from eq $\textcircled{3}$ and $\textcircled{4}$

~~$$[h] = \begin{bmatrix} 4 & 3/2 \\ -2 & 1/2 \end{bmatrix}$$~~

4) g - Parameter (Inverse h - parameter)

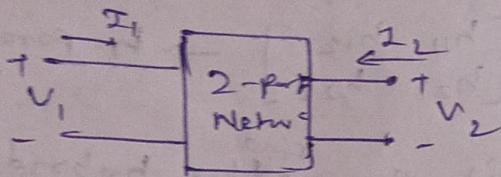

$$\begin{pmatrix} I_1 \\ V_2 \end{pmatrix} = f \begin{pmatrix} V_1 \\ I_2 \end{pmatrix}$$

$$I_1 = g_{11}V_1 + g_{12}V_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$


$$[g] = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$$

Relation b/w h - and g parameters :-

$$[H] = [g]^{-1} \text{ or } [g] = [H]^{-1}$$

Q. for the circuit given below find the inverse hybrid parameter g_{21} .

Sol.

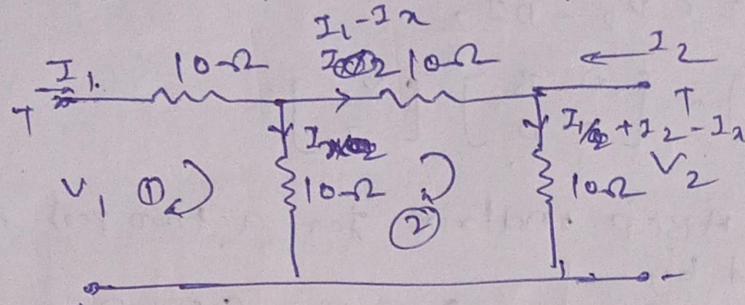

Sol:-

$$V_1 - 10I_1 - \frac{10I_2}{2} = 0$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

$$V_1 = 10(I_1 + I_2) \quad \text{---(1)}$$

$$10I_2 - 10(I_1 - I_2) - 10(I_1 + I_2 - I_1) = 0$$

$$10I_2 + 10I_2 + 10I_2 - 10I_1 - 10I_1 - 10I_2 = 0$$

But $I_2 = 0$


$$30I_2 - 20I_1 = 0$$

$$\boxed{I_1 = \frac{3}{2}I_2}$$

$$V_2 = 10(I_2 - I_1) \quad [\because I_2 = 0]$$

$$\begin{aligned} g_{21} &= \frac{V_2}{V_1} = \frac{10(I_2 - I_1)}{V_1} = \frac{\frac{3}{2}I_2 - I_1}{\frac{3}{2}I_2 + I_1} \\ &= \frac{I_2}{5I_2} = 0.2 \end{aligned}$$

5) ABCD Parameter :- or ~~poles~~

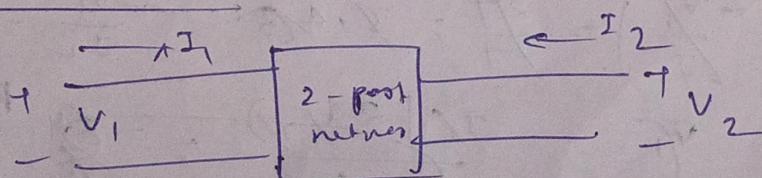

$$\begin{pmatrix} V_1 \\ Z_{21} \end{pmatrix} = f \begin{pmatrix} V_2 \\ Z_{22} \end{pmatrix}$$

$$V_1 = AV_2 - BI_2$$


$$I_1 = CV_2 - DJ_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Q. The ABCD matrix for a two port network is defined by

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

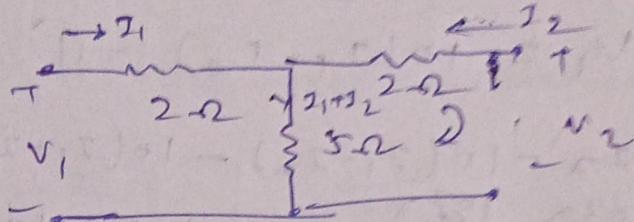then find the parameter B for given network



Sol:-

$$B = \frac{-V_1}{I_2} \Big|_{V_2=0}$$

$$V_1 - 2I_1 + 5I_2 = 0$$

$$V_1 = 7I_1 + 5I_2$$

$$\text{Eqn } 5(I_1 + I_2) + 2I_2 = 0 \quad (\because V_2 = 0)$$

$$7I_2 = -5I_1$$


$$I_2 = -\frac{5}{7}I_1 \quad I_1 = -\frac{7}{5}I_2$$

$$V_1 = \begin{cases} I_1 - 5 \times \frac{5}{7}I_1 \\ = I_1 \left(\frac{24}{7} \right) \end{cases} \quad V_1 = 7 \left(-\frac{7}{5}I_2 \right) + 5I_2 \\ = -\frac{24}{5}I_2$$

$$B = \frac{-V_1}{I_2} \Big|_{V_2=0} = \frac{24}{7} = 3.43 \quad -\frac{V_1}{I_2} = -\frac{24}{5}$$

$$V_1 = \frac{I_1 \left(\frac{24}{7} \right)}{5/7 I_1} = -\frac{24}{5} \quad B = 4.8$$

$$= -4.8.$$

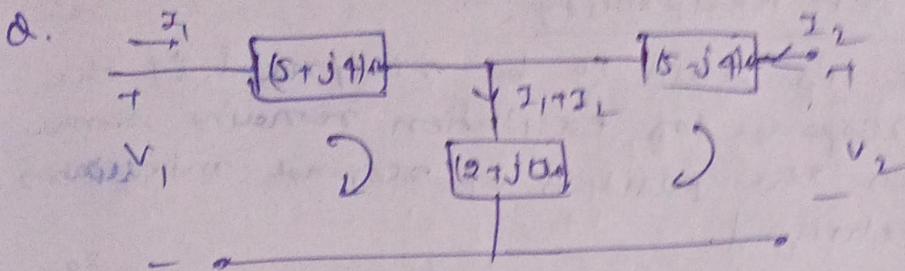

Find ABCD Parameters.

Sol:-

$$\begin{cases} v_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{cases}$$

$$v_1 - (5+j4)I_1 - (I_1 + I_2)(2+j0) = 0$$

$$v_1 - (7+j4)I_1 - 2I_2 = 0$$

$$v_1 = (7+j4)I_1 + 2I_2 \quad \text{--- (1)}$$

$$(I_1 + I_2)(2+j0) + (I_2)(5-j4) = v_2 = 0$$

$$2I_1 + 2I_2(7-j4) - v_2 = 0$$

$$I_1 = 6 \quad v_2 = I_2(3.5-j2)$$

$$I_1 = \frac{1}{2}v_2 - (3.5-j2)I_2 \quad \text{--- (2)}$$

put it in eq 1

$$v_1 = (7+j4)\left[\frac{1}{2}v_2 - (3.5-j2)I_2\right] + 2I_2$$

$$= (7+\frac{j}{2})v_2 - \{(7+j4)(3.5-j2) + 2\}I_2$$


$$v_1 = (3.5+j2)v_2 - [3.5 \cdot 5 I_2] \quad \text{--- (A)}$$

$$I_1 = 3.5v_2 - (3.5-j2)I_2 \quad \text{--- B}$$

$$[ABCD] = \begin{pmatrix} (3.5-j2) & -3.5 \\ 3.5 & (3.5+j2) \end{pmatrix}$$


Condition for Reciprocity:-

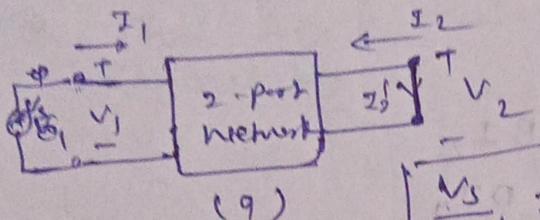A network is said to be reciprocal if the ratio of response to excitation remains same even when the position of response and excitation are interchanged.



(a)

$$\frac{V_3}{I_2'} = \frac{V_3}{I_1'}$$

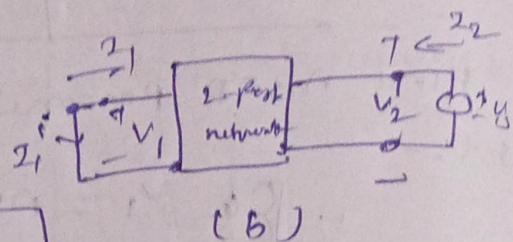

(b)

In case - (a)

2

$$V_1 = V_3 \quad I_1 = I_1' \quad I_2 = I_2' \quad V_2 = 0$$

In case - (b)

$$V_1 = 0 \quad I_1 = I_1' \quad V_2 = V_3 \quad I_2 = I_2'$$

Now

i) Z -parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (2)}$$

for case - (a)

$$\text{from eq } (1) \quad V_3 = Z_{11}I_1 + Z_{12}I_2' \quad \text{--- (A)}$$

from eq (2)

$$0 = Z_{21}I_1 + Z_{22}I_2' \quad \text{--- (B)}$$

$$I_1 = \frac{Z_{22}I_2'}{Z_{21}}$$

put it in eq (A)

$$V_3 = \frac{Z_{11}Z_{22}}{Z_{21}} I_2' + Z_{12}I_2'$$

$$\frac{V_3}{I_2'} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}Z_{12}}$$

For case - (b)

$$V_1 = 0 \quad I_{21} = -I_1' \quad V_2 = V_s \quad I_2 = I_2$$

Put these values in eq ①

$$0 = Z_{11}(-I_1') + Z_{12}I_2$$

$$I_2 = \frac{Z_{11}I_1'}{Z_{12}} \quad \rightarrow \quad \textcircled{B}$$

Put the values in eq ②

$$V_s = Z_{21}(-I_1') + Z_{22}I_2$$

$$= Z_{21}(-I_1') + Z_{22}\left(\frac{Z_{11}}{Z_{12}}\right)I_1'$$

$$\frac{V_s}{I_1'} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{12}}$$

Now we know for self-adjoint

$$\frac{V_1}{I_1'} = \frac{V_s}{I_1'}$$

$$\text{so, } \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{12}}$$

$$\boxed{Z_{21} = Z_{12}} \rightarrow Z\text{-parameter}$$


Similarly, $\boxed{Y_{21} = Y_{12}}$ $\rightarrow Y\text{-parameter}$

$$\boxed{AD - BC = 1} \rightarrow ABCD \text{ parameter}$$


$$\boxed{g_{12} = -g_{21}} \rightarrow g\text{-parameter}$$

Condition for symmetry 2 -

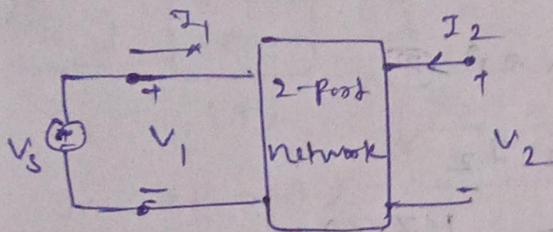A two port network is said to be symmetrical if the ports can be interchanged without changing the port voltage & current.



(a)

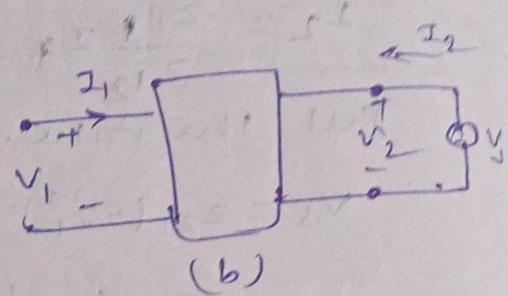

(b)

2.

$$V_1 = V_1 \quad I_1 \geq 0 \quad \frac{V_2}{I_2} = \frac{V_2}{I_2} \geq 0$$

$$\left. \frac{V_s}{I_1} \right|_{I_2=0} = \left. \frac{V_s}{I_2} \right|_{I_1=0}$$

Z-Parameter

for case (a)

$$V_1 = V_s \quad I_1 = I_1 \quad V_2 = V_2 \quad I_2 = 0$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (2)}$$

put case-(a) in eq (1) & (2)

$$V_s = Z_{11}I_1 \rightarrow \frac{V_s}{I_1} = Z_{11} \quad \text{--- (A)}$$

put case-b in eq (1) & (2)

$$\text{Q } V_1 = Z_{11}(0) + Z_{12}I_2$$

$$V_1 = Z_{12}I_2 \quad \text{--- (B)}$$

$$\text{Q } V_s = Z_{21}(0) + Z_{22}I_2$$

$$\frac{V_s}{I_2} = Z_{22} \quad \text{--- (B)}$$

Applying symmetry condn.

$$\boxed{I_{11} = I_{22}}$$

Y-Parameter :-

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (i)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (ii)}$$

put case (a) in eq (i) & (ii)

$$I_1 = Y_{11}V_s + Y_{12}V_2 \quad \text{& } 0 = Y_{21}V_1 + Y_{22}V_2$$

$$\frac{V_0}{V_s} = \frac{I_1}{V_s} \quad \text{--- (iii)} \quad I_1 = \frac{Y_{22}Y_{11} - Y_{12}Y_{21}}{Y_{22}}$$

put case b in eq (i) & (ii)

$$I_2 = Y_{21}V_1 + Y_{22}V_s$$

$$0 = Y_{11}V_1 + Y_{12}V_s$$

$$V_1 = -\frac{Y_{12}V_s}{Y_{11}}$$

$$I_2 = Y_{21}\left(-\frac{Y_{12}}{Y_{11}}\right)V_s + Y_{22}V_s$$

$$\frac{V_s}{I_2} = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{21}Y_{12}}$$

Equating both

$$\frac{Y_{22}}{Y_{22}Y_{11} - Y_{12}Y_{21}} = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{21}Y_{12}}$$

$$\boxed{Y_{11} = Y_{22}}$$

Parameter	"cond" of Reciprocity	"cond" of Symmetry
Z	$Z_{12} = Z_{21}$	$Z_{11} = Z_{22}$
Y	$Y_{12} = Y_{21}$	$Y_{11} = Y_{22}$
ABCD	$AD - BC = 1$	$A = D$
h	$h_{12} = -h_{21}$	$h_{11}h_{22} - h_{12}h_{21} = 1$

Relation b/w Z and ABCD parameters! —

Taking ABCD parameters eqn?

2.

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$V_2 = \frac{I_1}{C} + \frac{D}{C} I_2 \quad \text{--- (1)}$$

$$V_1 = A \left[\frac{I_1}{C} + \frac{D}{C} I_2 \right] - BI_2$$

$$V_1 = \frac{A}{C} I_1 + \frac{AD - BC}{C} I_2 \quad \text{--- (2)}$$

on comparing with Z-parameters:

$$Z_{11} = \frac{A}{C} \quad Z_{12} = \frac{AD - BC}{C}$$

$$Z_{21} = \frac{1}{C} \quad Z_{22} = \frac{D}{C}$$

Determine Z parameter from h-parameter

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$V_2 = \frac{I_2}{h_{22}} - \frac{h_{21}}{h_{22}} I_1$$

$$V_2 = -I_1 \left(\frac{h_{21}}{h_{22}} \right) + \frac{1}{h_{22}} (I_2) \quad \text{--- (3)}$$

$$V_1 = h_{11} I_1 + h_{12} \left(-\frac{h_{21}}{h_{22}} z_1 + \frac{1}{h_{22}} z_2 \right)$$

$$= h_{11} I_1 - \frac{h_{12} h_{21}}{h_{22}} z_1 + \frac{h_{12}}{h_{22}} I_2$$

$$V_1 = \left(\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right) + \frac{h_{12}}{h_{22}} I_2 \quad \text{--- (A)}$$


On comparing with z -parameters.

$$z_{11} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \quad z_{12} = \frac{h_{12}}{h_{22}}$$

$$z_{21} = -\frac{h_{21}}{h_{22}} \quad z_{22} = \frac{1}{h_{22}}$$

Interconnection of two ports:

(a) series connection

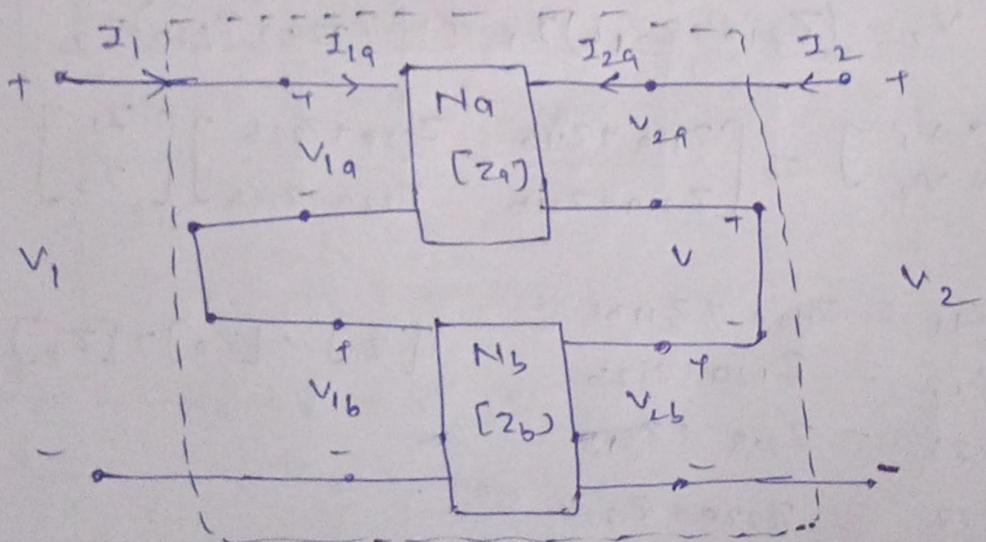

$$I_1 = I_{1a} = I_{1b} \quad \text{--- (i)}$$

$$V_1 = V_{1a} + V_{1b} \quad \text{--- (ii)}$$

$$I_2 = I_{2a} = I_{2b} \quad \text{--- (iii)}$$

$$V_2 = V_{2a} + V_{2b} \quad \text{--- (iv)}$$

for N_a,

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix}$$

for N_b,

$$\begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

on eqn (ii),

$$V_1 = V_{1a} + V_{1b}$$

$$= (Z_{11a} I_{1a} + Z_{12a} I_{2a}) + (Z_{11b} I_{1b} + Z_{12b} I_{2b})$$

$$V_1 = (Z_{11a} + Z_{11b}) I_1 + (Z_{12a} + Z_{12b}) I_2$$

similarly

$$V_2 = (Z_{21a} + Z_{21b}) I_1 + (Z_{22a} + Z_{22b}) I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = Z_{11a} + Z_{11b}$$


$$[z] = [z_a] + [z_b]$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

② Parallel connection :-

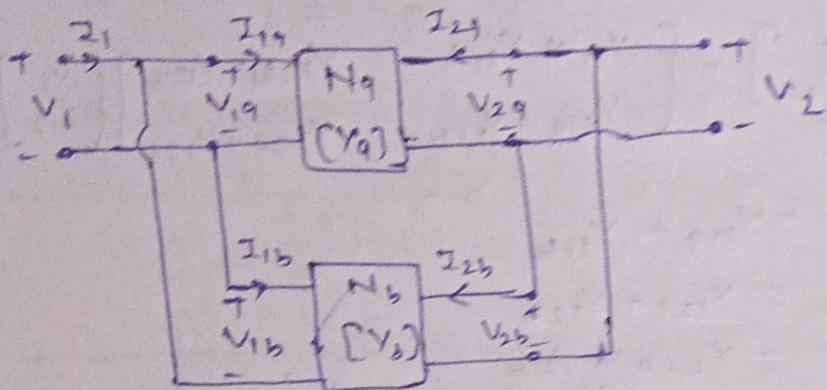

$$V_1 = V_{1a} = V_{1b} \quad \text{---(i)}$$

$$V_2 = V_{2a} = V_{2b} \quad \text{---(ii)}$$

$$I_1 = I_{1a} + I_{1b} \quad \text{---(iii)}$$

$$I_2 = I_{2a} + I_{2b} \quad \text{---(iv)}$$

for N_a

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

for N_b

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

$$I_{1a} = Y_{11a} V_{1a} + Y_{12a} V_{2a}$$

$$I_{1b} = Y_{11b} V_{1b} + Y_{12b} V_{2b}$$

$$I_1 = I_{1a} + I_{1b}$$

$$= Y_{11a} V_{1a} + Y_{12a} V_{2a} + Y_{11b} V_{1b} + Y_{12b} V_{2b}$$

$$= (Y_{11a} + Y_{11b}) V_1 + (Y_{12a} + Y_{12b}) V_2 \quad \text{---(3)}$$

Similarly,

$$I_2 = (Y_{21a} + Y_{21b})V_1 + (Y_{22a} + Y_{22b})V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$


$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

2.)

$$[Y] = [Y_a] + [Y_b]$$

Cascade Connection :-

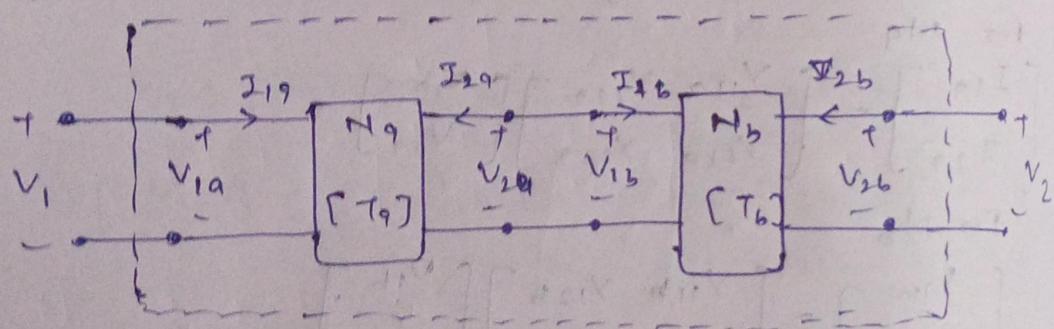

$$V_1 = V_{1a} \quad I_{1b} = -I_{2a} \quad I_2 = I_{2b}$$

$$I_1 = I_{1a} \quad V_{1b} = V_{2a} \quad V_2 = V_{2b}$$

for N_a

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$

V₁

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$[T] = [T_a][T_b]$$

Q. For the network shown below.

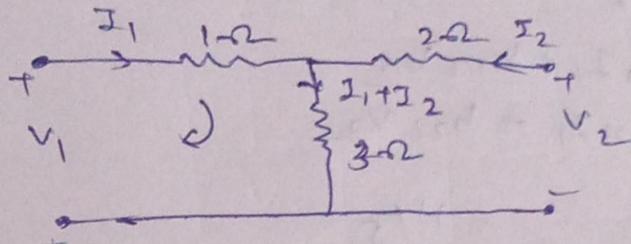

Find

- a) Z-parameter
- b) Y-parameter
- c) T-parameter
- d) h-parameter
- e) g-parameter.

Sol: - (a) Z-parameter.

$$V_1 = 4I_1 + 3I_2 \quad \text{--- (1)}$$

$$V_2 = 3I_1 + 5I_2.$$

$$[Z] = \begin{bmatrix} 4 & 3 \\ 3 & 5 \end{bmatrix}$$

$$(b) [Y] = [Z]^{-1} = \frac{1}{|Z|} \text{adj}(Z)$$

$$= \frac{1}{11} \begin{bmatrix} 5 & -3 \\ -3 & 4 \end{bmatrix}$$

$$= \begin{bmatrix} 5/11 & -3/11 \\ -3/11 & 4/11 \end{bmatrix}$$

(c) T-parameter

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 4/3$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = 11/3$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = 1/3$$

$$D = -\frac{I_1}{I_2} \Big|_{V_2=0} = 5/3$$

e) h-parameter

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = 11/5$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_2=0} = 3/5$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} = -3/5$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = 1/5$$

$$[h] = \begin{bmatrix} 11/5 & 3/5 \\ -3/5 & 1/5 \end{bmatrix}$$

$$\boxed{h_{11} = 11/5}$$

f) g-parameter

$$[g] = [h]^{-1} = \frac{1}{11/5} \left\{ \text{adj}(h) \right\}$$

$$= \frac{5}{11} \begin{bmatrix} 1/5 & -3/5 \\ 3/5 & 11/5 \end{bmatrix}$$

$$= \begin{bmatrix} 1/11 & -3/11 \\ 3/11 & 11/11 \end{bmatrix}$$