
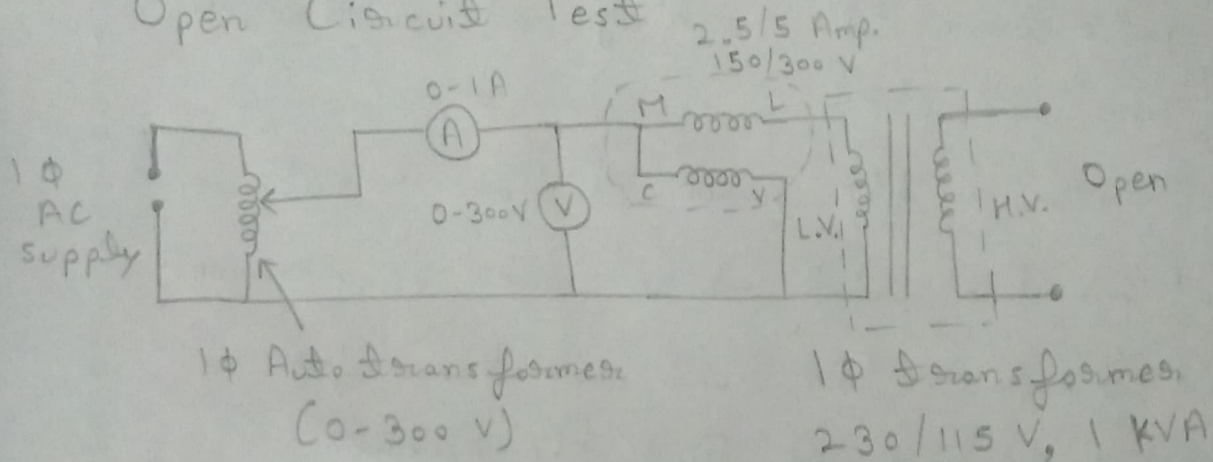


Circuit Diagram :-

Open Circuit Test

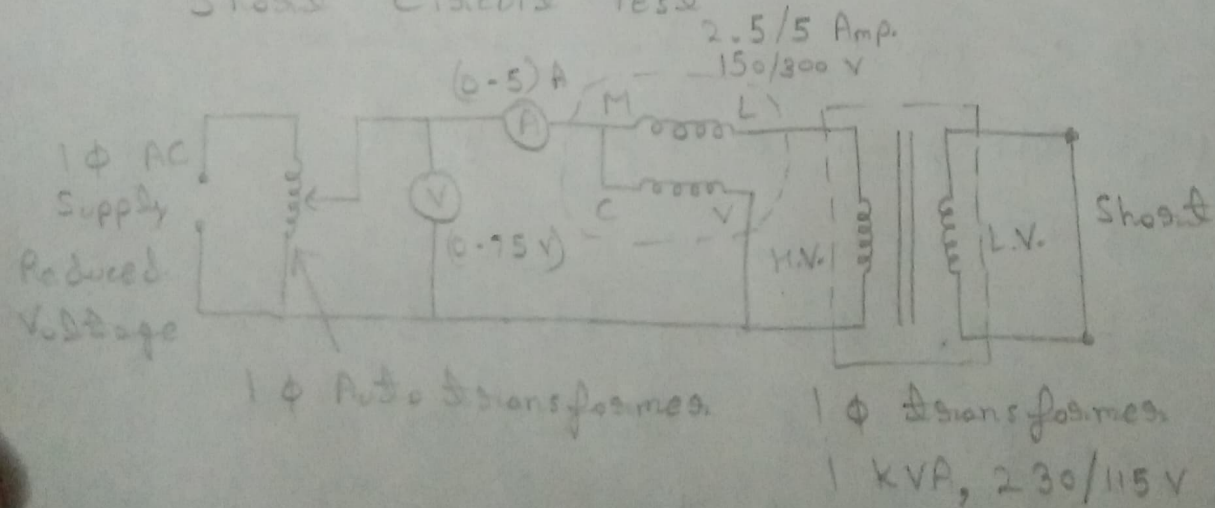

Short Circuit Test



TUTORIAL / PRACTICAL NO.

Object:- To determine efficiency and regulation of a 1- ϕ transformer by open-circuit and short-circuit test.

Apparatus Used:-

- 1- ϕ Transformer 1 KVA 1 No.
- 1- ϕ Auto transformer 0-300 V 1 No.
- Ammeter (0-1) Amp. 1 No.
- Ammeter (0-5) Amp. 1 No.
- Voltmeter (0-75 V) & (0-300 V) 1 No.
- Wattmeter 2.5/5 Amp. 1 No.
(0-150/300) V

Theory:-

The efficiency of transformer can be calculated as-

$$\begin{aligned}\text{Efficiency } \eta &= \frac{\text{Output}}{\text{Input}} \\ &= \frac{\text{Output}}{\text{Output} + \text{Losses}} \\ &= \left[1 - \frac{\text{Losses}}{(\text{Output} + \text{Losses})} \right]\end{aligned}$$

When $\cos \theta = W_{sc} / I_1 V_1$

Observation Table :-

Open Circuit Test

S.No	Input Voltage V_1	No Load Current I_0	Wattmeter Reading W
1	230V	0.52 A	5×2

Short Circuit Test

S.No	Short Circuit Voltage	Full Load Current I_{sc}	Wattmeter Reading W_{sc}
1	28V	4.3 A	10×2

TUTORIAL / PRACTICAL NO.

Calculation :-

η is calculated as given formula

$$\eta = \frac{x S \cos \phi}{x S \cos \phi + P_i + P_c x^2}$$

where,

$$P_i = W, P_c = W_{sc}$$

S = rated V_A of the transformer

x = fraction of the full load transformer

As given transformer is fully loaded,

$$\therefore x = 1$$

$$\therefore P_c = 20 \text{ W}$$

$$\therefore P_i = 10 \text{ W}$$

$$\therefore S = 1 \text{ KVA}$$

$$P = VI \cos \phi$$

$$10 = 230 \times 0.52 \times \cos \phi$$

$$\cos \phi = \frac{10}{230 \times 0.52} = 0.083$$

$$\eta = \frac{1 \times 10^3 \times 0.083}{1 \times 10^3 \times 0.083 + 10 + 20 \times 1} \Rightarrow \frac{83}{113}$$

$$\boxed{\eta = 0.73}$$

TUTORIAL / PRACTICAL NO.

Result:- Efficiency of a given

1- ϕ transformer is 0.73

Precaution:-

- 1) All connections should be tight
- 2) Under short circuit test
Auto transformer should move
from zero voltage.