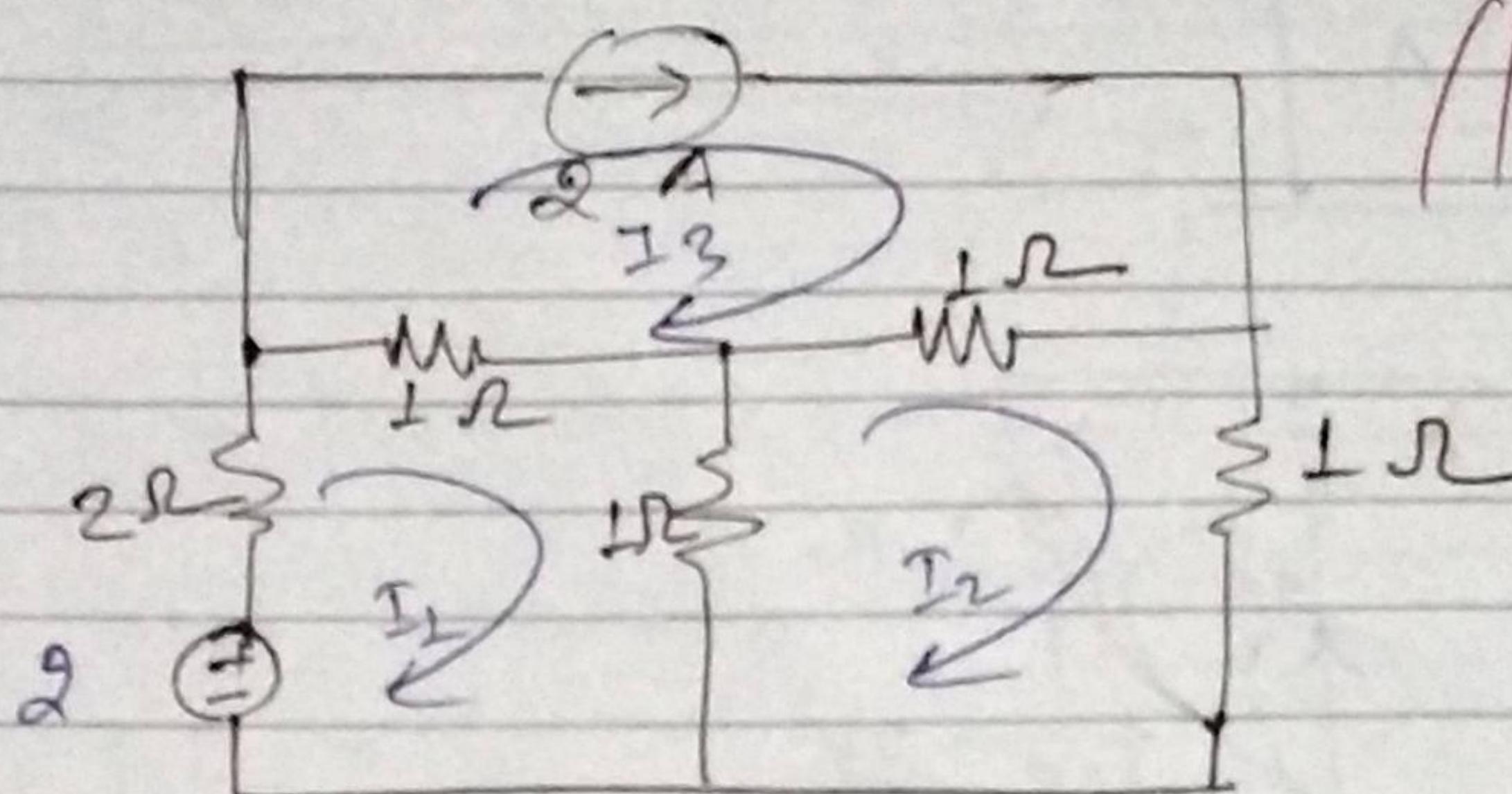


Ques. Find the mesh current in the below N/W -



// Single mesh bcz
current source
is only in one
mesh. //

① :-

$$-2 + 2I_1 + (I_1 - I_3) - (I_1 - I_2) = 0$$

$$4I_1 - I_2 - I_3 = 2 \quad \textcircled{1}$$

② :-

$$(I_2 - I_3) + I_2 + (I_2 - I_1) = 0$$

$$-I_1 + 3I_2 - I_3 = 0 \quad \textcircled{2}$$

③ :- $I_3 = 2A \quad \textcircled{3}$

③ in ① & ② :-

$$4I_1 - I_2 = 4 \quad \textcircled{4}$$

$$-I_1 + 3I_2 = 2 \quad \textcircled{5}$$


$$3 \times \textcircled{4} + \textcircled{5} \div$$

$$11 I_1 = 14 \quad \boxed{E_1 = \frac{14}{11} A}$$

$$-\frac{14}{11} + 3I_2 = 2 \Rightarrow 3I_2 = 2 + \frac{14}{11}$$

$$\boxed{I_2 = \frac{12}{11} A}$$

Ques :-

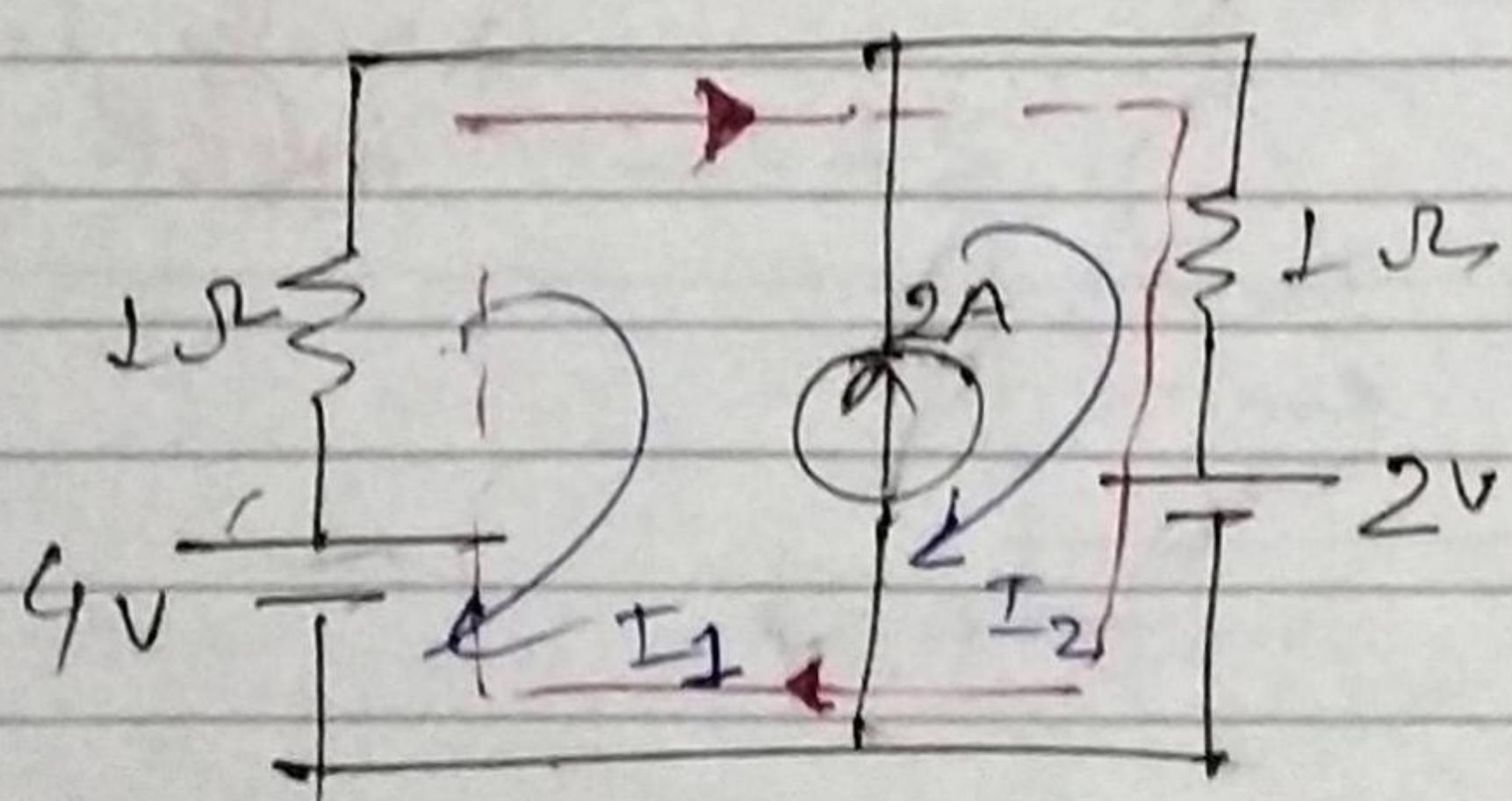

$$\text{Super mesh :-} \quad -4 + I_1 + I_2 + 2 = 0$$

$$I_1 + I_2 = 2 \quad \textcircled{1}$$


$$-I_1 + I_2 = 2 \quad \textcircled{2}$$

$$\textcircled{1} + \textcircled{2} \quad -2I_2 = 4 \quad \boxed{I_2 = 2A} \quad \boxed{I_1 = 0 A}$$

Nodal Analysis :-

Procedure :-

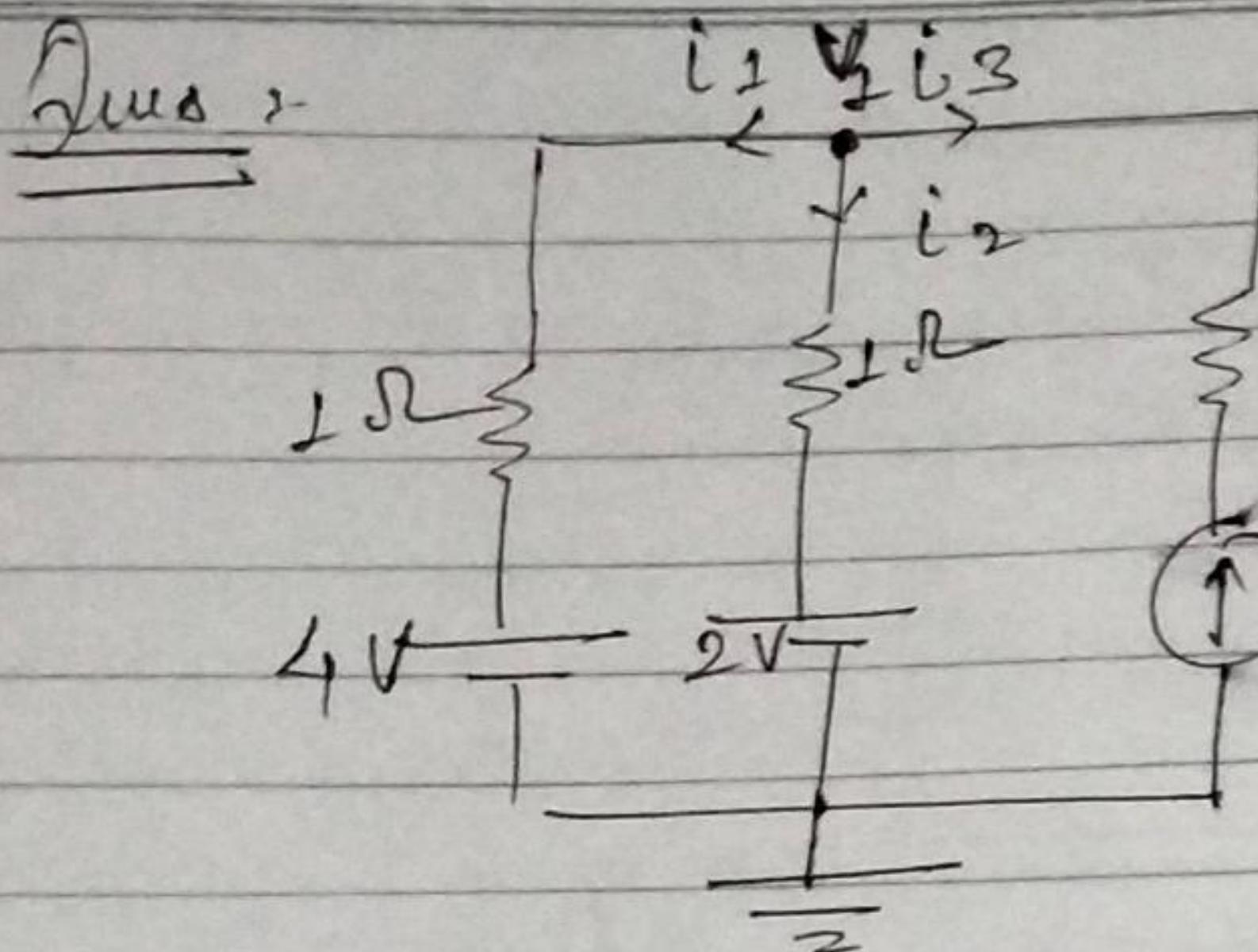- * Identify total no of nodes.
- * Assign the voltage at each node, one of the node is taken as the reference node. (OR datum) And the reference node potential should be equal to the ground potential.
- * Develop KCL eqns for each non reference node.
- * By solving RCL ~~no~~ eqns find node voltages.




$$i_1 + i_2 + i_3 = 0$$

$$\frac{(V_1 - 0) - 4}{1} + \frac{(V_1 - 0) - 2}{1} = 0$$

$$2V_1 - 4 - 2 - 2 = 0$$

$$\boxed{V_1 = 4V}$$

Ques 3:-

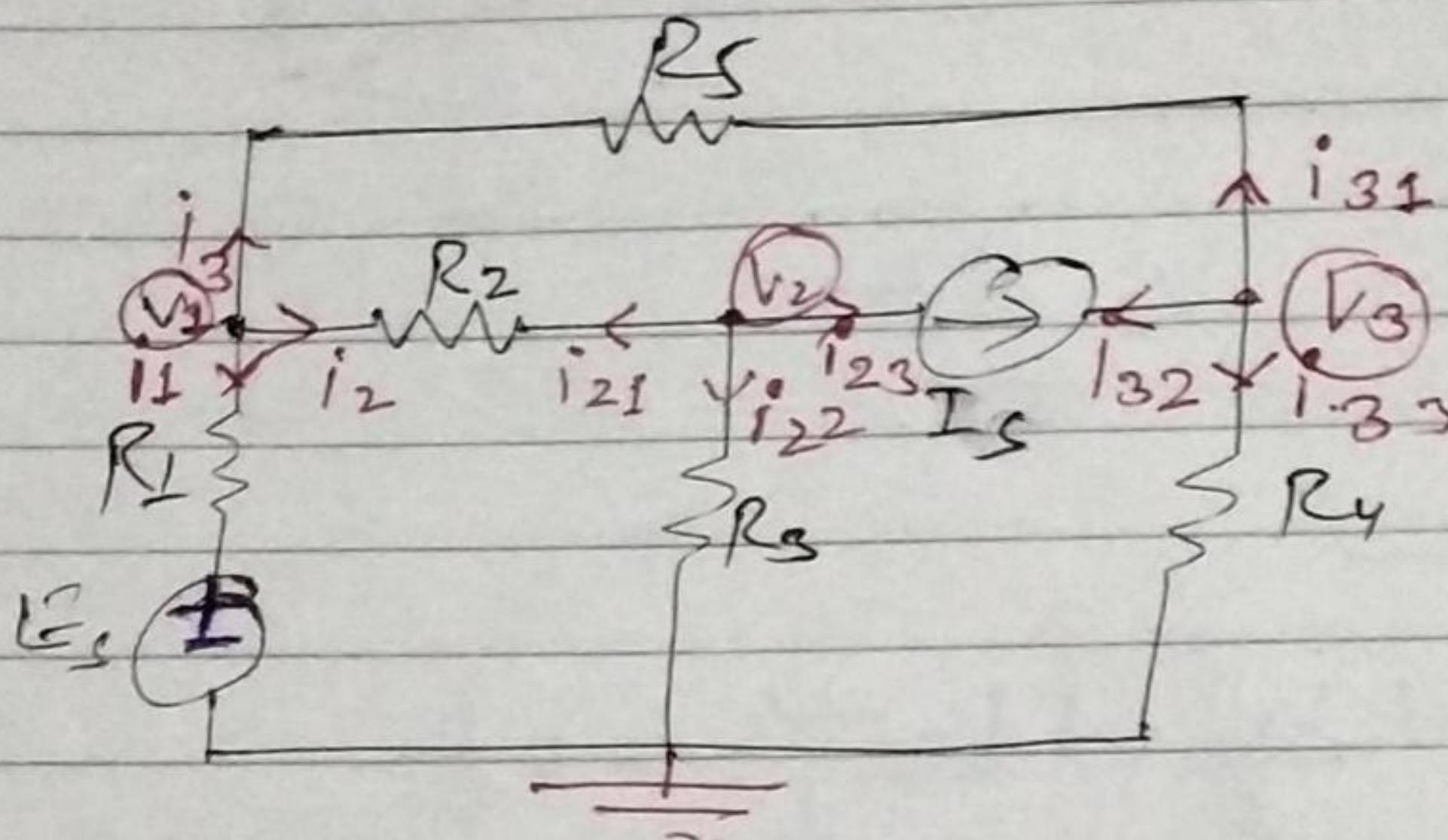

Node 1 :-

$$i_1 + i_2 + i_3 = 0$$

$$\frac{(V_1 - 0) - E_s}{R_1} + \frac{(V_1 - V_2)}{R_2} + \frac{V_1 - V_3}{R_5} = 0$$

Node 2 :-


$$i_{21} + i_{22} + i_{23} = 0$$

$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - 0}{R_3} + I_s = 0$$

Node 3 :- $i_{31} + i_{32} + i_{33} = 0$

$$\frac{V_3 - V_1}{R_5} - I_s + \frac{V_3 - 0}{R_4} = 0$$

Ans.

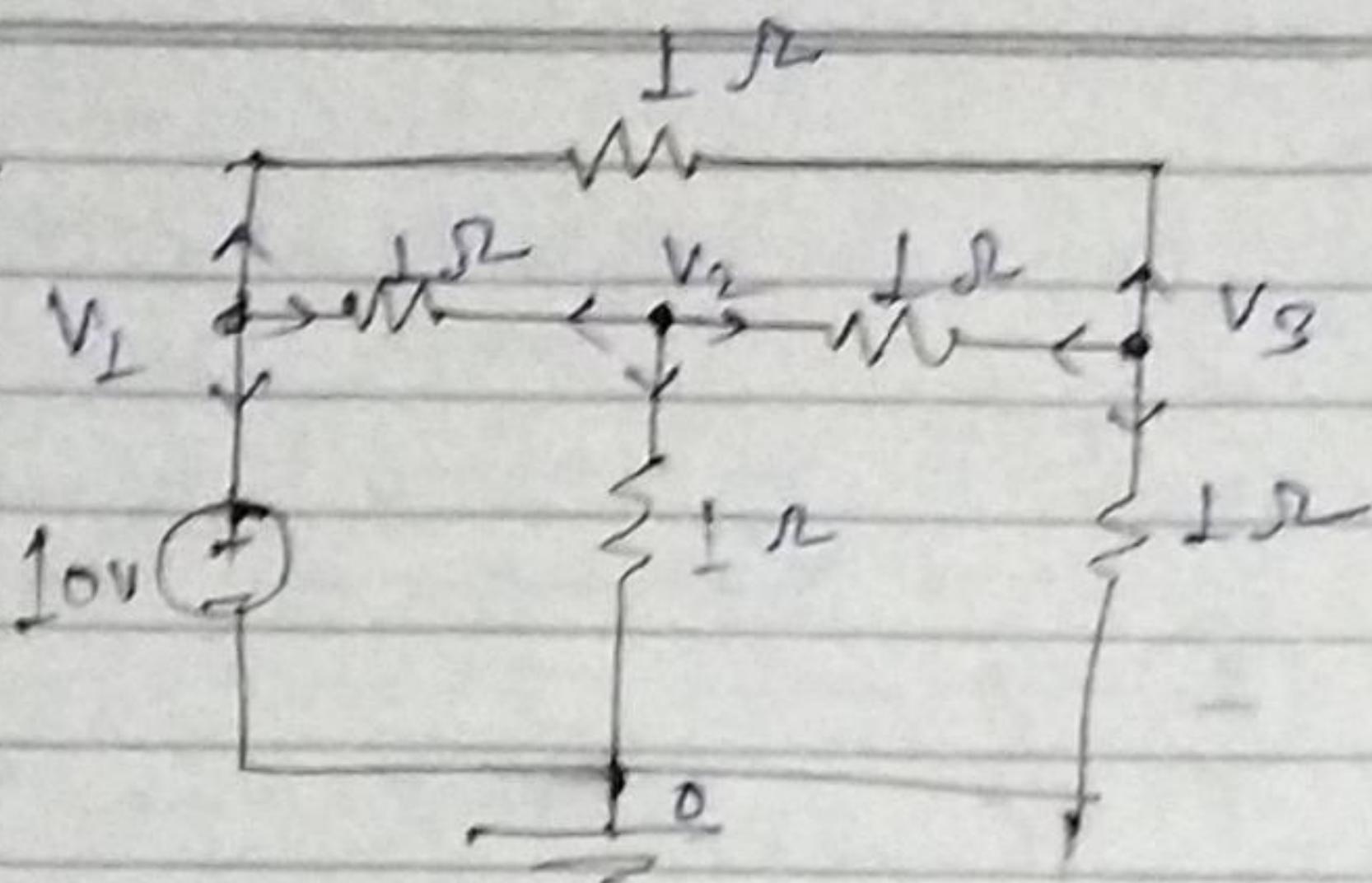

$$\boxed{\frac{V_1 - 0}{1} = 10 \quad V_1 - V_2 + V_1 - V_3 = 0}$$

At Node ① :- $V_1 = 10V$

At Node ② :-

$$\frac{V_2 - 10}{1} + \frac{V_2}{1} + \frac{V_2 - V_3}{1} = 0$$

$$3V_2 - V_3 = 10 \quad \textcircled{1}$$

At Node ③ :-

$$\frac{V_3 - 10}{1} + \frac{V_2 - V_3}{1} + \frac{V_3}{1} = 0$$

$$-V_2 + 3V_3 = 10 \quad \textcircled{2}$$

$$\textcircled{1} \times 3 + \textcircled{2}$$


$$8V_2 = 40V$$

$$-5 + 3V_3 = 10$$

$$\boxed{V_2 = 5V}$$

$$3V_3 = 15$$

$$\boxed{V_3 = 5V}$$

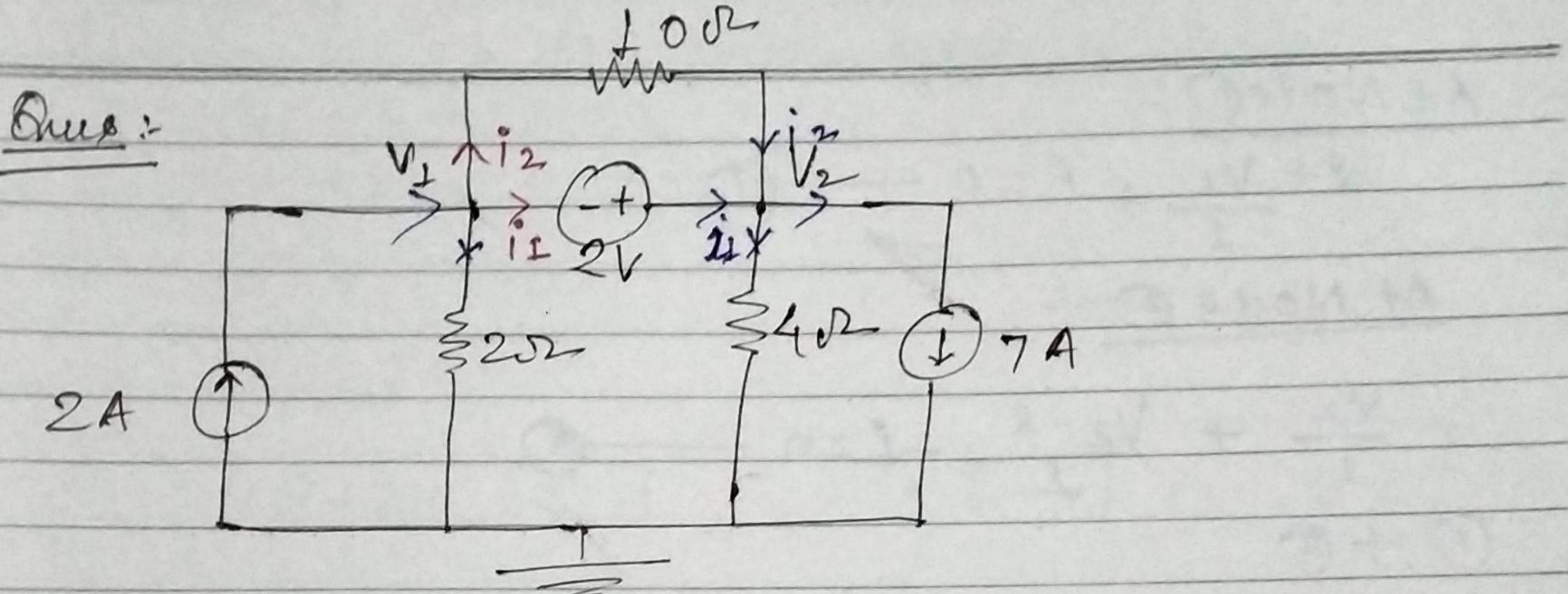

At Node ① :-

$$-2 + \frac{v_1}{2} + i_1 + i_2 = 0 \quad \text{--- } ①$$

At Node ② :-

$$-i_2 - i_1 + \frac{v_2}{4} + 7 = 0 \quad \text{--- } ②$$

① + ②


$$-2 + \frac{v_1}{2} + \frac{v_2}{4} + 7 = 0 \rightarrow \text{Super Node by } ①$$

from first node and from the Ckt from second node

$$v_2 - v_1 = 2 \quad \text{--- } ③$$

$$\therefore v_1 = -7.33V \quad v_2 = -5.33V$$

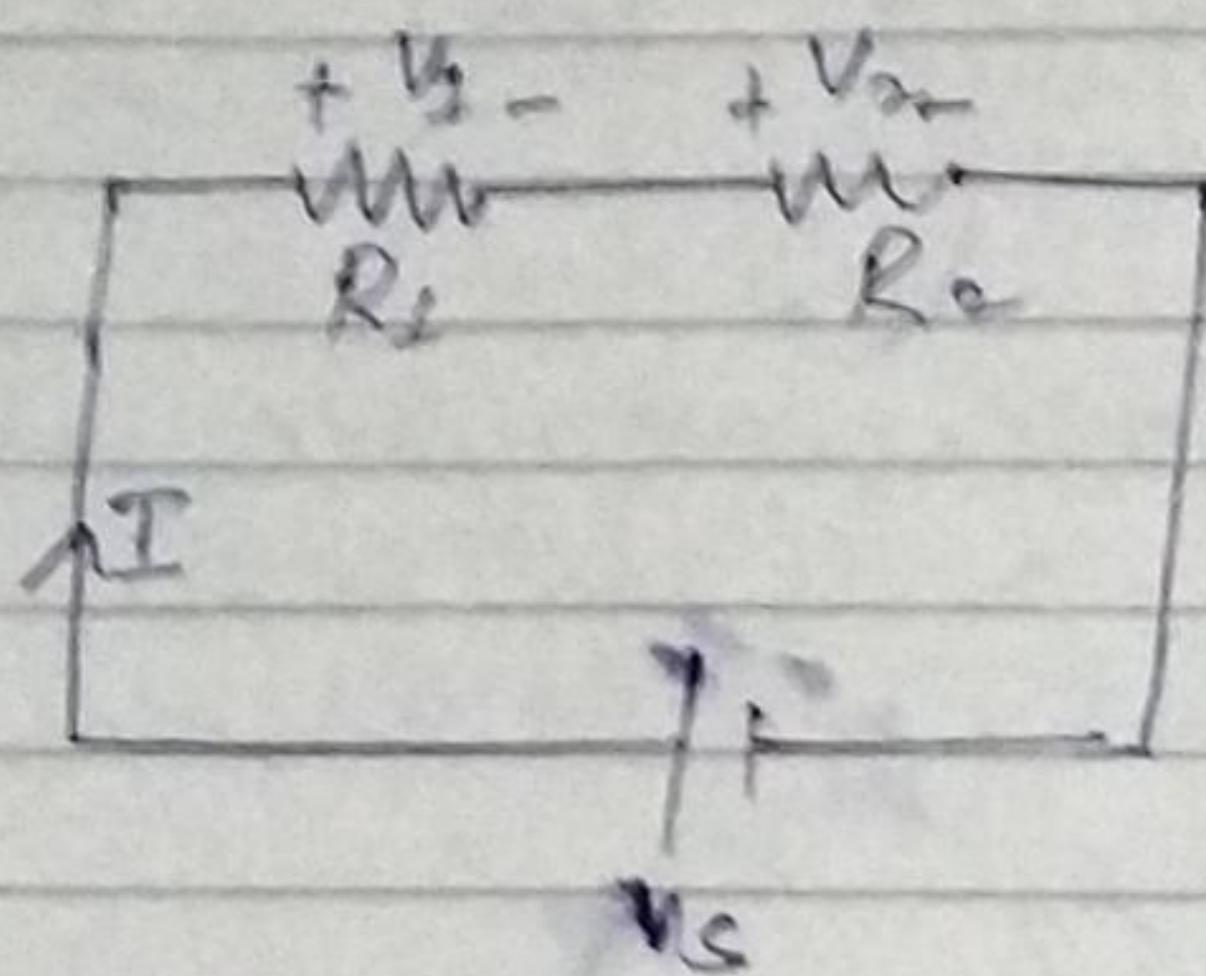
Voltage Division in Series Combination :-



$$R_{eq} = R_1 + R_2$$

$$V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$$


$$V_2 = V_s = \frac{R_2}{R_1 + R_2}$$

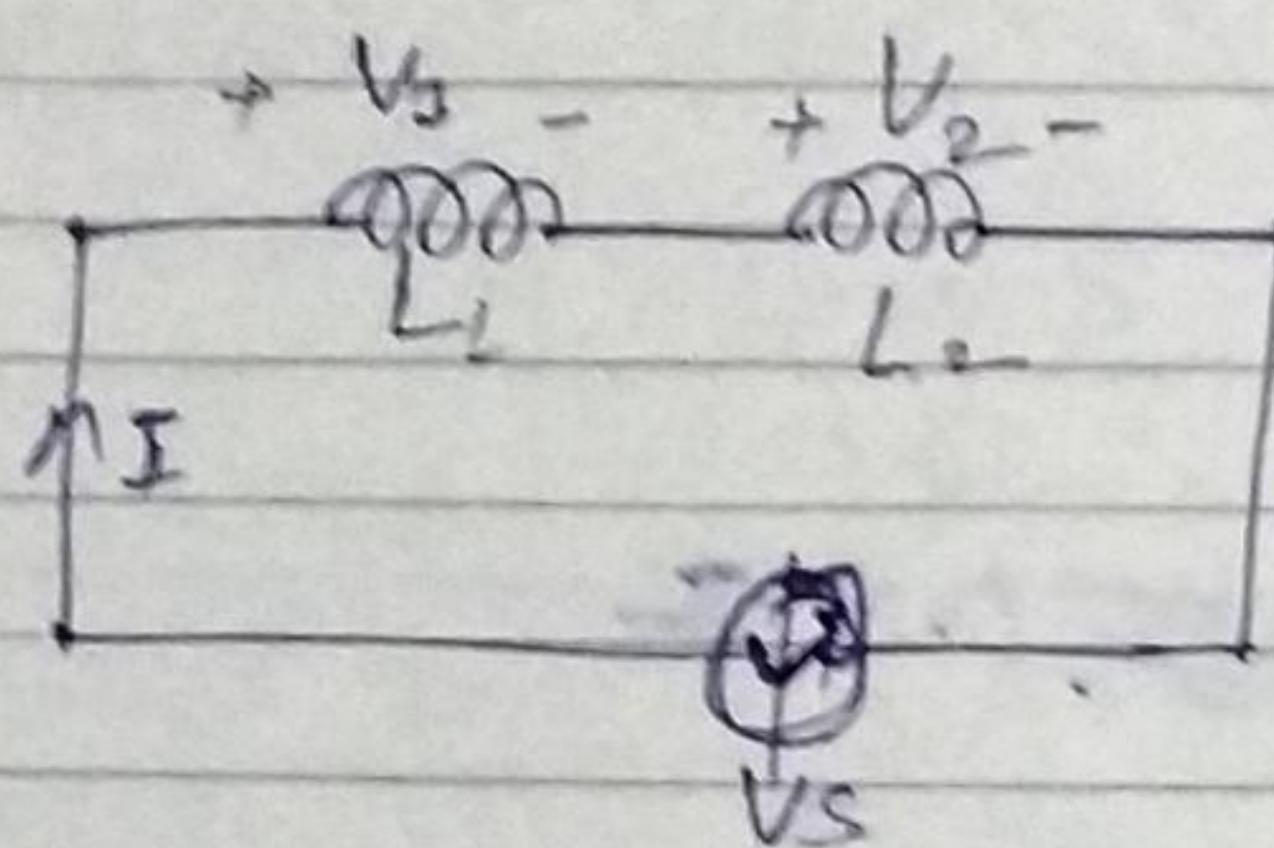

$$L_{eq} = L_1 + L_2$$

$$V_1 = V_s \left(\frac{L_1}{L_1 + L_2} \right)$$
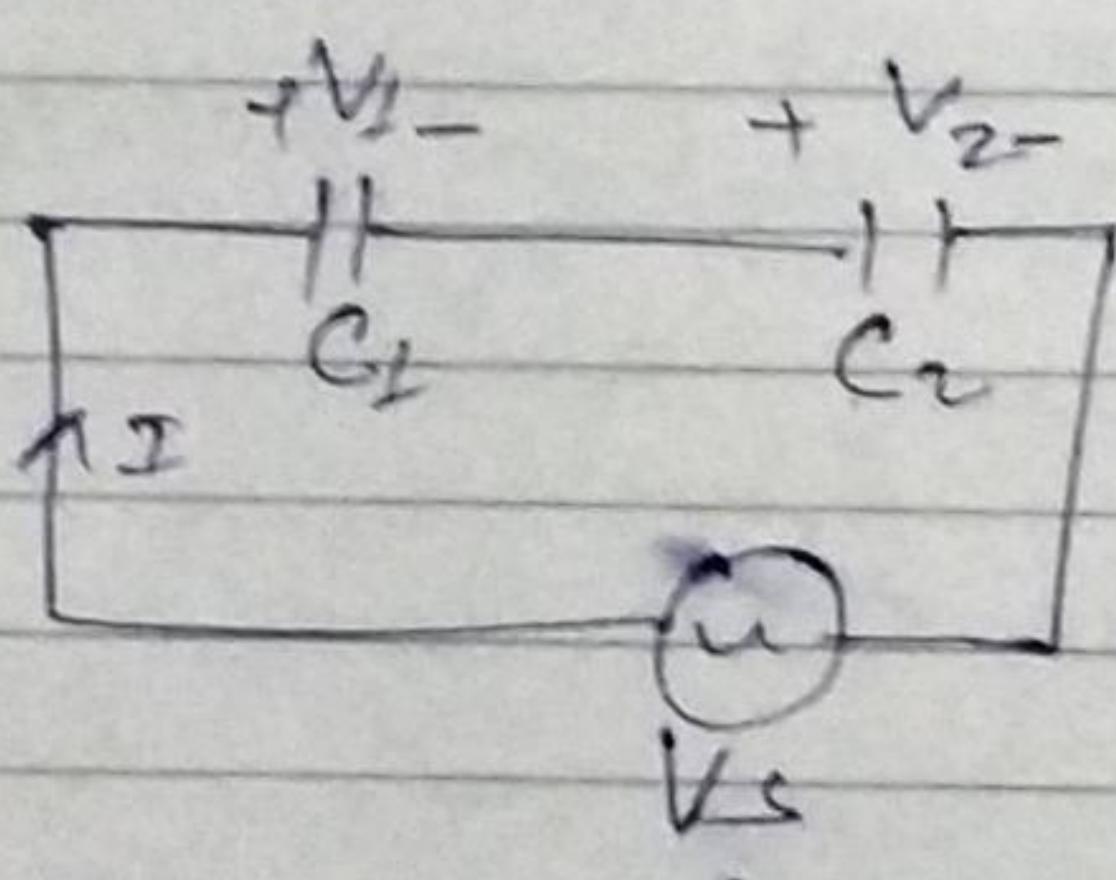
$$V_2 = V_s \left(\frac{L_2}{L_1 + L_2} \right)$$



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$V_1 = V_s \cdot \frac{C_2}{C_1 + C_2}$$

$$V_2 = V_s \cdot \frac{C_1}{C_1 + C_2}$$

$$V_1 = V_s \cdot \frac{1}{j\omega C_1}$$

$$\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} = \frac{V_s C_1 C_2}{C_1 + C_2} \left(\frac{1}{j\omega C_1} \right)$$

$$V_1 = \frac{V_s C_2}{C_1 + C_2}$$

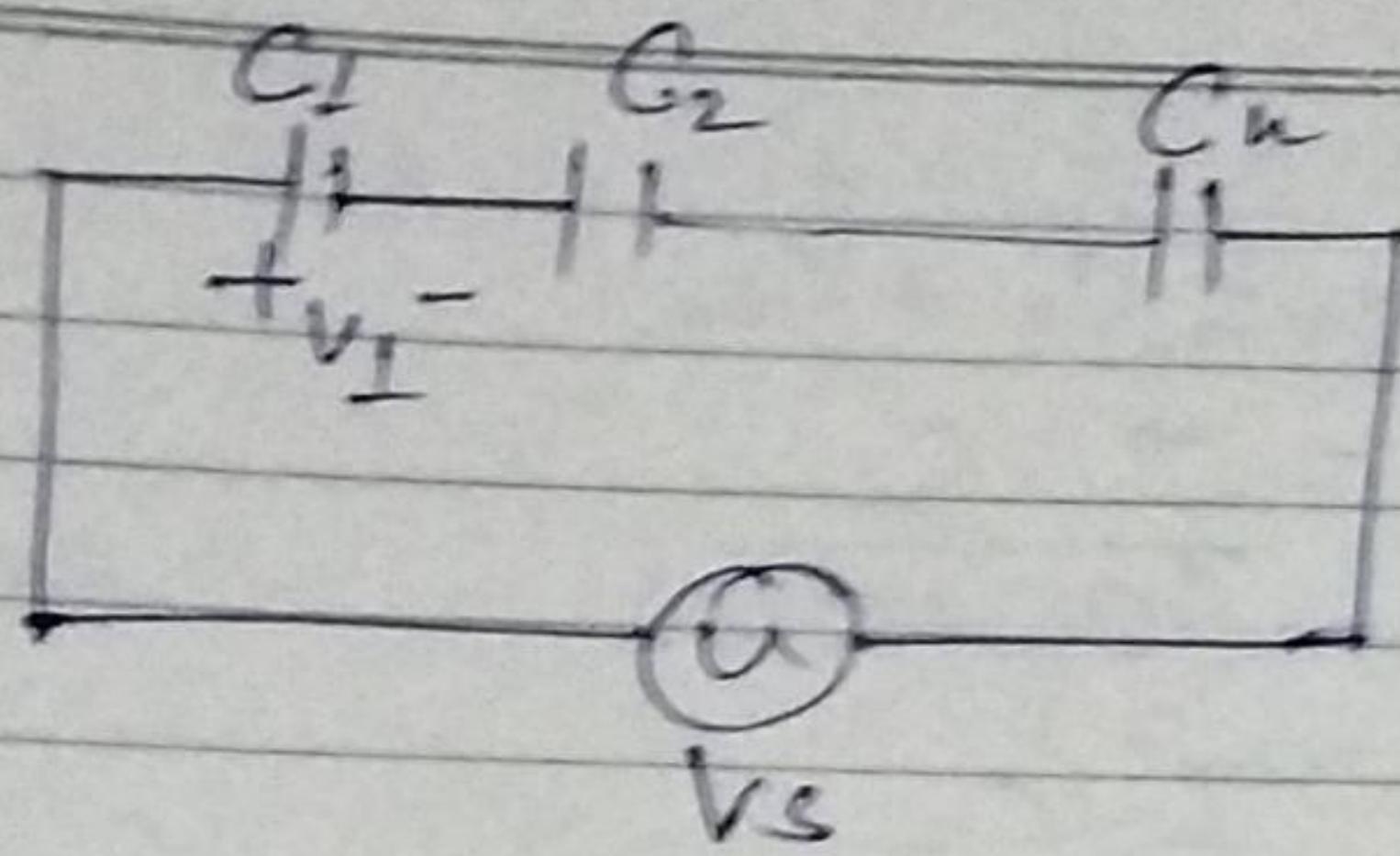


$$V_L = V_s \cdot \frac{1}{\frac{1}{C_L} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

$$\left[\frac{1}{C_L} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right]$$

$$V_L = \frac{V_s}{\left(\frac{1}{j\omega C_L} + \frac{1}{j\omega C_2} + \dots + \frac{1}{j\omega C_n} \right)} \times \frac{1}{j\omega C_L}$$


$$\left[\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right]$$

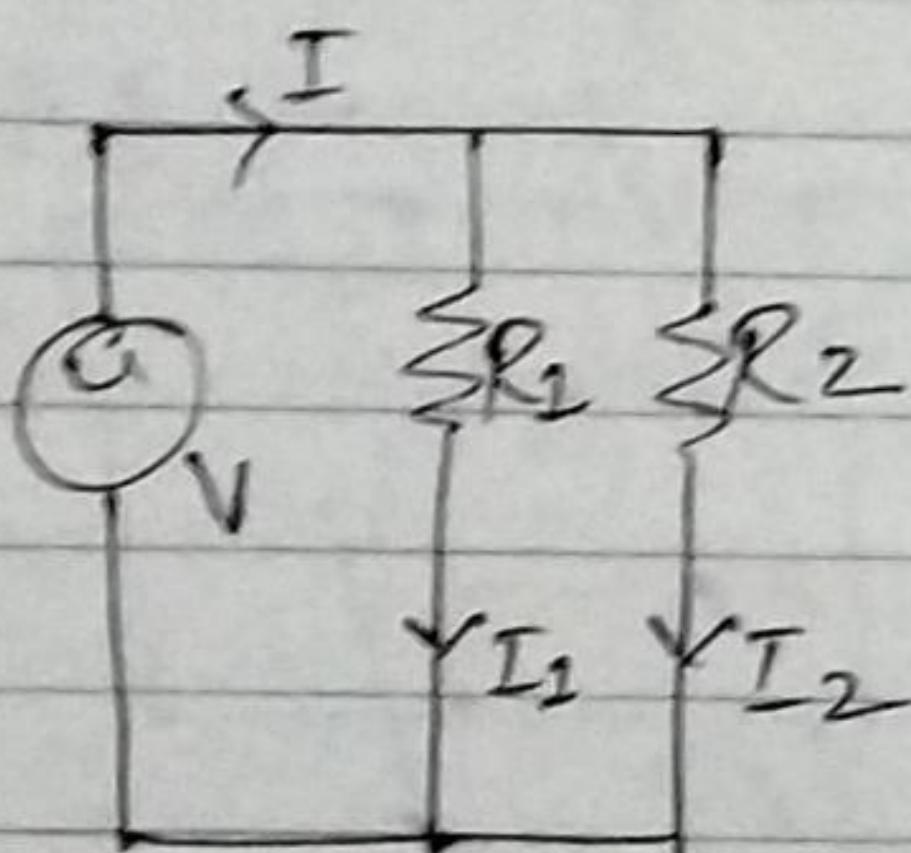Parallel Combination in Current Division:-




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$
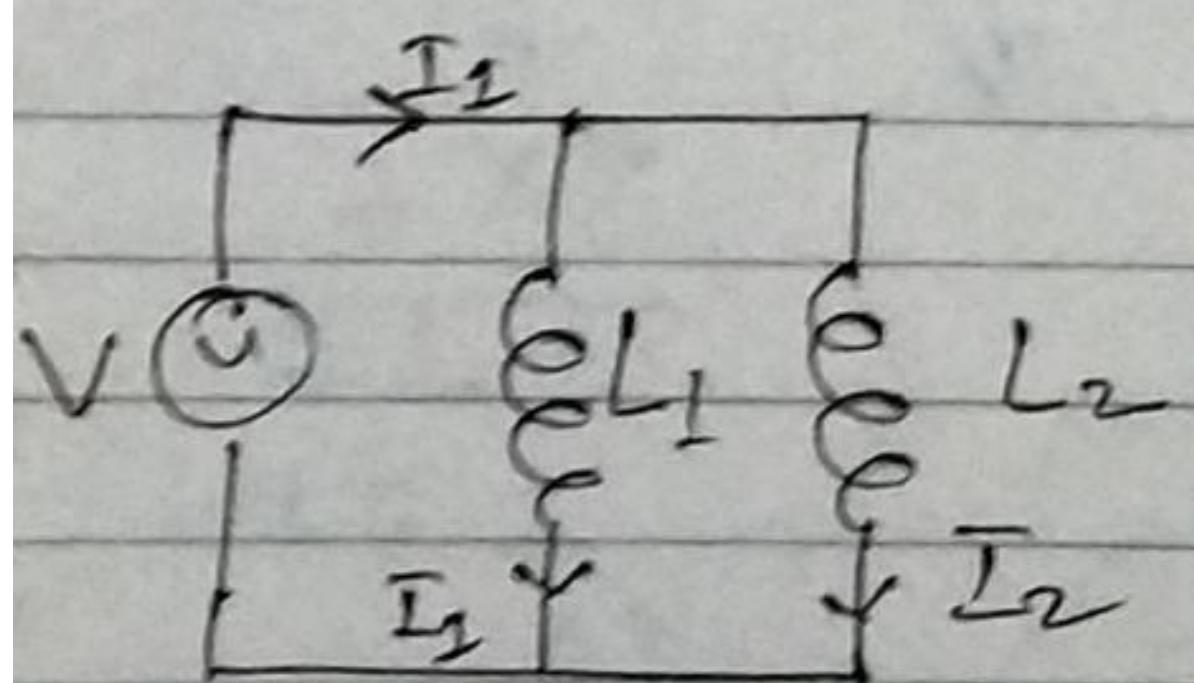
$$I_1 = \frac{I \cdot R_2}{R_1 + R_2} \quad I_2 = \frac{I \cdot R_1}{R_1 + R_2}$$




$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

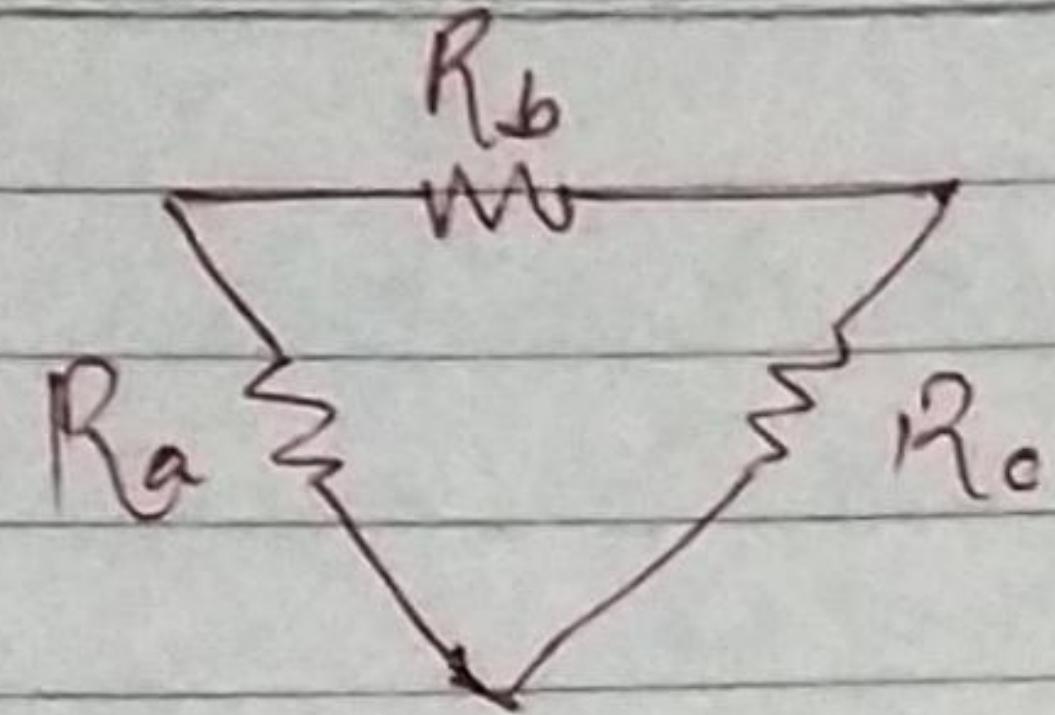
$$I_1 = \frac{I \cdot L_2}{L_1 + L_2} \quad I_2 = \frac{I \cdot L_1}{L_1 + L_2}$$



DELTA

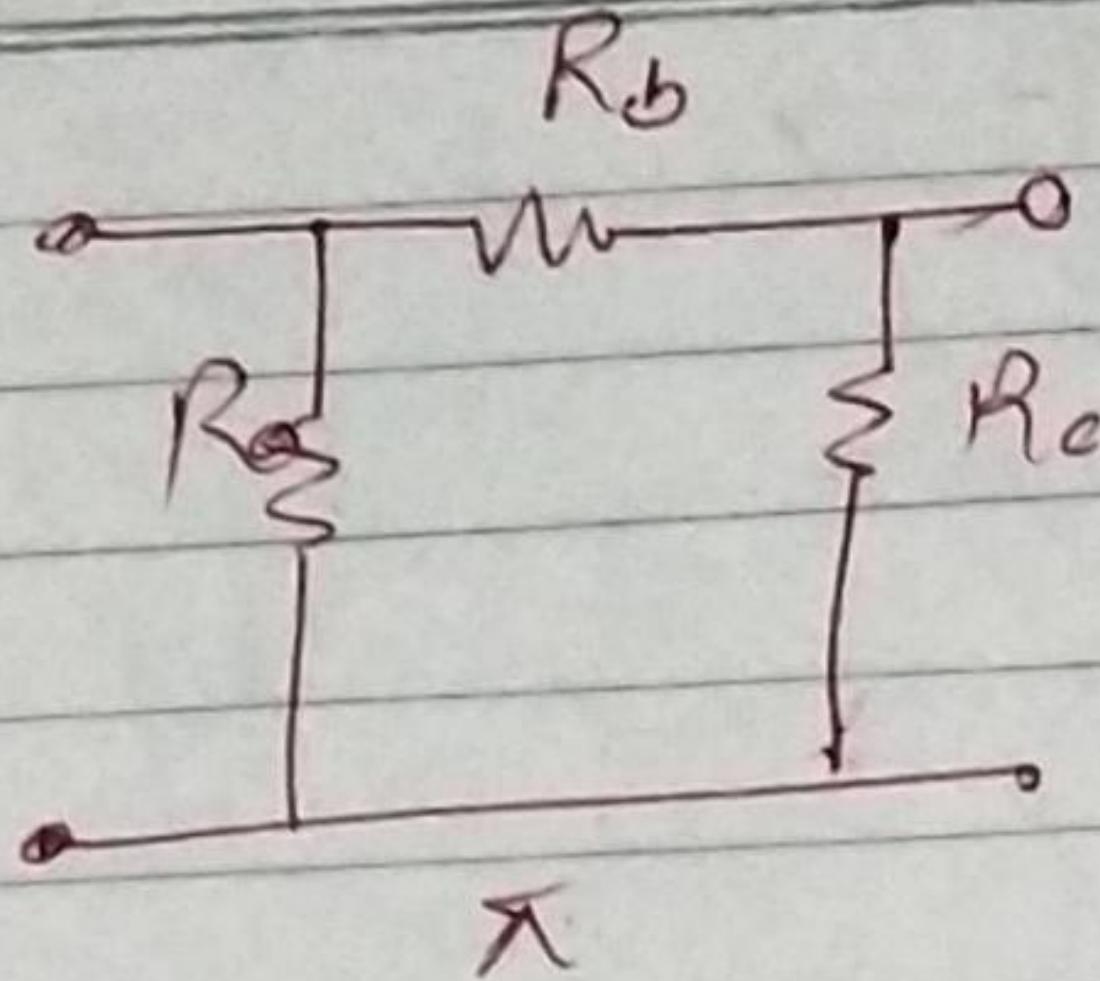

Delta to Star :-

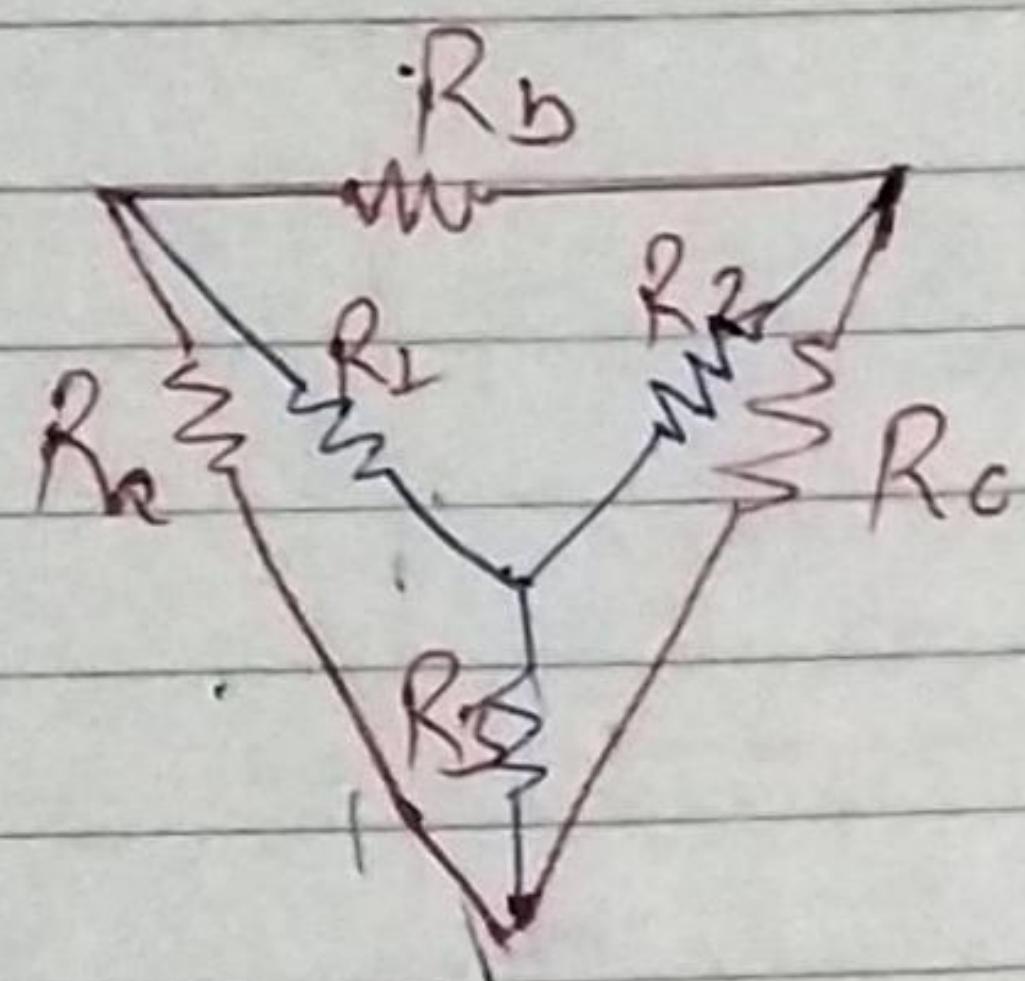

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$


Star to Delta :-

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Ques

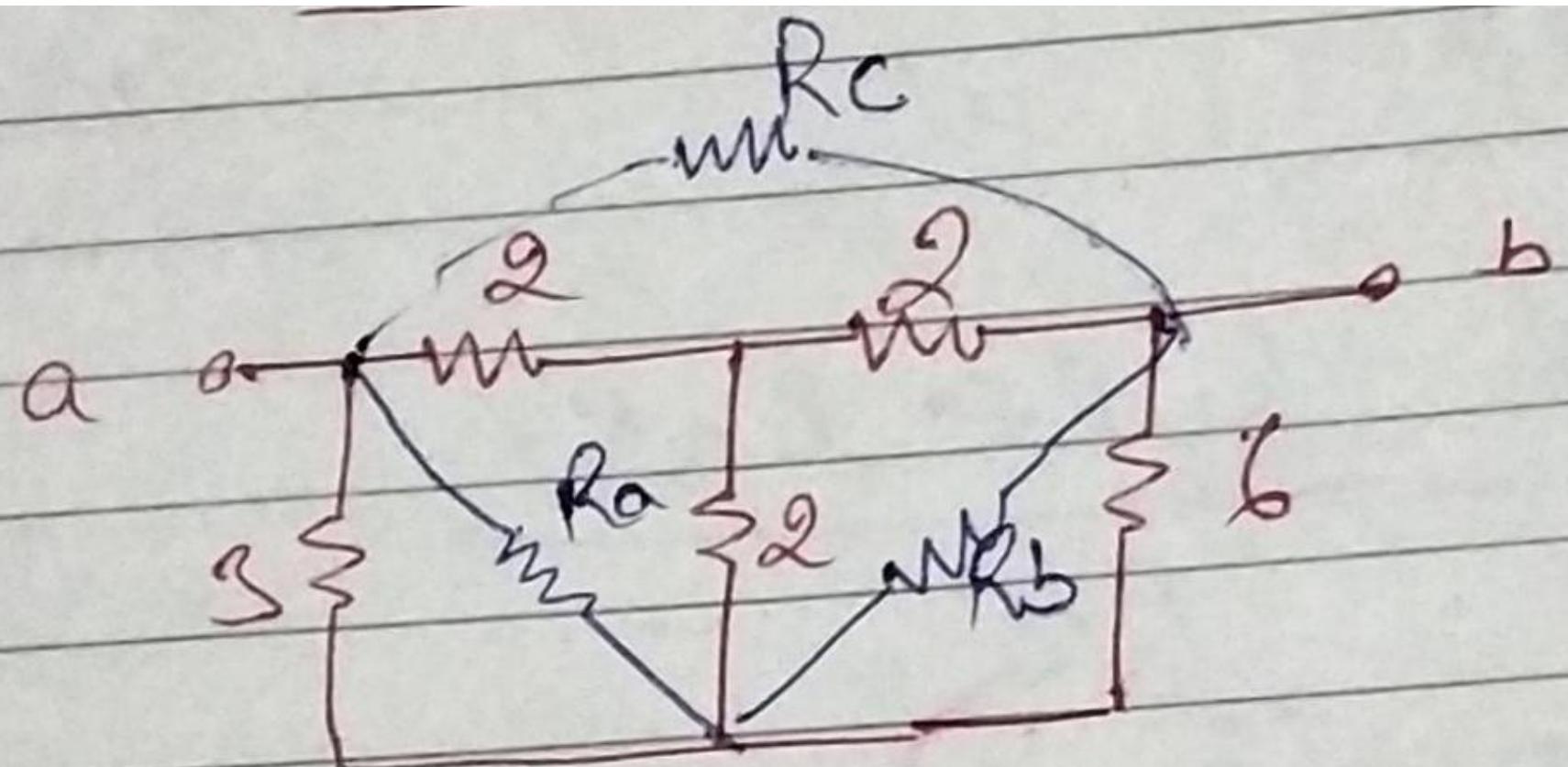


Star to Delta

$$R_a = \frac{2 \times 2 + 2 \times 2 + 2 \times 2}{2} = 6 \Omega$$

$$R_b = \frac{2 \times 2 + 2 \times 2 + 2 \times 2}{2} = 6 \Omega$$


$$\text{and, } R_c = 6 \Omega$$

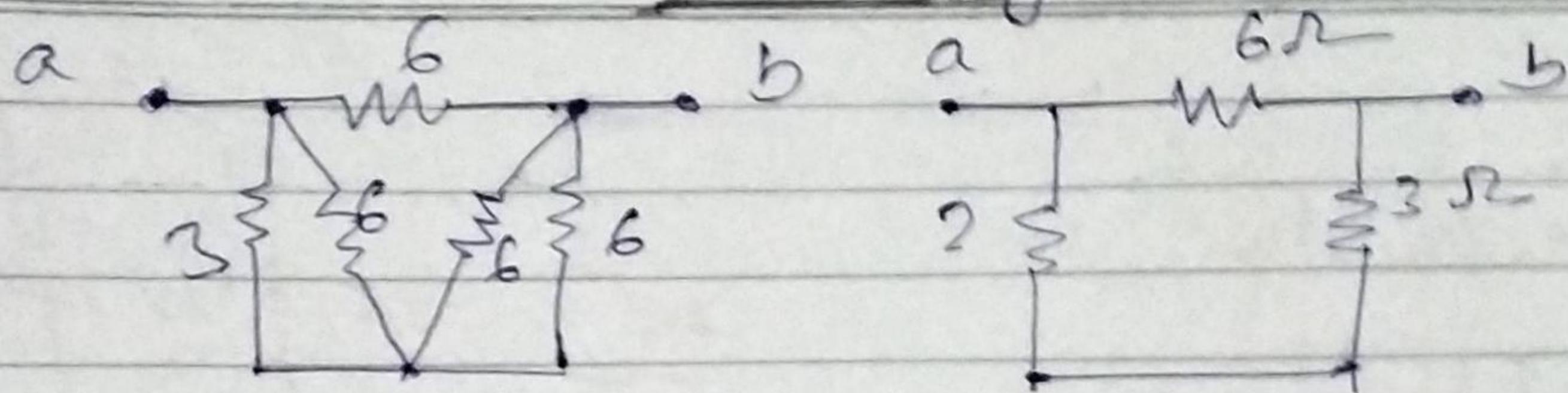NOTE:- ① When Resistors of equal value transform from star to delta the resistance value increases by 3 times (and same of Inductance) ~~& proportionally~~
 ② When Capacitors of equal value transformed from Δ to star the capacitance value decreases by 3 times.





$$R_{ab} = 6/(2+3) \Rightarrow 6/5 = \frac{6 \times 5}{6+5} = \left(\frac{30}{11}\right) \Omega$$


Delta to Star :-

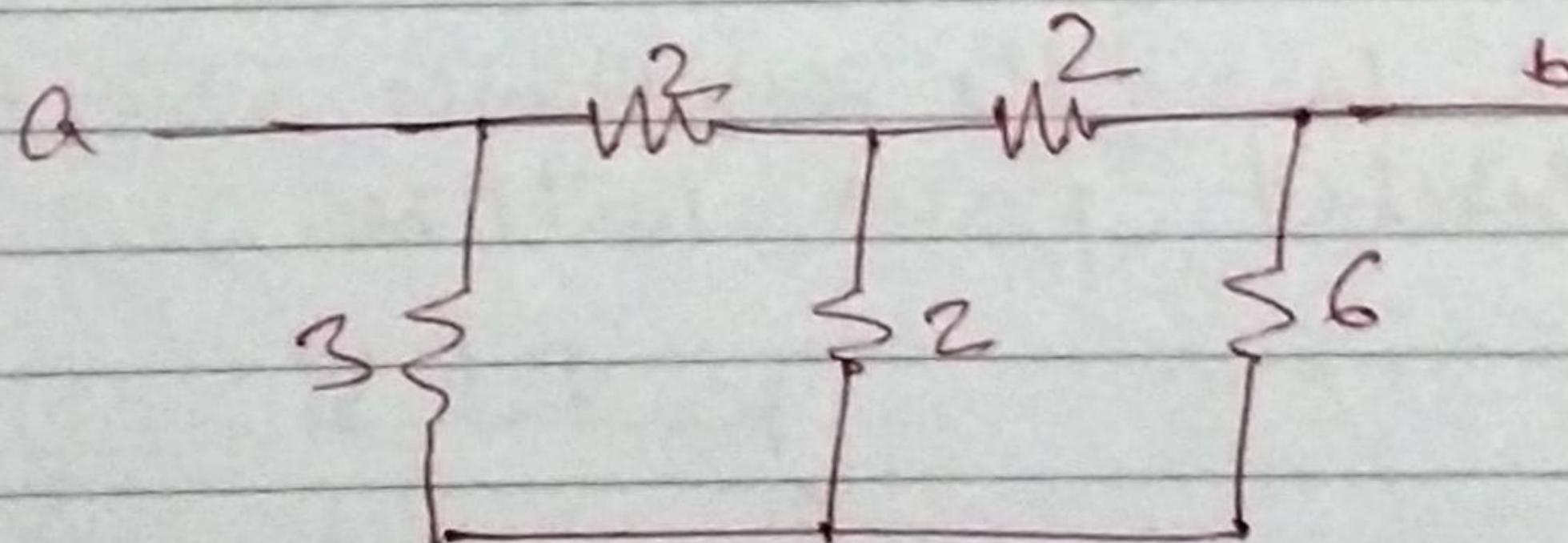

Ans :-

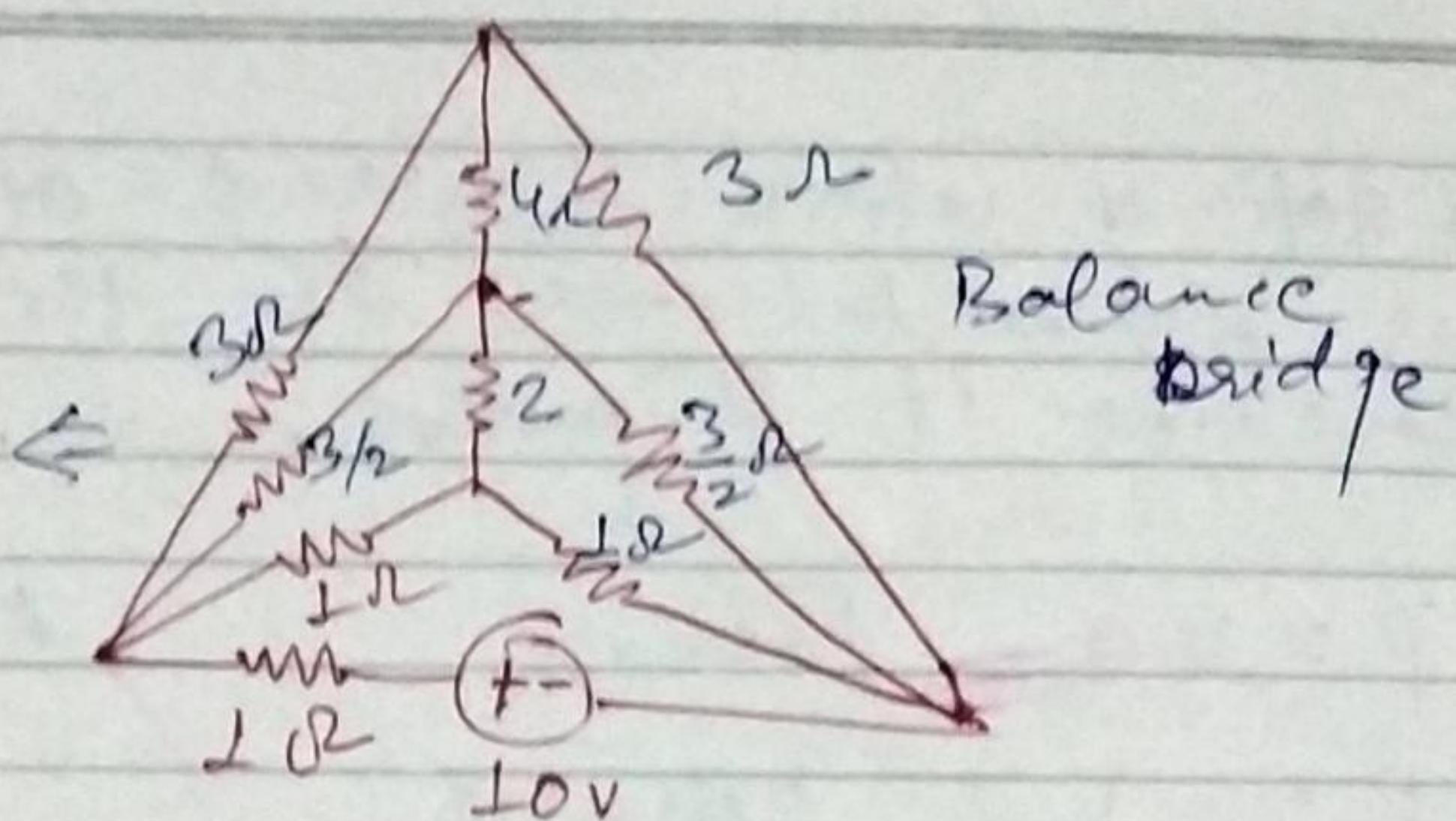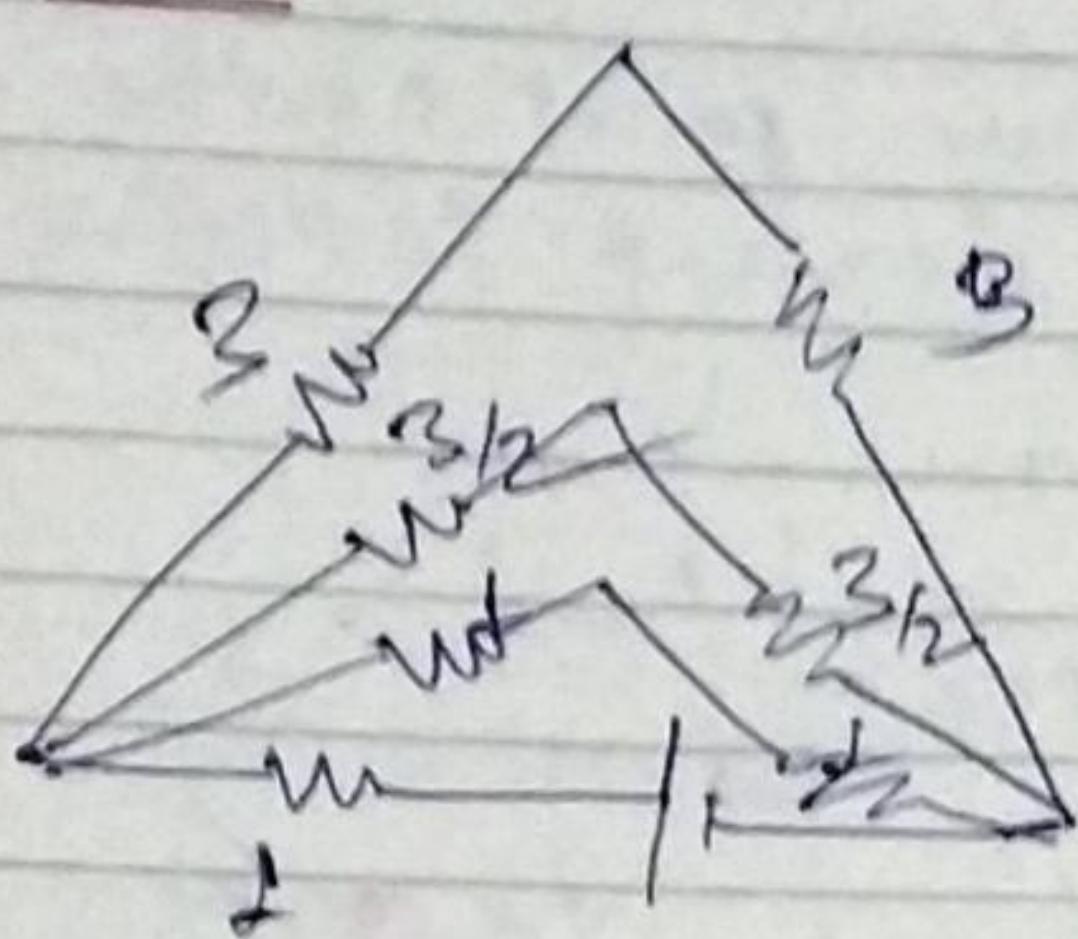
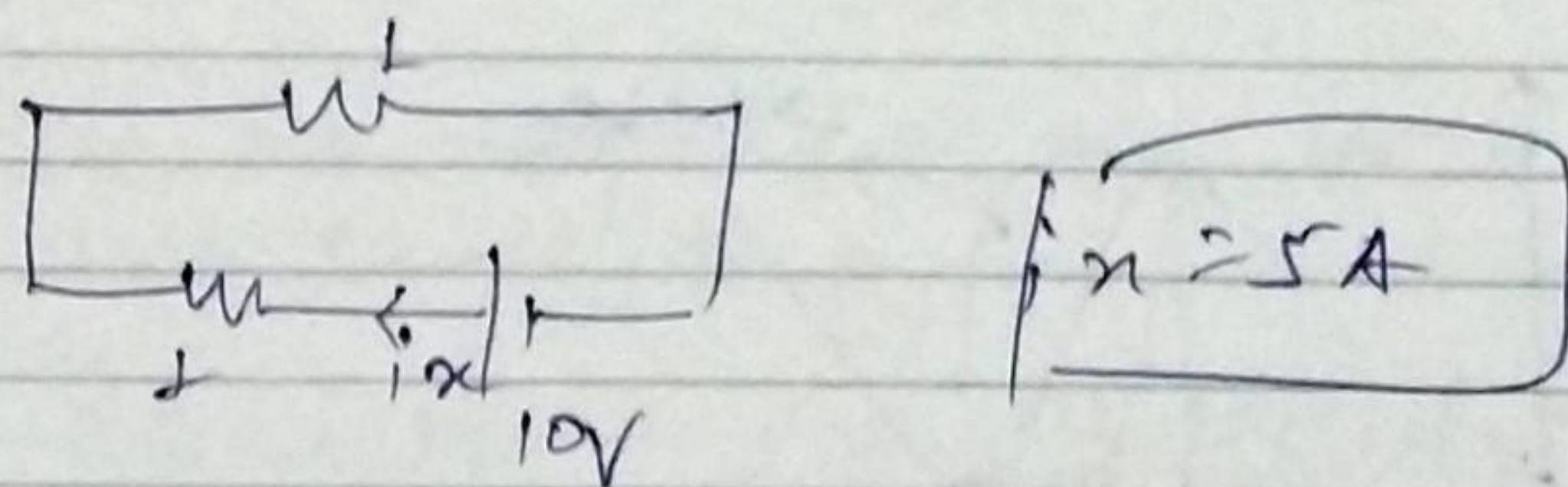
$$6 \parallel 3 \parallel 2 = 2 \parallel 2 = 1\Omega$$



Type of Elements :-

1: Active And Passive Elements:- Active Elements - when an element ~~is~~ is capable of delivering energy for infinite time or capable of providing power gain then the element is called as active element. for eg:- Current source, voltage source, transistor, opamp etc

Passive Elements:- When an element is not capable of providing energy independently for an infinite time or not capable of providing power gain then the element is called passive element.

E.g:- Resistor, Inductor, Capacitor, Transformer.

* If ratio of voltage to current at any point on the char. curve is ≥ 0 , then the element is active otherwise it is passive.

$$P = V I \quad \text{Passive}$$


$$P = -V I \quad \text{Delivered}$$

ACTIVE

V
Load
Passive $\frac{V}{I}$
+ve slope $\frac{V}{I}$

PASSIVE

ACTIVE
(-ve) slope

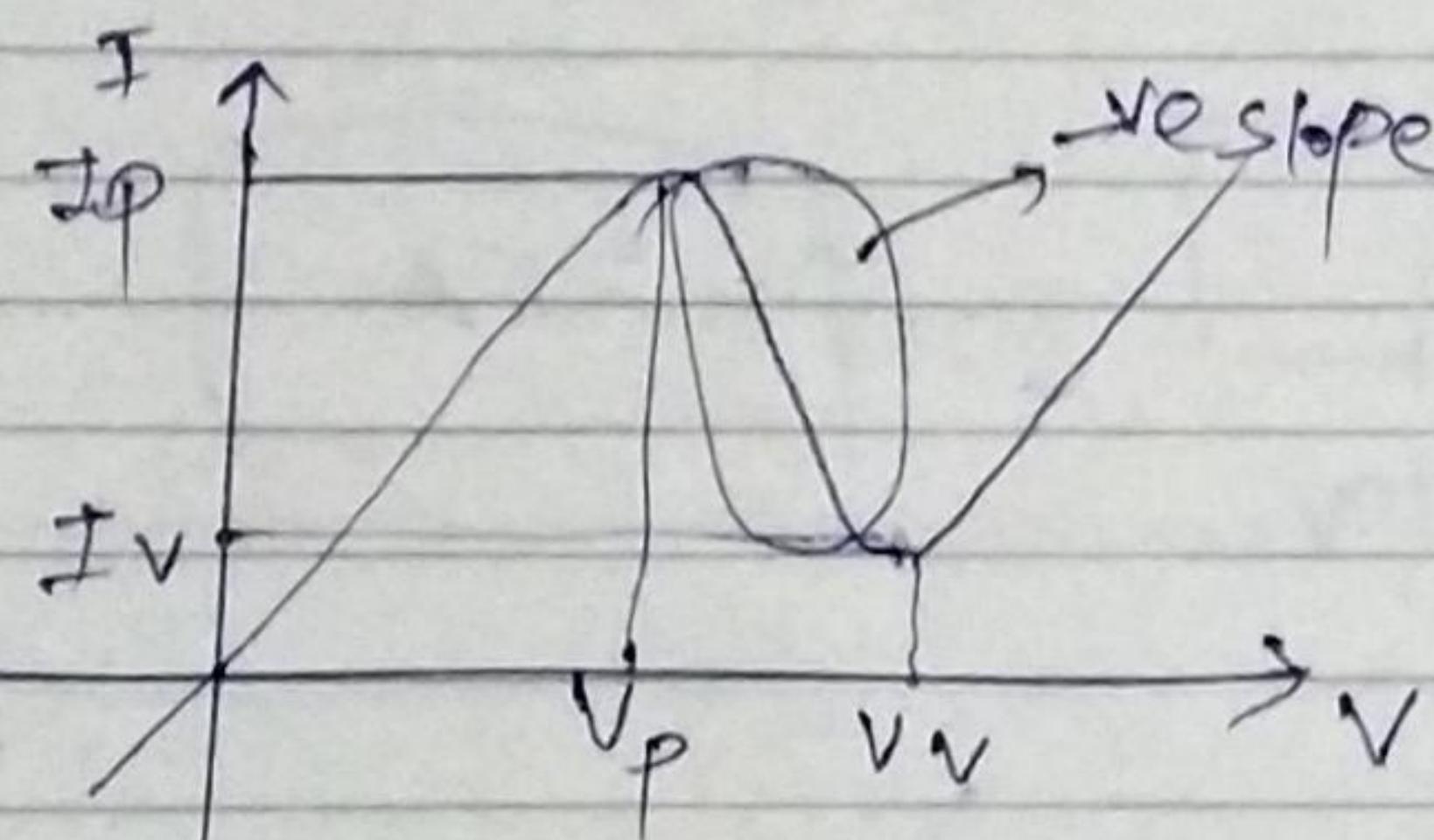


Tunnel Diode
Characteristics

Bidirectional And unidirectional Element :-

* Bidirectional — When element properties and char. are independent of the direction of the current then the element is called as bidirectional element.

Unidirectional — When element properties and char. depends upon the direction of the current then the element is called as unidirectional element.

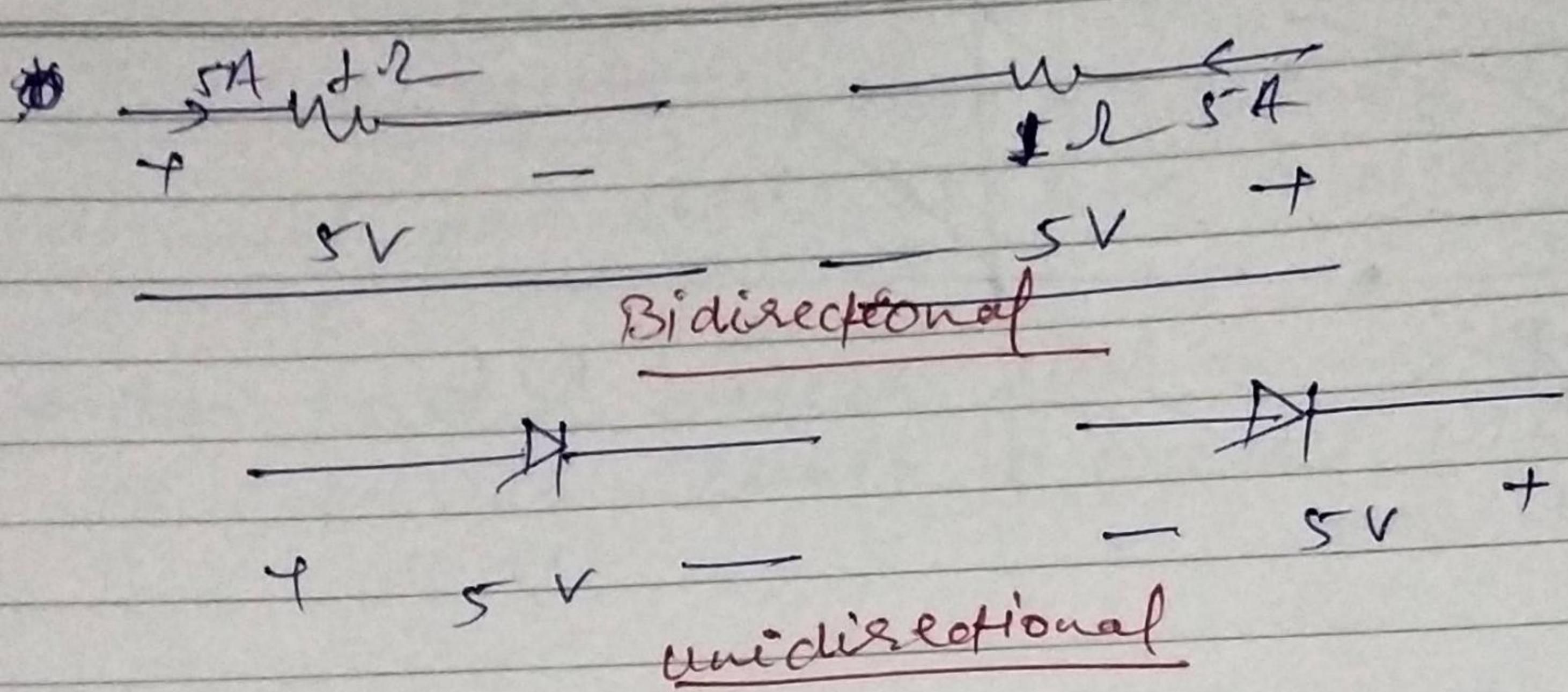* If the characteristic curve is similar in opposite quadrants then the element is bidirectional otherwise it is unidirectional.



Lumped Elements :- are considered as the separate elements which are very small in size.

Distributed Elements — are electrically non separable.

Linear And Non Linear Element :- ~~driving~~

* Linearity is the property of an element if ~~driving~~ a linear relationship b/w excitation and response.

* Every Linear element must exhibit bidirectional property.

