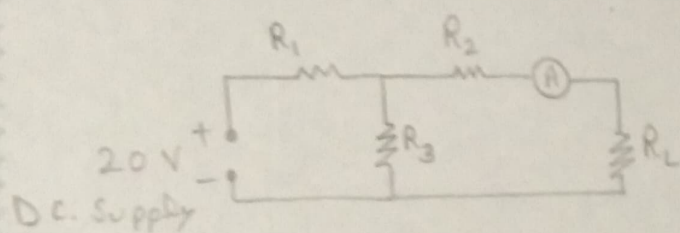
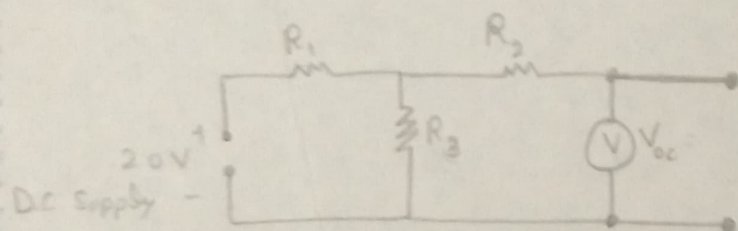
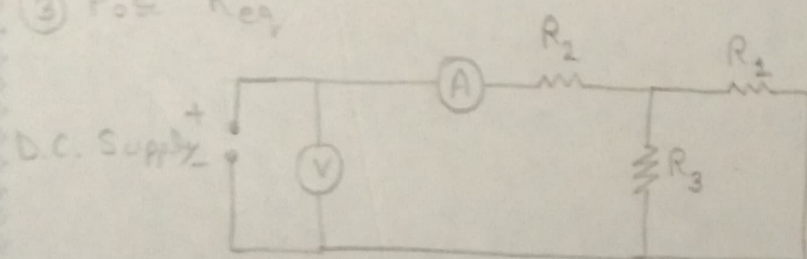
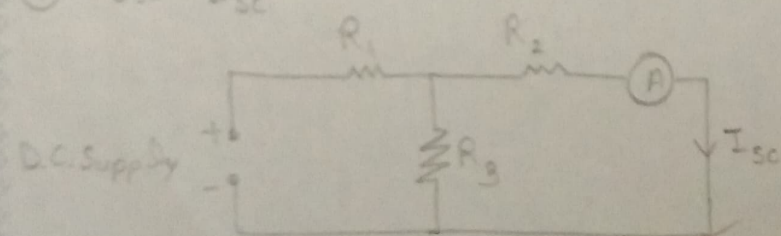


Circuit Diagram :-① For I_{LA} ② For V_{oc} ③ For R_{eq} ④ For I_{sc} 

TUTORIAL / PRACTICAL NO.

Object :- To verify the Thevenin's and Norton's Theorem.

Apparatus :-

- | | | |
|-----------------------|----------------|-------|
| • D.C. Voltmeter | 0 - 10/20 Volt | 1 No. |
| • D.C. Ammeter | 0 - 1/2 A | 1 No. |
| • Load Resistance | 15 Ω | 1 No. |
| • Power Supply (D.C.) | 0 - 17.5 volt | 1 No. |
| • Network kit | | |
| • Connecting Leads | | |

Theory :-

Thevenin's Theorem :-

For any linear bilateral network irrespective of its complexities can be reduced into a Thevenin's equivalent circuit having the Thevenin's open circuit voltage ' V_{Th} ' in series with the Thevenin's equivalent resistance R_{Th} along with load resistance R_L .


Norton's Theorem :-

Any linear bilateral network irrespective of its complexities can be reduced into a Norton's equivalent circuit having a

Observation Table :-

S.No	$I_{LA}(mA)$	$R_L(\Omega)$	$V_{oc}(V)$	$I_{sc}(mA)$	$V(V)$	I
1	3.1 mA	0.047	0.33	5.7 mA	7.43	33.1
2	3.9 mA	0.047	0.40	6.9 mA	9.13	40.9

R_1	0.216 k Ω
R_2	0.047 k Ω
R_3	0.011 k Ω

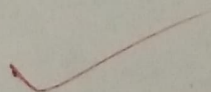

TUTORIAL / PRACTICAL NO.

Norton's short circuit current I_N in parallel with Norton's equivalent resistance R_N in parallel with load resistor R_L .

Formula Used:-

$$I_L = \frac{V_{Th}}{(R_{Th} + R_L)}$$

$$I_L = I_{sc} \cdot \frac{R_{eq}}{R_L + R_{eq}}$$

where,

I_L = Load Current

$V_{Th} = V_{oc}$ = Open Circuit Voltage = Thevenin's Voltage

$R_{Th} = R_{eq}$ = Equivalent Resistance across load terminals

R_L = Load Resistance (19Ω)

I_{sc} = Short Circuit Current

Calculation:-

$$R_{Th} = (R_1 \parallel R_3) + R_2$$

$$= \frac{0.216 \times 0.011}{0.216 + 0.011} + 0.047$$


$$= 0.010 + 0.047$$

$$R_{Th} = 0.057 \text{ k}\Omega$$

$$V_{Th} = ?$$

Using fig. 2,

$$R_T = 0.227 \text{ k}\Omega$$

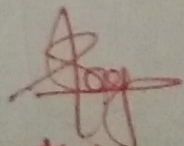
9/3/22

TUTORIAL / PRACTICAL NO.

$$I_T = \frac{V}{R_T} = \frac{7.43}{0.227 \times 10^3}$$

$$I_T = 32.73 \text{ mA (Total Current)}$$

$$V_{Th} = I_T \times R_3$$

$$= 32.73 \times 0.011$$

$$V_{Th} = 0.36 \text{ V}$$

$$I_L = \frac{V_{Th}}{(R_{Th} + R_L)}$$

$$I_L = \frac{0.36}{0.057 + 0.047} = \frac{0.36}{0.104}$$

$$I_L = 3.46 \text{ mA}$$

$$\% \text{ error} = \frac{|3.46 - 3.1|}{3.1} \times 100 = 11.61 \%$$

Calculation of Norton's Theorem,

$$I_L = I_{sc} \times \frac{R_{eq.}}{R_L + R_{eq.}}$$

$$= 5.7 \times \frac{0.057}{0.057 + 0.047}$$

$$= 5.7 \times \frac{0.057}{0.104}$$

$$I_L = 3.12 \text{ mA}$$


$$\% \text{ error} = \frac{|3.12 - 3.1|}{3.1} \times 100 = 0.64 \%$$

TUTORIAL / PRACTICAL NO.

Result :- Here Thevenin's theorem is verified, having a % error of 11.61 % and Norton's theorem is verified, having a % error of 0.64 %.

Precautions :-

- ① All the connection should be tight.
- ② Proper care should be taken while connecting the terminal of ammeter and voltmeter.
- ③ All apparatus should be taken of suitable range and rating.
- ④ Reading should be taken correctly.

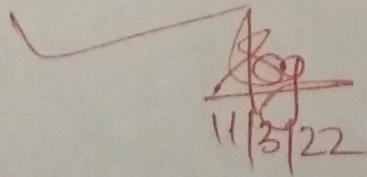
11/3/22