

Unit-2: 3- Phase Systems

Dr. Awadhesh Kumar

Assistant Professor, EED

MMMUT Gorakhpur

3-φ System Advantages :


- 1) 1-φ, pulsating,
- 2) not ss.
- 3) pf ↓
- 4) P
- 5) Rating ↑ phases

3-φ, Rotating
self starting of m/c

pf ↑

$\frac{3+R}{4}$ ↓ Cu

1.5 times more

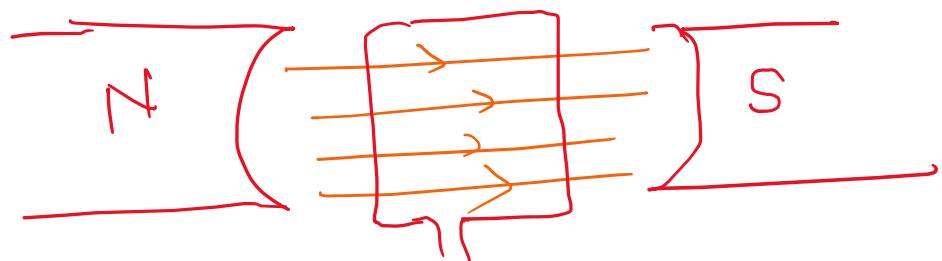


BCR

$\theta \rightarrow w \rightarrow t$

$\{z_0\} \rightarrow +$


$$e = - \frac{d\phi}{dt}$$

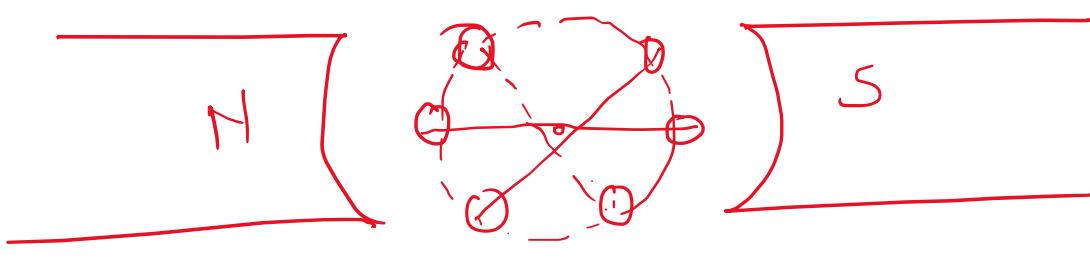

space
120° apart


R
G
Y
C₁
C₂
C₃
max emf

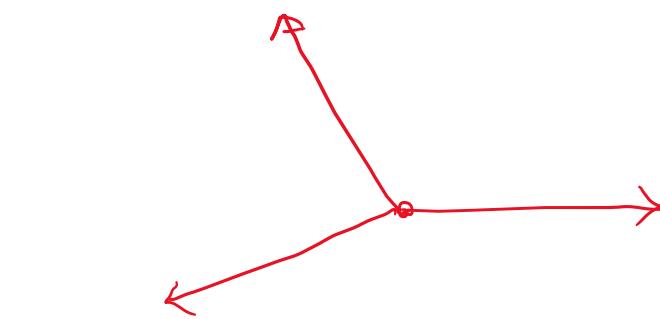Field system B → Stator
Armature C → Rotor






Phase sequence

RYB
BRY
YBR

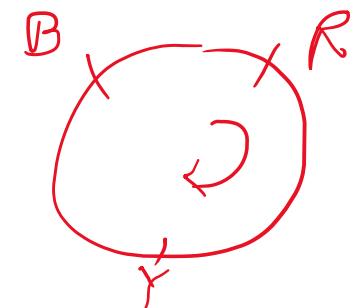

$$\frac{360}{3} = 120^\circ$$

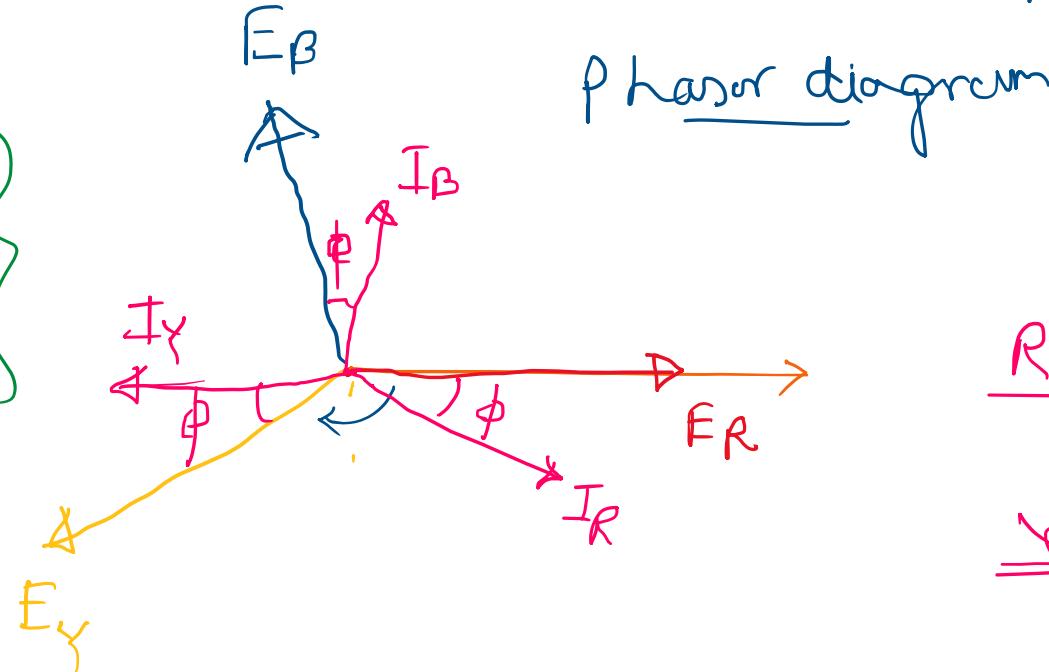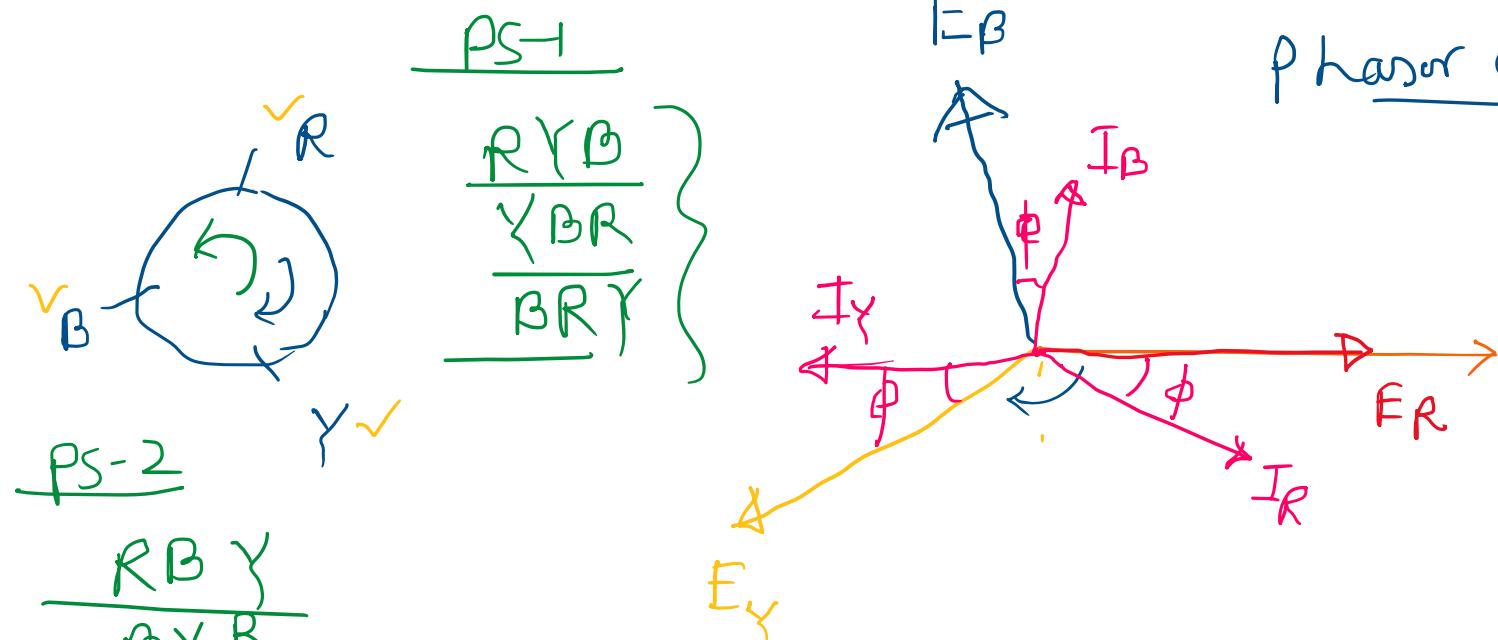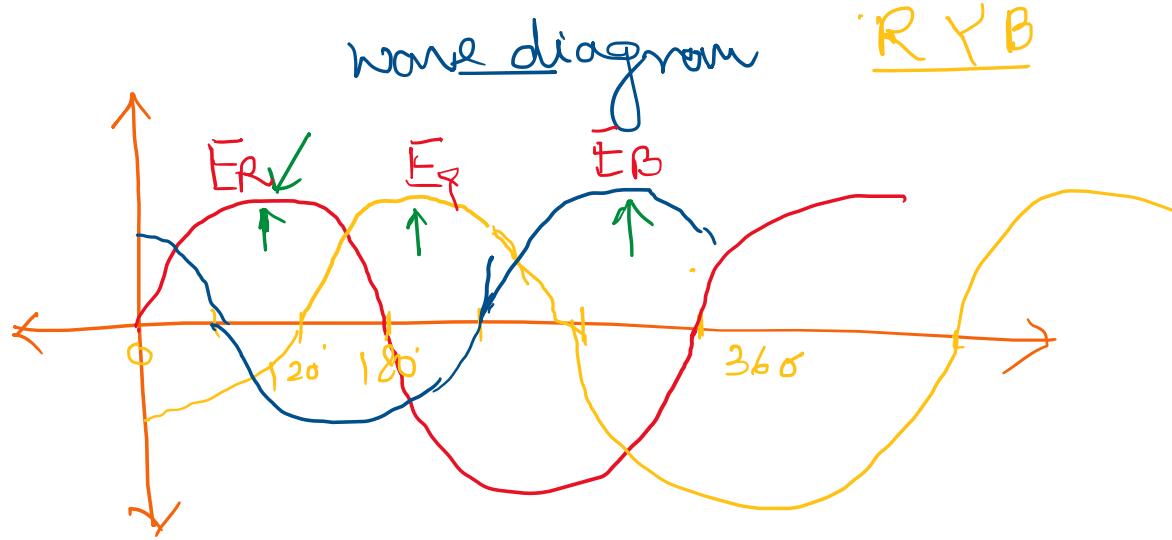

$$E_R = V_m \sin(\omega t) = V_m \angle 0^\circ$$

$$E_Y = V_m \sin(\omega t - 120^\circ) = V_m \angle -120^\circ$$

$$E_B = V_m \sin(\omega t - 240^\circ) = V_m \angle 240^\circ$$

$$V_m \sin(\omega t + 120^\circ) = V_m \angle 120^\circ$$

Balanced Load

3-φ, Logging Load

R phase

$$V_m \angle 0^\circ \quad I_m \angle \phi$$

Y


$$V_m \angle -120^\circ \quad I_m \angle -120 - \phi$$

B


$$V_m \angle 240^\circ \quad I_m \angle -240 - \phi$$

RYB

Phase V₀ Stage

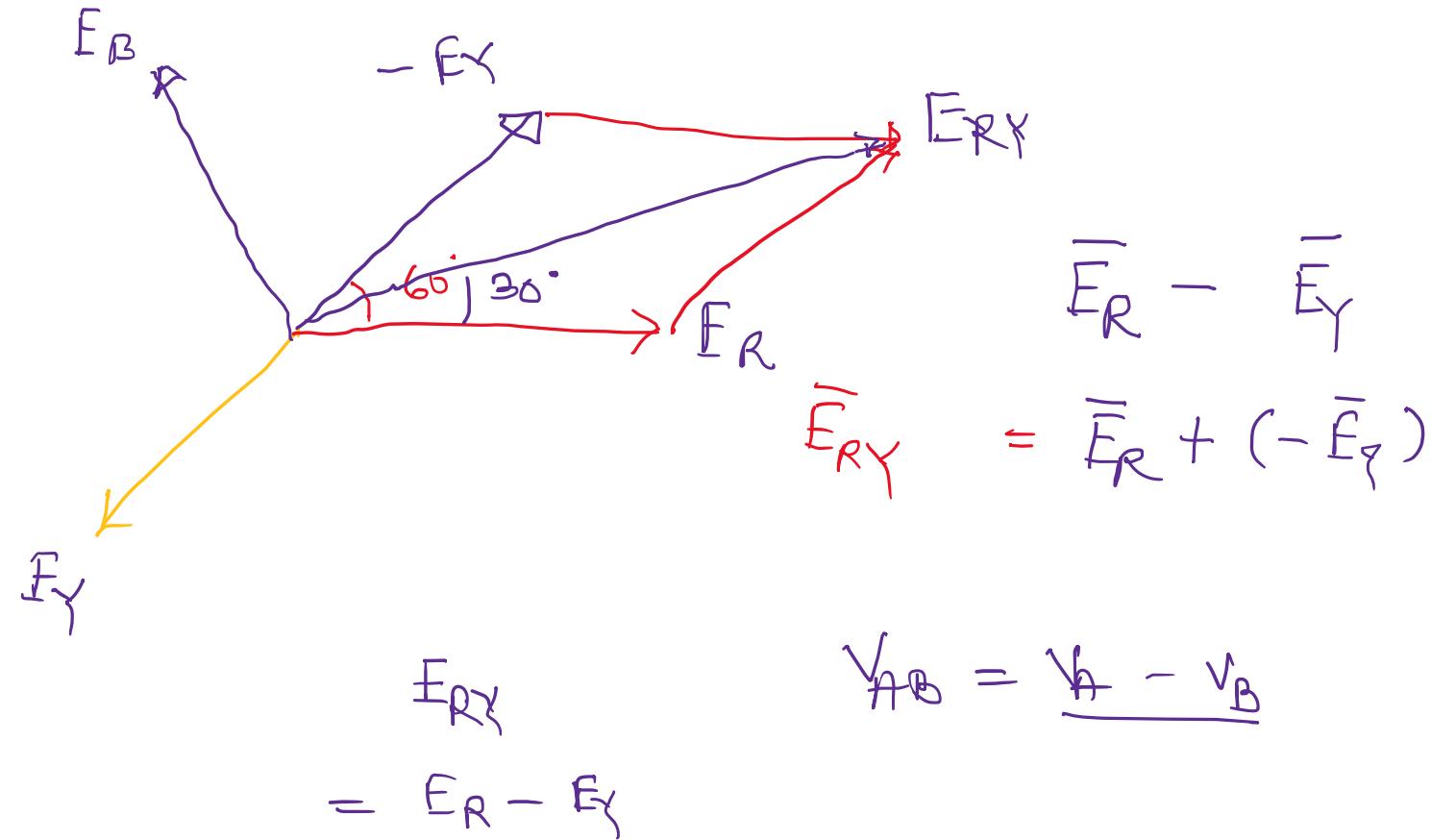

Star Connection

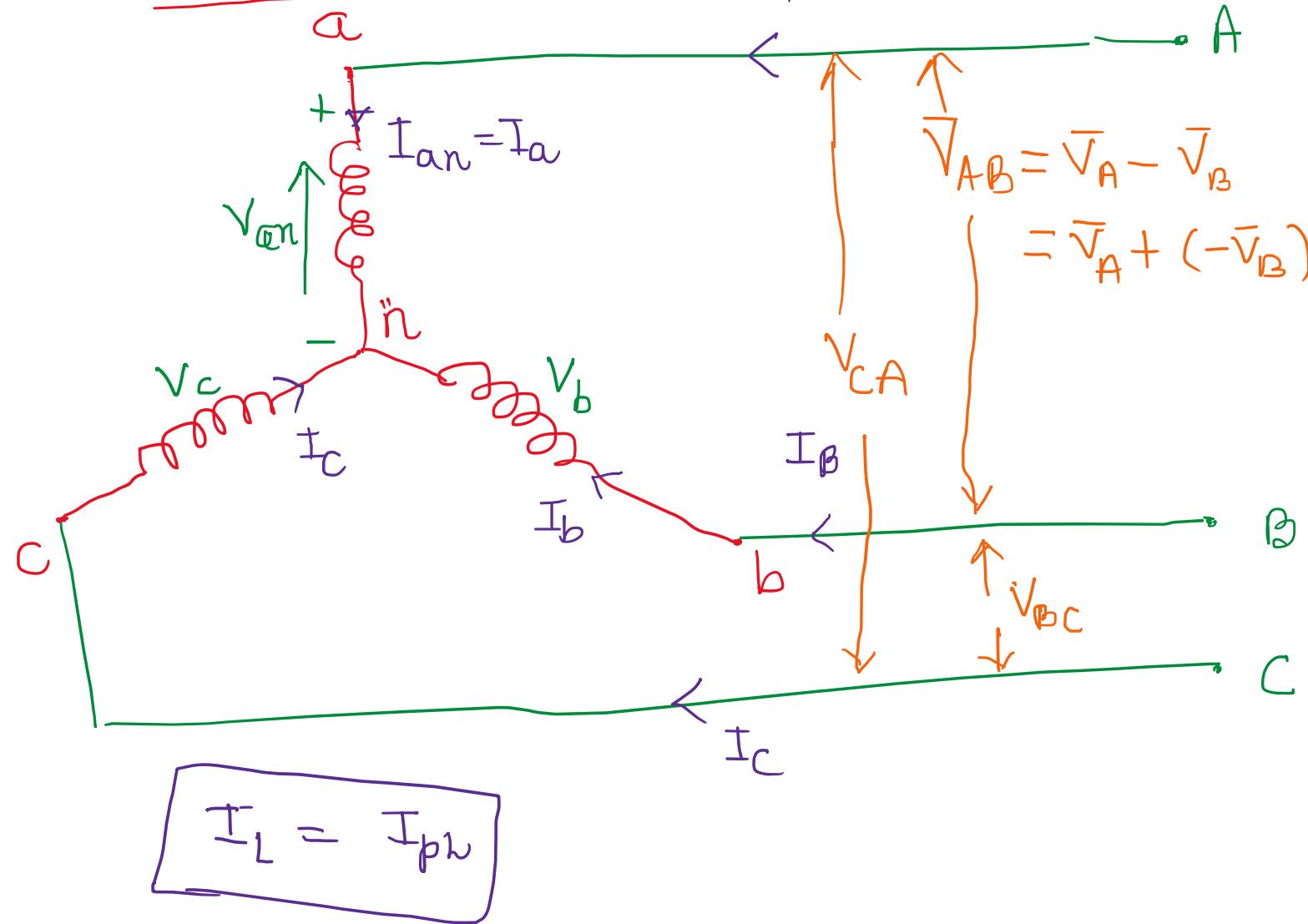


3- ϕ , 3-wire

3- ϕ , 4-wire

Line & phase


$$|V_{An}| = |V_{Bn}| = |V_{Cn}| = V_{ph}$$

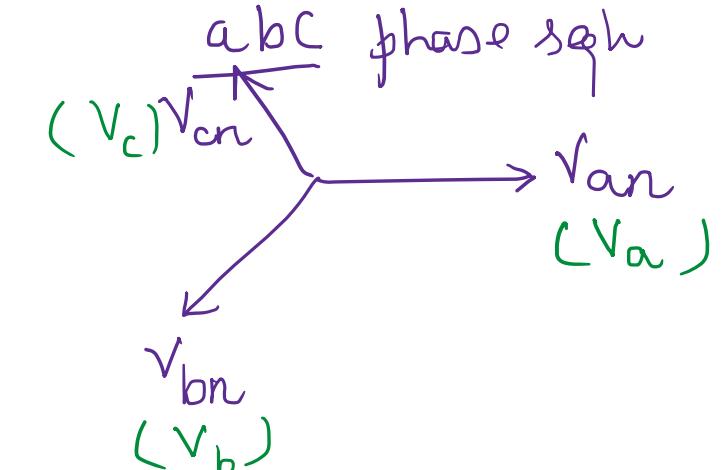


$$|V_{AB}| = |V_{BC}| = |V_{CA}| = V_L$$

$$|\bar{I}_A| = |\bar{I}_B| = |\bar{I}_C| = \bar{I}_L$$

$$|I_a| = |I_b| = |I_c| = I_{ph}$$

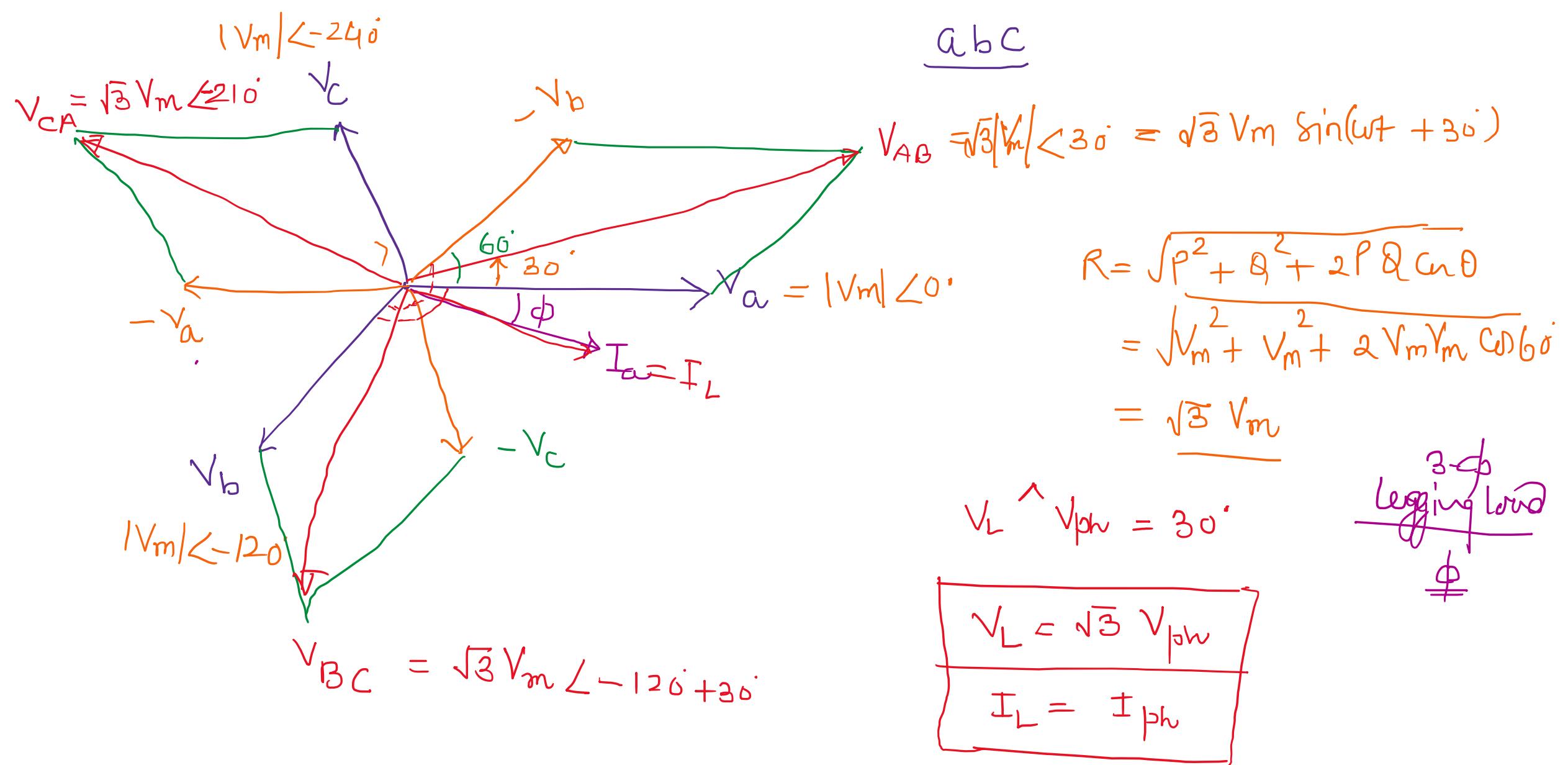

Delta Connection

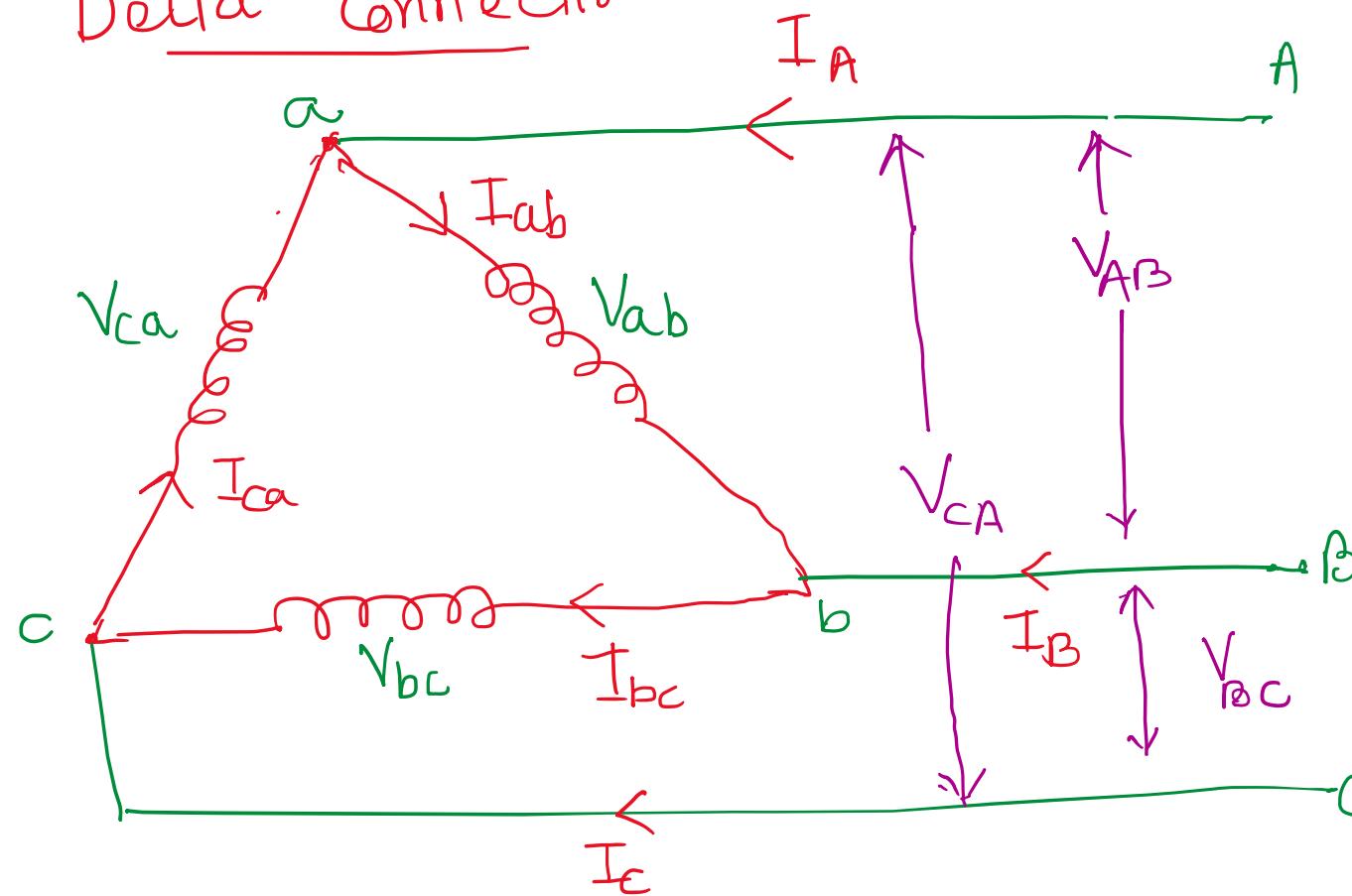

3- ϕ , 3-wire

V_{ab} V_{bc} V_{ca} \rightarrow phase

V_{AB} V_{BC} V_{CA} \rightarrow Line

$$V_{ab} = V_{AB}$$

$$\boxed{V_{ph} = V_L}$$

node a


\sqcap b

\sqcap c

$$\bar{I}_A = \bar{I}_{ab} - \bar{I}_{ca} \quad (1)$$

$$\bar{I}_B = \bar{I}_{bc} - \bar{I}_{ab} \quad (2)$$
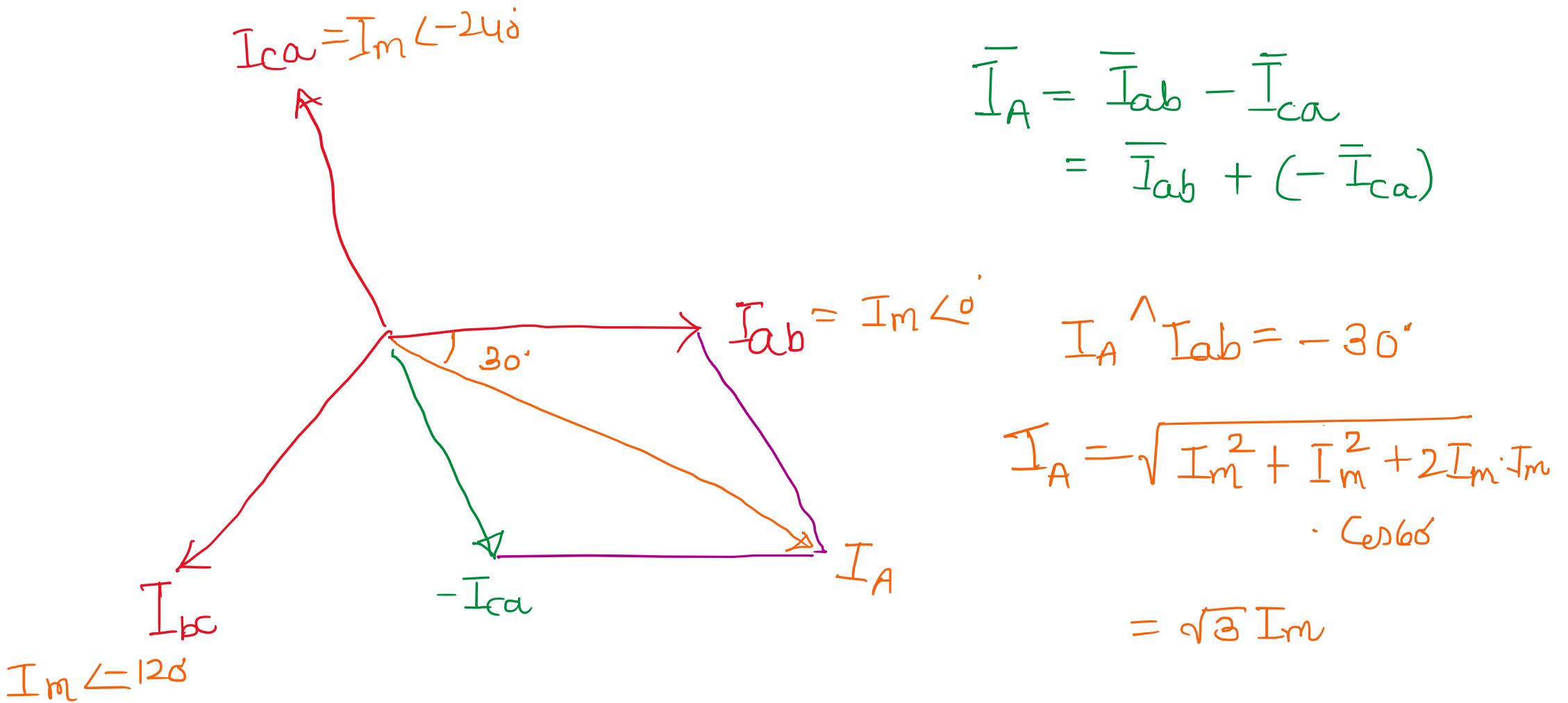
$$\bar{I}_C = \bar{I}_{ca} - \bar{I}_{bc} \quad (3)$$



$\checkmark_L = \sqrt{\rho w}$
$I_L = \sqrt{3} I_{pw}$


3-Φ Power :-

abc

$$V_a = V_p' \sin \omega t$$

$$V_b = V_p' \sin (\omega t - 120^\circ)$$
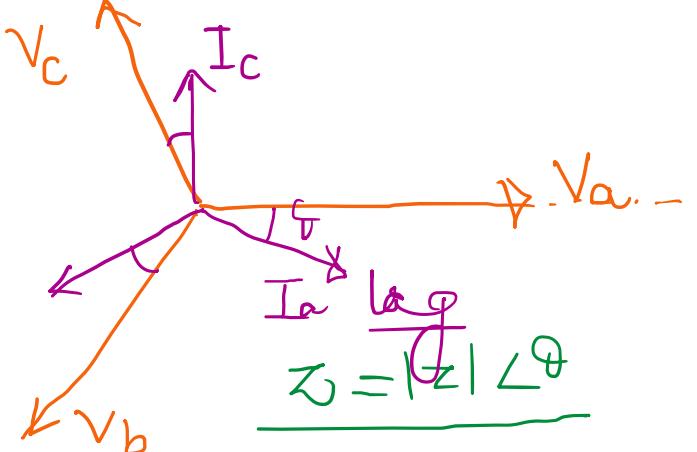
$$V_c = V_p' \sin (\omega t - 240^\circ)$$



$$|V_a| = |V_b| = |V_c| = V_p' \max V$$

$$|I_a| = |I_b| = |I_c| = I_p' \max \text{value}$$

$$I_a = I_p' \sin(\omega t - \theta)$$

$$I_b = I_p' \sin(\omega t - 120^\circ - \theta)$$

$$I_c = I_p' \sin(\omega t - 240^\circ - \theta)$$

$$\phi(t) = V_a I_a + V_b I_b + V_c I_c$$

$$= V_p' I_p' \sin \omega t \sin(\omega t - \theta) + V_p' I_p' \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \theta) + V_p' I_p' \sin(\omega t - 240^\circ) \sin(\omega t - 240^\circ - \theta)$$

$$= \frac{V_p' I_p'}{2} \left[2 \sin \omega t \sin(\omega t - \theta) + \frac{\dots}{\cos \theta - \cos(2\omega t - \theta)} + \frac{\dots}{\cos \theta - \dots} + \frac{\dots}{\cos \theta - \dots} \right]$$

$$\left[\cos \theta - \cos(2\omega t - \theta) + \cos \theta - \dots + \cos \theta - \dots \right]$$

$$= \frac{\sqrt{3} V_p I_p}{\sqrt{2} \sqrt{2}} \cdot 3 \cos \theta$$

$$= \sqrt{3} V_p I_p \cos \theta$$

$$\sqrt{P}(t) = 3 \sqrt{3} V_p I_p \cos \theta$$

$$\left\{ \begin{array}{l} P = 3 \sqrt{3} V_p I_p \cos \theta \quad \text{kW} \\ Q = 3 \sqrt{3} V_p I_p \sin \theta \quad \text{kVAR} \\ S = 3 \sqrt{3} V_p I_p \quad \text{kVA} \end{array} \right.$$

Y

$$P = 3 \frac{V_L}{\sqrt{3}} \cdot I_L \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

Δ

$$P = 3 V_L \frac{I_L}{\sqrt{2}} \cdot \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$\theta = \sqrt{3} V_L I_L \sin \theta$$

$$S = \sqrt{3} V_L I_L$$

$$1 - \phi$$

$$P(t) = \sqrt{3} V I \cos \theta - \sqrt{3} V I \sin \theta (\omega t - \theta)$$

$$P = \sqrt{3} V I \cos \theta$$

active

$$Q = \sqrt{3} V I \sin \theta \quad \text{reactive}$$

$$S = \sqrt{3} V I \quad \text{apparent}$$

Y

$$\left\{ \begin{array}{l} V_L = \sqrt{3} V_p \\ I_L = I_p \end{array} \right.$$

Δ

$$\left\{ \begin{array}{l} V_L = V_{ph} \\ I_L = \sqrt{3} I_p \end{array} \right.$$

$$Z = R + jX$$

$V_p \rightarrow$ } RMS Value
 $I_p \rightarrow$ } of phase
 Voltage &
 current

$$Z = \frac{V_{ph} \angle \theta_1}{I_{ph} \angle \theta_2}$$



$$Z \angle \theta = \frac{V_p}{I_p} \angle \theta_1 - \theta_2$$

$$\underline{\theta = \phi}$$

Measurement of 3-phase Power:

By 2-wattmeter method:

wattmeter measures $P = VI \cos \phi$

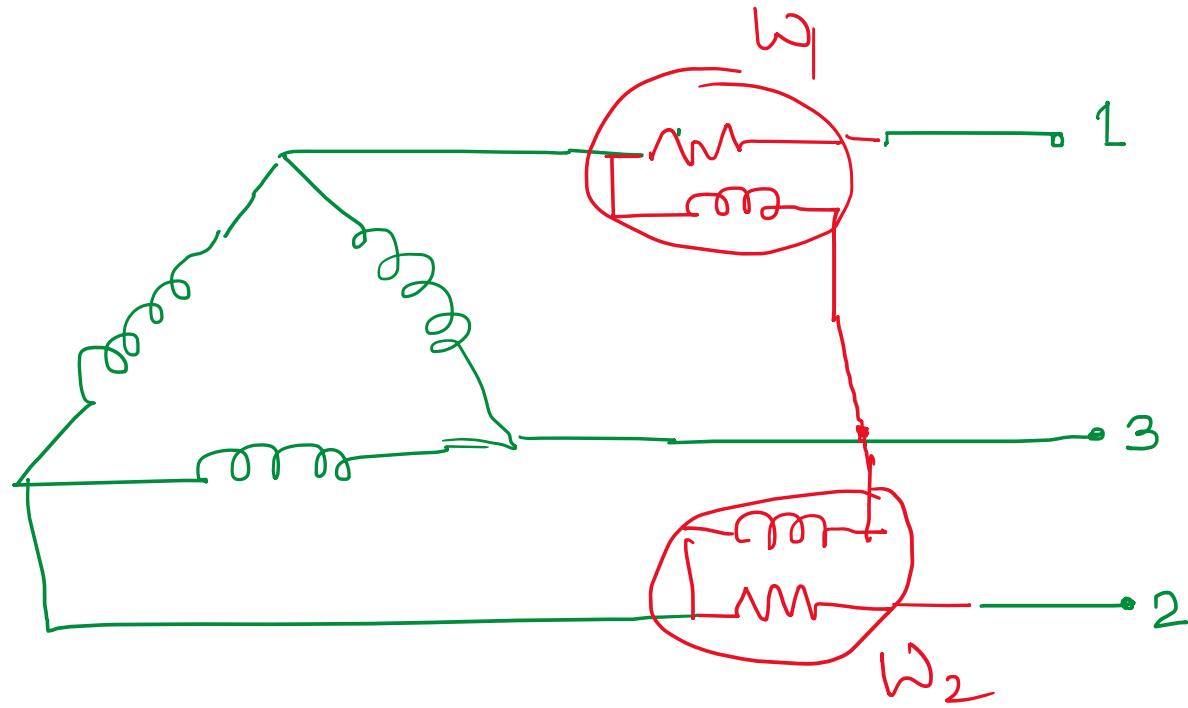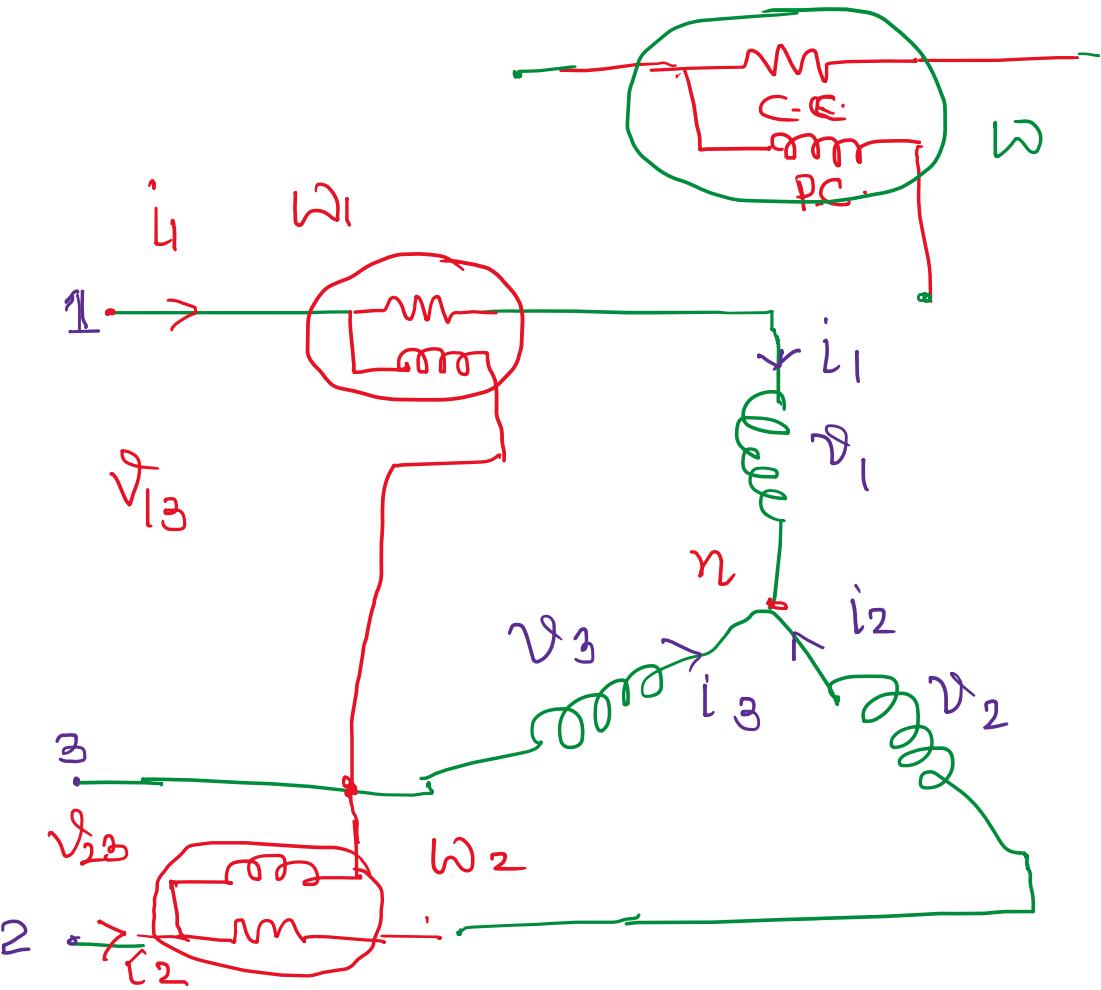

$$\omega_1 = v_{13} i_1$$

$$\omega_2 = v_{23} i_2$$

$$\omega_1 + \omega_2 = v_{13} i_1 + v_{23} i_2$$

$$= (v_1 - v_3) i_1 + (v_2 - v_3) i_2$$

$$= v_1 i_1 + v_2 i_2 - v_3 (i_1 + i_2)$$

$$= v_1 i_1 + v_2 i_2 + v_3 i_3$$

$$v_{13} = (v_1 - v_3)$$

$$v_{23} = (v_2 - v_3)$$


$$i_1 + i_2 + i_3 = 0$$

↓

$$i_1 + i_2 = -i_3$$

Sum of two ^{waveform} wattmeter readings = 3-φ tot^ω Power

$$W_1 + W_2 = P_1 + P_2 + P_3$$

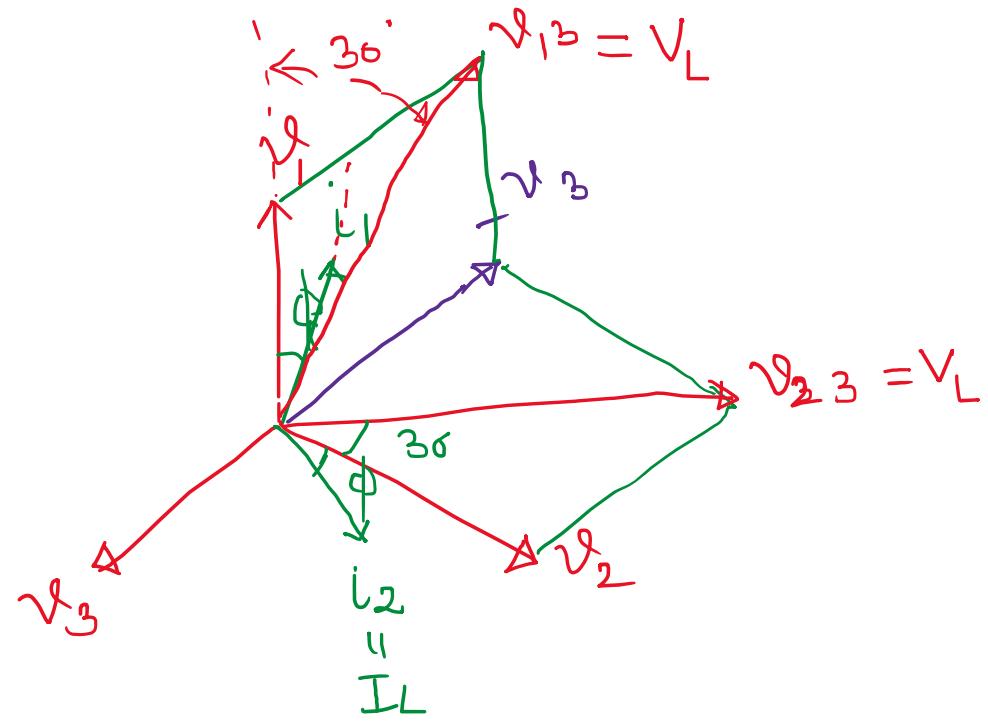

Lagging load
 $v_1 \wedge i_1 = \phi$

$$\begin{aligned}\omega_1 &= v_{13} i_1 \\ \omega_1 &= V_L I_L \cos(30 - \phi)\end{aligned}$$

$$\begin{aligned}\omega_{13} &= \bar{v}_1 - \bar{v}_3 \\ &= \bar{v}_1 + (-\bar{v}_3)\end{aligned}$$

$$v_{13} \wedge i_1 = 30 - \phi$$

$$i_1 = I_L$$

$$\omega_1 + \omega_2 = V_L I_L [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= V_L I_L 2 \cos 30 \cos \phi$$

$$\boxed{\omega_1 + \omega_2 = \sqrt{3} V_L I_L \cos \phi} \quad — (1)$$

$$\omega_2 = v_{23} i_2$$

$$\omega_2 = V_L I_L \cos(30 + \phi)$$

$$\omega_1 - \omega_2 = V_L I_L [\cos(30 - \phi) - \cos(30 + \phi)]$$

$$\boxed{\omega_1 - \omega_2 = V_L I_L 2 \sin 30 \sin \phi = V_L I_L \sin \phi} \quad — (2)$$

$$\omega_1 + \omega_2 = \sqrt{3} V_L I_L \cos\phi \quad \text{--- (1)}$$

$$\omega_1 - \omega_2 = V_L I_L \sin\phi \quad \text{--- (2)}$$

$$\frac{\tan \phi}{\sqrt{3}} = \frac{\omega_1 - \omega_2}{\omega_1 + \omega_2}$$

$$\tan\phi = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$\phi = \tan^{-1} \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$pf = \cos\phi = \cos \tan^{-1} \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

①

$$\underline{\omega_1 = \omega_2} \quad pf$$

②


$$\omega_2 = 0 \quad \omega_1 = \text{finite}$$

$$\phi < 60^\circ$$

$$\cos\phi = \frac{1}{2} \quad wf$$

Prob:  , 3- ϕ , 50Hz , $\underbrace{415V}_{V_L}$ supply , $\underbrace{20 \angle -30^\circ A}_{I_{ph}}$ Logging

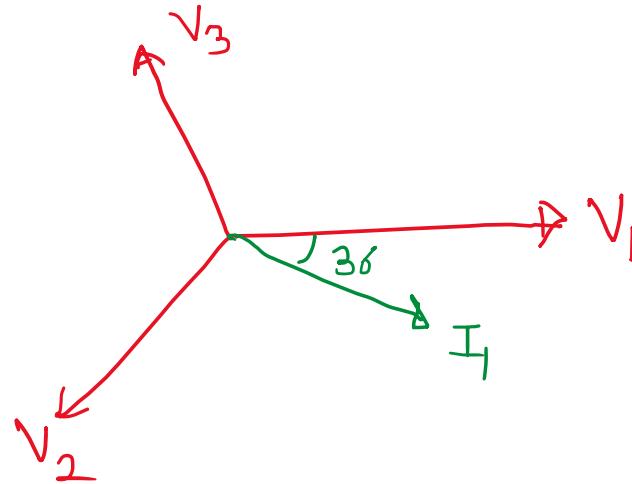- (i) Total Power supplied: (ii) Phasor Diagram
 (iii) the overall pf



$$V_L = 415V$$

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 239.6V \quad (V_L = \sqrt{3} V_p)$$

$$I_L = I_p = 20A$$

$$\phi = V_1^\wedge I_1 = -30^\circ$$

$$(i) P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 415 \times 20 \cos 30^\circ$$

$$(ii) \omega \phi = \omega 30^\circ = 0.866 \text{ Logging}$$

$\sqrt{2-3}$

Prob 1 $\text{bal } \Delta$

$$Z = |2+j9| \Omega / \text{phase} \quad 3\phi, \quad 400V = V_L$$

$$= R + jX_L$$


1) I_L

2) P_f

3) Power drawn, $P = \sqrt{3} V_L I_L \cos\phi$

4) Reactive volt amp $Q = \sqrt{3} V_L I_L \sin\phi$

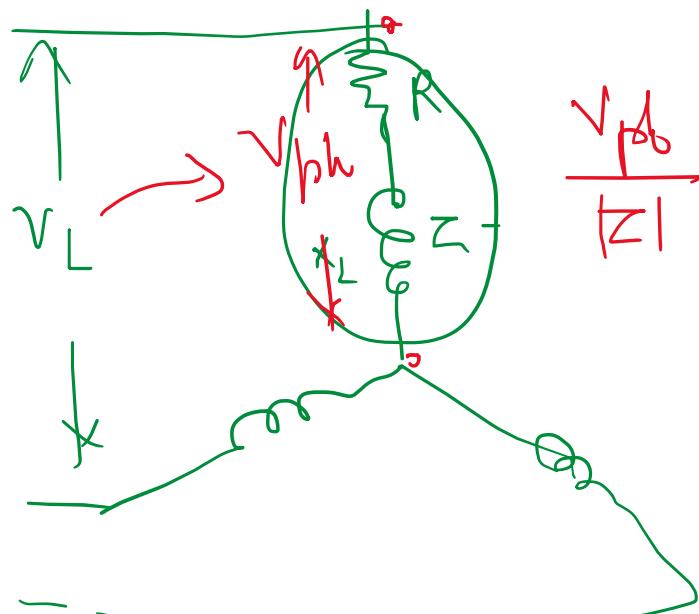5) Total Volt Amp, $S = \sqrt{3} V_L I_L$



$$\frac{V_{ph}}{|Z|} \quad \frac{V_{ph} \angle \theta}{Z \angle \phi}$$

$$= \frac{\sqrt{3} V_L \angle \theta}{jX} \quad = \frac{\sqrt{3} V_L \angle \theta}{X} \angle -90^\circ$$

$$= (V_p/X) \angle \theta - 90^\circ$$

$$|Z| = \sqrt{R^2 + X_L^2} = 15 \Omega$$

$$I_{ph} = \frac{V_{ph}}{|Z|}$$

$$V_{ph} = V_L$$

$$I_L = \sqrt{3} I_{ph}$$

Z

$$Z = R \quad R \angle 0^\circ$$

$$= R + jX \quad |Z| \angle \phi$$

$$= R - jX \quad |Z| \angle -\phi$$

$$= jX \quad X \angle 90^\circ$$

$$= -jX \quad X \angle -90^\circ$$