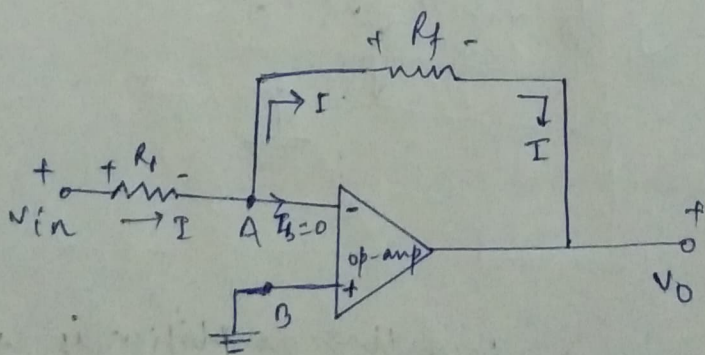


Ans:- • The output is inverted with respect to input, which is indicated by minus sign, for inverting amplifier.

• The voltage gain depends on the ~~ratio~~ ratio of the two resistances. Hence, selecting R_f and R_i , the required value of gain can be easily obtained.


• If the ratio of R_f and R_i is K , which is other than one, the circuit is called scale changer.

• Inverting amplifier functions as scale changer through small signals with constant gain



Ques 10. Draw the circuit diagram of the op-amp integrator and derive the expression for its output voltages and list all the applications of it.

Ans :-

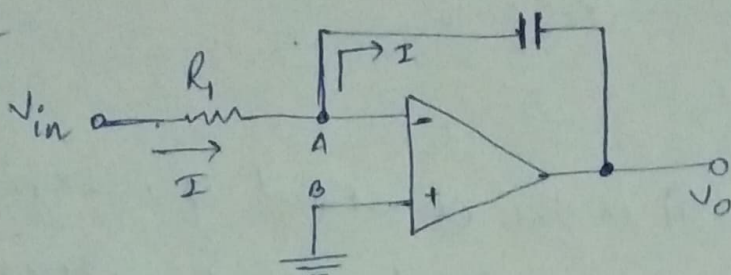

Op-amp integrator.

From the input side we can write,

$$I = \frac{V_{in} - V_A}{R_1} = \frac{V_{in}}{R_1}$$

From output side, we can write,

$$I = C_f \frac{d(V_A - V_o)}{dt}$$

i.e. $I = -C_f \frac{dV_o}{dt}$

Equating the two equations (1) and (2)

$$\frac{V_{in}}{R_1} = -C_f \frac{dV_o}{dt}$$

Integrating both sides,

$$\int_0^t \frac{V_{in}}{R_1} dt = -C_f \int \frac{dV_o}{dt} \cdot dt$$

i.e. $\int_0^t \frac{V_{in}}{R_1} dt = -C_f V_o$

$$\therefore V_o = -\frac{1}{R_1 C_f} \int_0^t V_{in} dt + V_o(0)$$

where $V_o(0)$ is the constant of integration, indicating the initial output voltage.

The applications of op-amp integrator are as follows:-

- 1) Calculus operations in analog computers.
- 2) ramp generators
- 3) wave shaping circuits,
- 4) A/D converters.
- 5) In solving the differential equations.



Ques 11: Draw the output waveforms of op-amp differentiator if its input waveform is

- (a) Step signal
- (b) Square wave
- (c) Sine signal.

Ans: (a)


step signal

(input)

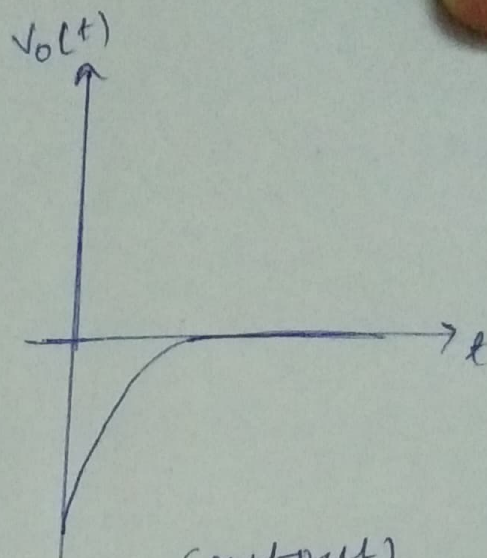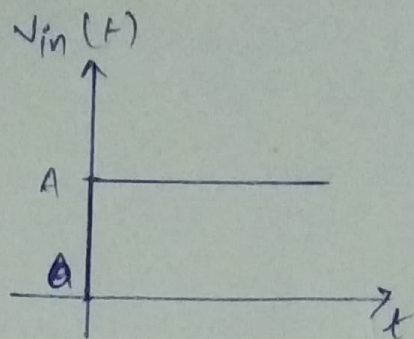


(output)

Square wave

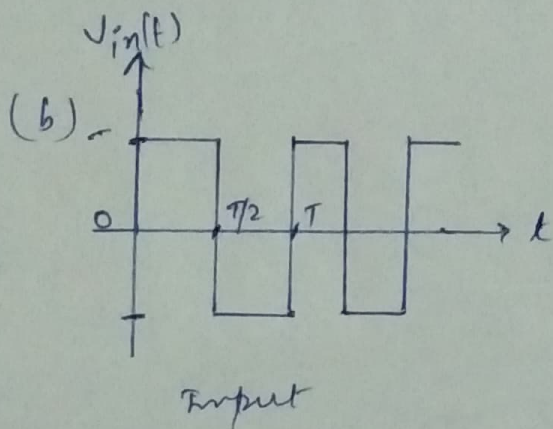


Input

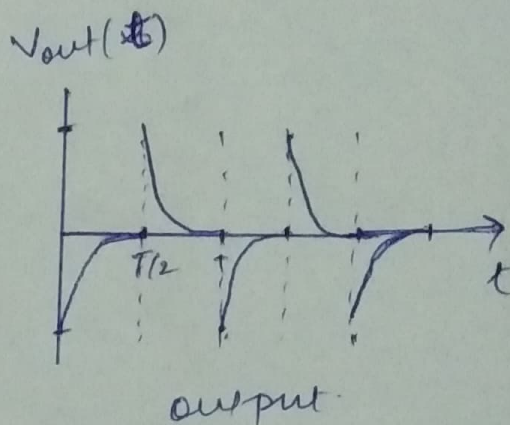


output

(c) Sine signal

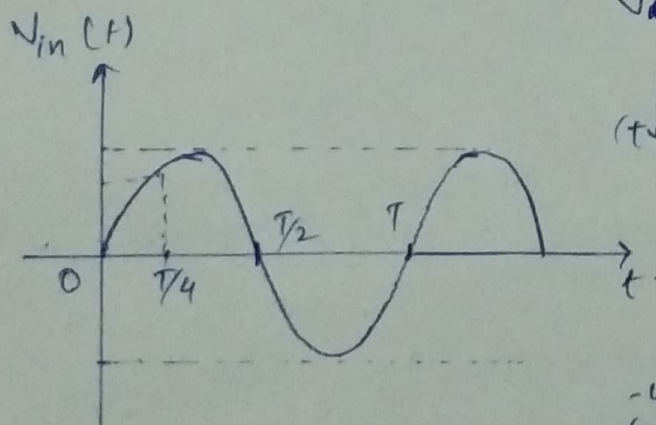

Input

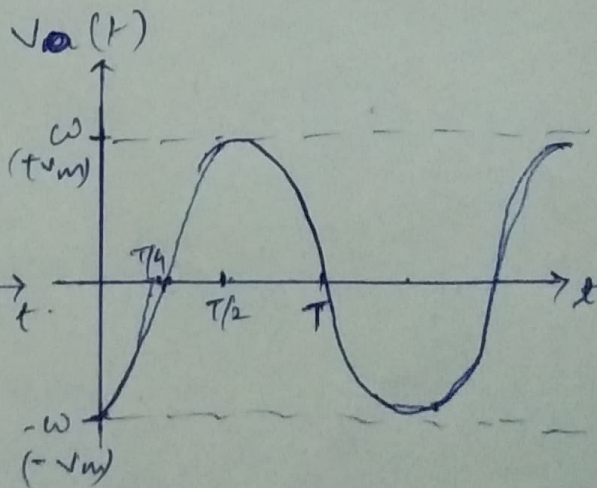

output