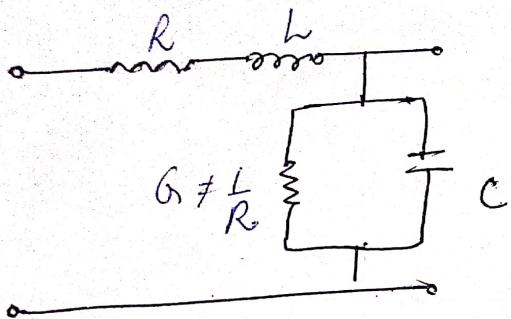


- Transmission Lines - Equations of Voltage and Current on TX Line
  - Propagation Constant and Characteristic Impedance
  - Reflection Coefficient and VSWR


Equivalent diagram:



Binary Constant:

$$\begin{aligned} R & (\Omega/m) \\ L & (\text{H/m}) \\ G & (\text{S/m}) \\ C & (\text{F/m}) \end{aligned}$$

Equation of Transmission line:

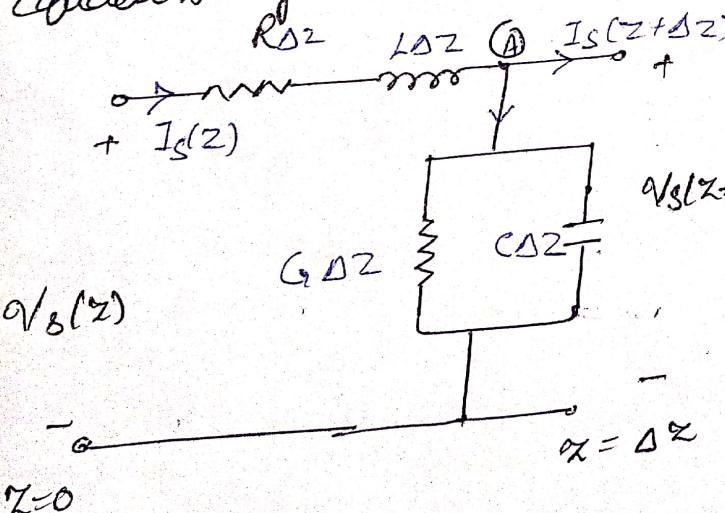

Applying KVH:

$$\begin{aligned} \Rightarrow v_s(z) - I_s(z) R \Delta Z - j \omega L \Delta Z I_s(z) \\ - v_s(z + \Delta Z) = 0 \\ \Rightarrow v_s(z) - v_s(z + \Delta Z) = I_s(z) \Delta Z (R + j \omega L) \\ \Rightarrow \frac{v_s(z) - v_s(z + \Delta Z)}{\Delta Z} = I_s(z) (R + j \omega L) \end{aligned}$$

Taking Lim as  $\Delta Z$  is very small

$$\lim_{\Delta Z \rightarrow 0} \frac{v_s(z) - v_s(z + \Delta Z)}{\Delta Z} = \lim_{\Delta Z \rightarrow 0} I_s(z) (R + j \omega L)$$

$$\Rightarrow \frac{dv_s(z)}{dz} = I_s(z) (R + j \omega L) \quad (1)$$

$$\Rightarrow \frac{d^2 V_S}{dz^2} = \frac{d I_S(z)}{dz} (R + j\omega L) - \textcircled{2}$$

Applying nodal at A

$$\rightarrow -I_S(z) + I_S(z + \Delta z) + V_S(z + \Delta z)(G + j\omega C) \Delta z = 0$$

$$\rightarrow I_S(z) - I_S(z + \Delta z) = V_S(z + \Delta z)(G + j\omega C) \Delta z$$

$$\Rightarrow \frac{I_S(z) - I_S(z + \Delta z)}{\Delta z} = V_S(z + \Delta z)(G + j\omega C)$$

$$\Rightarrow \lim_{\Delta z \rightarrow 0} \frac{I_S(z) - I_S(z + \Delta z)}{\Delta z} = \lim_{\Delta z \rightarrow 0} V_S(z + \Delta z)(G + j\omega C)$$

$$\Rightarrow \frac{d I_S(z)}{dz} = V_S(z)(G + j\omega C) \quad \text{---} \textcircled{3}$$

$$\Rightarrow \frac{d^2 I_S(z)}{dz^2} = \frac{d V_S(z)}{dz} (G + j\omega C) \quad \text{---} \textcircled{4}$$

$$\frac{d^2 V_S(z)}{dz^2} = V_S(z)(G + j\omega C)(R + j\omega L)$$

$$\boxed{\frac{d^2 V_S(z)}{dz^2} - \gamma^2 V_S(z) = 0} \quad \begin{matrix} \text{Voltage} \\ \text{Equation} \end{matrix}$$

(using eq \textcircled{2} and \textcircled{3})

$$\frac{d^2 I_S(z)}{dz^2} = I_S(z)(R + j\omega L)(G + j\omega C)$$

$$\boxed{\frac{d^2 I_S(z)}{dz^2} - \gamma^2 I_S(z) = 0} \quad \begin{matrix} \text{Current} \\ \text{Equation} \end{matrix}$$

(using \textcircled{4} and \textcircled{1}).

Solutions :  $\boxed{V_S(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}}$

$$I_S(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$$\Downarrow \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$\gamma \rightarrow$  Propagation Constant

$$\rightarrow \text{The wavelength } \lambda = \frac{2\pi}{\beta}$$

$$\rightarrow \text{Wave Velocity } u = \frac{\omega}{\beta} = f\lambda$$

18  
30  
24

$$\frac{12+1-1}{30}$$

$$\frac{14}{32} \times 93.75\%$$

$$\frac{18}{12}$$



## → Characteristic Impedance - ( $Z_0$ )

It is defined as ratio of forward travelling voltage wave and forward travelling current wave at any point of transmission line.

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \frac{V_0^+}{I_0^+} = \frac{V_0^-}{I_0^-}$$

$$Z_0 = R_0 + jX_0$$

$$\therefore -Y V_0^+ = -(R + j\omega L) I_0^+$$

$$-Y V_0^- = -(R + j\omega L) I_0^-$$

$$\Rightarrow Z_0 = \frac{V_0^+}{I_0^+} = \frac{V_0^-}{I_0^-} = \frac{R + j\omega L}{Y} = \frac{Y}{G + j\omega C}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

## → Lossless Transmission Line:

$$R = G = 0$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\Rightarrow \alpha + j\beta = \sqrt{j\omega L \times j\omega C}$$

$$\Rightarrow \alpha + j\beta = j\omega \sqrt{LC}$$

$$\Rightarrow \alpha = 0 \text{ and } \beta = \omega \sqrt{LC}$$

- A transmission line is said to be lossless if the conductors of the line are perfect ( $\sigma \approx \infty$ ) and the dielectric medium separating them is lossless ( $\sigma \approx 0$ ).

$$\Rightarrow \eta_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{0 + j\omega L}{0 + j\omega C}} = \sqrt{\frac{\omega L}{\omega C}}$$

$$\Rightarrow Z_0 = \sqrt{\frac{L}{C}}$$

$$\eta_p = \frac{1/C}{\sqrt{1/L}} = \frac{1/C}{\sqrt{1/(LC)}} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{c^2 Z_0}} = \frac{1}{c Z_0}$$

## → Distortionless Transmission Line:

- A distortionless line is one in which the attenuation constant  $\alpha$  is frequency independent while the phase constant  $\beta$  is clearly dependent on frequency.

$$\frac{R}{G} = \frac{L}{C}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)/(G + j\omega C)}$$

$$\Rightarrow \alpha + j\beta = \sqrt{RG(1 + j\omega L/R)(1 + j\omega C/G)}$$

$$\Rightarrow \sqrt{RG} \sqrt{\left(1 + j\frac{\omega L}{R}\right) \left(1 + j\frac{\omega C}{G}\right)} = \sqrt{RG} \left(1 + j\frac{\omega L}{R}\right)$$



$$\Rightarrow \alpha + j\beta = \sqrt{RG} + j\omega \sqrt{\frac{RG}{R^2}}$$

$$\Rightarrow \alpha + j\beta = \sqrt{RG} + j\omega \sqrt{\frac{L}{R}}$$

$$\Rightarrow \alpha + j\beta = \sqrt{RG} + j\omega \sqrt{LC}$$


$$\boxed{\alpha = \sqrt{RG} \text{ and } \beta = \omega \sqrt{LC}}$$

$$\Rightarrow \boxed{\gamma_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}}$$

$$\Rightarrow Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{R(1+j\omega \frac{L}{R})}{G(1+j\omega \frac{C}{G})}} = \sqrt{\frac{R(1+j\omega \frac{L}{R})}{G(1+j\omega \frac{L}{R})}}$$

$$\boxed{Z_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}}}$$

→ Input Impedance of Transmission line.

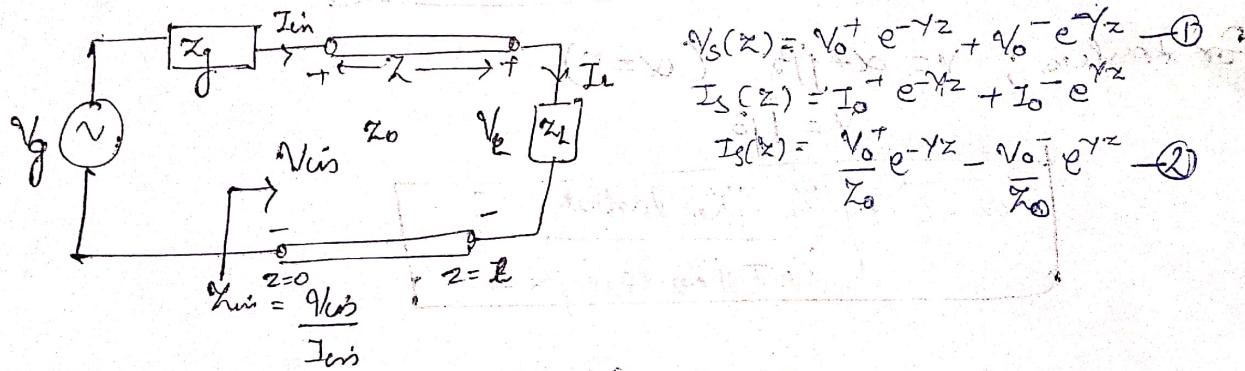

At  $z=0$ ,  $V_s(0) = V_{in} = V_o^+ + V_o^-$  — (3)

$$I_s(0) = I_{in} = \frac{V_o^+}{Z_0} - \frac{V_o^-}{Z_0}$$

$$I_{in} Z_0 = V_o^+ - V_o^-$$
 — (4)

At  $z=l$ ,  $V_s(l) = V_L = V_o^+ e^{-\gamma l} + V_o^- e^{\gamma l}$  — (5)

$$I_s(l) = I_L = \frac{V_o^+}{Z_0} e^{-\gamma l} + \frac{V_o^-}{Z_0} e^{\gamma l}$$
 — (6)

(Add eq(5) and (6))  $\Rightarrow V_L + I_L Z_0 = 2 V_o^+ e^{-\gamma l}$

$$V_o^+ = \left( \frac{V_L + I_L Z_0}{2} \right) e^{\gamma l} = \left( \frac{I_L Z_L + I_L Z_0}{2} \right) e^{\gamma l}$$

(Sub 5 and 6)  $\Rightarrow V_L - I_L Z_0 = 2 V_o^- e^{\gamma l}$

$$V_o^- = \frac{V_L - I_L Z_0}{2} e^{-\gamma l}$$

$$\boxed{\frac{V_o^-}{2} = I_L (Z_L - Z_0) e^{-\gamma l} \quad \text{and} \quad \boxed{V_o^+ = I_L \frac{(Z_L + Z_0)}{2} e^{\gamma l}}}$$

equates  
propage  
Reflex

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_0^+ + V_0^-}{\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}} = Z_0 \left[ \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right]$$

$$\Rightarrow Z_{in} = Z_0 \left[ \frac{\frac{I_{in}}{Z_0} (Z_L + Z_0) e^{Yl} + \frac{I_{in}}{Z_0} (Z_L - Z_0) e^{-Yl}}{\frac{I_{in}}{Z_0} (Z_L + Z_0) e^{Yl} - \frac{I_{in}}{Z_0} (Z_L - Z_0) e^{-Yl}} \right] \\ = Z_0 \left[ \frac{Z_L (e^{Yl} + e^{-Yl}) + Z_0 (e^{Yl} - e^{-Yl})}{Z_L (e^{Yl} - e^{-Yl}) + Z_0 (e^{Yl} + e^{-Yl})} \right].$$

$$\Rightarrow Z_{in} = \frac{V_{in}}{I_{in}}$$

$$\Rightarrow Z_{in} = Z_0 \left[ \frac{Z_L \cosh(Yl) + Z_0 \sinh(Yl)}{Z_0 \sinh(Yl) + Z_L \cosh(Yl)} \right]$$


$$Z_{in} = Z_0 \left[ \frac{Z_L + Z_0 \tanh Yl}{Z_0 + Z_L \tanh Yl} \right]$$

For lossless;  $\gamma = \alpha + j\beta$  ( $\alpha = 0$ )

$$\gamma = j\beta$$

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \cdot \tanh \beta l}{Z_0 + jZ_L \tanh \beta l} \right]$$

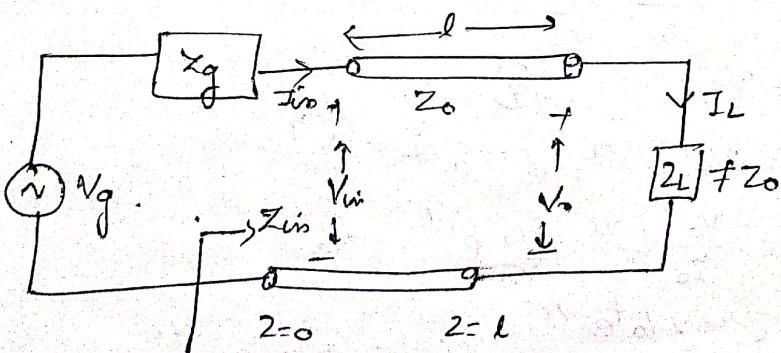$\Rightarrow$  Reflection Coefficient at load:



$$V_S(Z) = V_0^+ e^{-Yl} + V_0^- e^{Yl}$$

$$I_S(Z) = \frac{V_0^+ e^{-Yl}}{Z_0} - \frac{V_0^- e^{Yl}}{Z_0}$$

$$V_S(Z=l) = V_0^+ e^{-Yl} + V_0^- e^{Yl} = V_L \quad (A)$$

$$I_S(Z=l) = I_L Z_0 = V_0^+ e^{-Yl} - V_0^- e^{Yl} \quad (B)$$

Reflection Coefficient = Reflected Intensity

Transmitted Intensity  
Incident Intensity

$$= V_0^- / V_0^+$$

$$\boxed{V = \frac{V_0^-}{V_0^+} e^{2\gamma l}} \Rightarrow \text{Voltage Reflection Coefficient}$$

Adding eq<sup>n</sup> A and eq<sup>r</sup> B

$$V_L + I_L Z_0 = 2V_0^+ e^{-\gamma l}$$

$$V_0^+ = \left( \frac{V_L + I_L Z_0}{2} \right) e^{\gamma l}$$

$$V_0^+ = \left( \frac{I_L Z_L + I_L Z_0}{2} \right) e^{\gamma l}$$

$$\text{Similarly } V_0^- = \left( \frac{I_L Z_L - I_L Z_0}{2} \right) e^{-\gamma l}$$

The Voltage Reflection Coefficient at any point on the line is the ratio of the reflected voltage wave to that of the incident wave.

$$\Gamma_V = \frac{(I_L Z_L - I_L Z_0) e^{-\gamma l/2}}{(I_L Z_L + I_L Z_0) e^{\gamma l/2}} e^{2\gamma l}$$

$$\boxed{\Gamma_V = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

At load

$$\Gamma_I = -\frac{V_o}{Z_0} e^{\gamma l}$$

$$\frac{V_o}{Z_0} e^{-\gamma l}$$

⇒ Current Reflection  
Coefficient

$$\Gamma_I = -\frac{\frac{V_o}{Z_0}}{\frac{V_o}{Z_0} + e^{2\gamma l}} = -\Gamma_V$$

$$\Rightarrow \boxed{\Gamma_I = -\left(\frac{Z_L - Z_0}{Z_L + Z_0}\right)}$$

$$\boxed{\Gamma_I = -\Gamma_V}$$

→ The current reflection coefficient at any point on the line is the negative of the voltage reflection coefficient at the point.



April 2018

अप्रैल

21 | Saturday

23 | Monday

Standing Wave Ratio (SWR)

$$S = \frac{V_{max}}{V_{min}} = \frac{I_{max}}{I_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

SWR is defined as the ratio of the maximum magnitude of the standing wave to minimum magnitude of the standing wave.

22 | Sunday

Voltage Standing Wave Ratio - It is a measure of the impedance matching between the transmission line and antenna.

$$\eta_{SWR} = S_V = \frac{|V_{max}|}{|V_{min}|} = \frac{1 + |\Gamma_V|}{1 - |\Gamma_V|}$$

$$S_V = \frac{1 + |\Gamma_V|}{1 - |\Gamma_V|}$$

March'18						
S	M	T	W	T	F	S
			01	02	03	
04	05	06	07	08	09	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

April'18						
S	M	T	W	T	F	S
01	02	03	04	05	06	07
08	09	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30					

May'18						
S	M	T	W	T	F	S
		01	02	03	04	05
06	07	08	09	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

April 2018

अप्रैल

24 | Tuesday



25 | Wednesday

Current Standing Wave Ratio :

$$ISWR = S_I = \frac{|I_{max}|}{|I_{min}|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$S_I = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$\text{Range of } \Gamma \Rightarrow -1 \leq \Gamma \leq 1$$

$$\text{Range of } S \Rightarrow 1 \leq S \leq \infty$$

Also

$$\Gamma = \frac{S - 1}{S + 1}$$

April 2018

अप्रैल

26 | Thursday गुरु

27 | Friday शुक्र

Q. Airline has  $\lambda_0 = 70\Omega$  and phase constant  $(\beta) = \frac{3\text{ rad}}{\text{m}}$ , and  $f = 100\text{ MHz}$ .  
means air filled b/w conductors.  
Lossless

$$Z_0 = \gamma_0 = \sqrt{\frac{L}{C}}$$

$$\beta = 3 = \omega \sqrt{LC}$$

$$210 = \omega L$$

$$L = \frac{210}{2\pi f} = -\textcircled{1}$$

$$\frac{\lambda_0}{3} = \sqrt{\frac{L}{C}} \times \frac{1}{\omega \sqrt{LC}} = \frac{1}{\omega C}$$

$$C = \frac{3}{70 \times 10^8} -\textcircled{2}$$

Q. A distortionless line has  $Z_0 = 60\Omega$ ,  $\epsilon = 20\text{ mNp/m}$  and  $v = 0.6c$ . Find  $R, C$ . ( $f = 100\text{ MHz}$ )

$$\sqrt{\frac{R}{G}} = Z_0 = \sqrt{\frac{L}{C}} = 60 -\textcircled{1}$$

$$v = \frac{L}{\sqrt{LC}} = 0.6 \times 3 \times 10^8 -\textcircled{3}$$

$$\alpha = \sqrt{RG} = 20 \times 10^{-3} -\textcircled{2}$$

March'18

S	M	T	W	T	F	S
				01	02	03
04	05	06	07	08	09	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

April'18

S	M	T	W	T	F	S
01	02	03	04	05	06	07
08	09	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30					

May'18

S	M	T	W	T	F	S
		01	02	03	04	05
06	07	08	09	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

April 2018

अप्रैल

28 | Saturday शनि

$$\frac{V}{Z_0} = \frac{1}{\sqrt{LC}}$$

$$V_{Z_0} = \sqrt{\frac{L}{C}} \times \frac{1}{\sqrt{LC}} = \frac{1}{C}$$

$$c = \frac{1}{V_{Z_0}} = \frac{1}{60 \times 0.6 \times 3 \times 10^8} =$$

$$\sqrt{RG} \times \sqrt{\frac{R}{G}} = 60 \times 20 \times 10^{-3}$$

$$R = 1200 \times 10^{-3} = 1.2 \Omega/m$$

29 | Sunday रवि

$$\lambda = \frac{V}{f} = \frac{0.6 \times 3 \times 10^8}{100 \times 10^6}$$

$$\lambda = 1.8 \text{ m}$$

June'18						
S	M	T	W	T	F	S
03	04	05	06	07	08	09

July'18						
S	M	T	W	T	F	S
01	02	03	04	05	06	07
08	09	10	11	12	13	14

August'18						
S	M	T	W	T	F	S
05	06	07	08	09	10	11