



Balanced slope detector → combination of 2 simple slope detectors.

Primary tank circuit T_p → tuned @ f_c → frequency detector

Secondary

- T_1 tank circuit → tuned @ $f_c + \Delta f$
- T_2 tank circuit → tuned @ $f_c - \Delta f$

Working:-

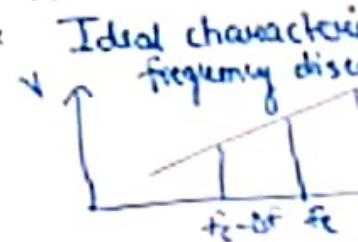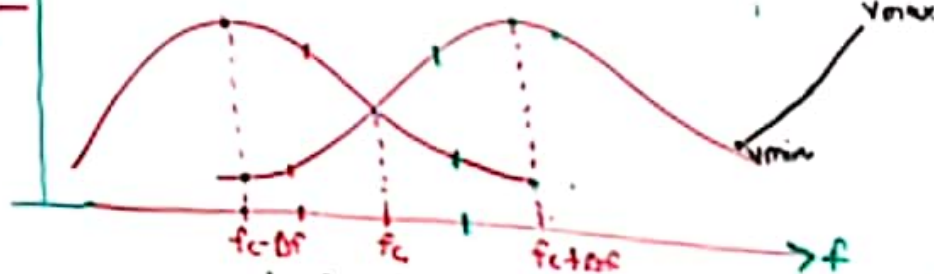

$f = f_c$

Induced V @ T_1 = Induced V @ T_2

$V_{O1} = V_{O2}$

$|V_{R1}| = |V_{R2}|$

$V_o(t) = 0$ gain

$f_c < f < f_c + \Delta f$

Induced V @ R_1 > Induced V @ R_2

$V_{O1} > V_{O2}$

$V_o(t) = V_{R1} - V_{R2} > 0$

@ $f_c + \Delta f = V_{max} = V_o(t)$


$f_c - \Delta f < f < f_c$

Induced V @ R_1 < Induced V @ R_2

$V_{O1} < V_{O2}$

$V_o(t) = V_{R1} - V_{R2}$

@ $f_c - \Delta f = V_{min} = V_o(t)$

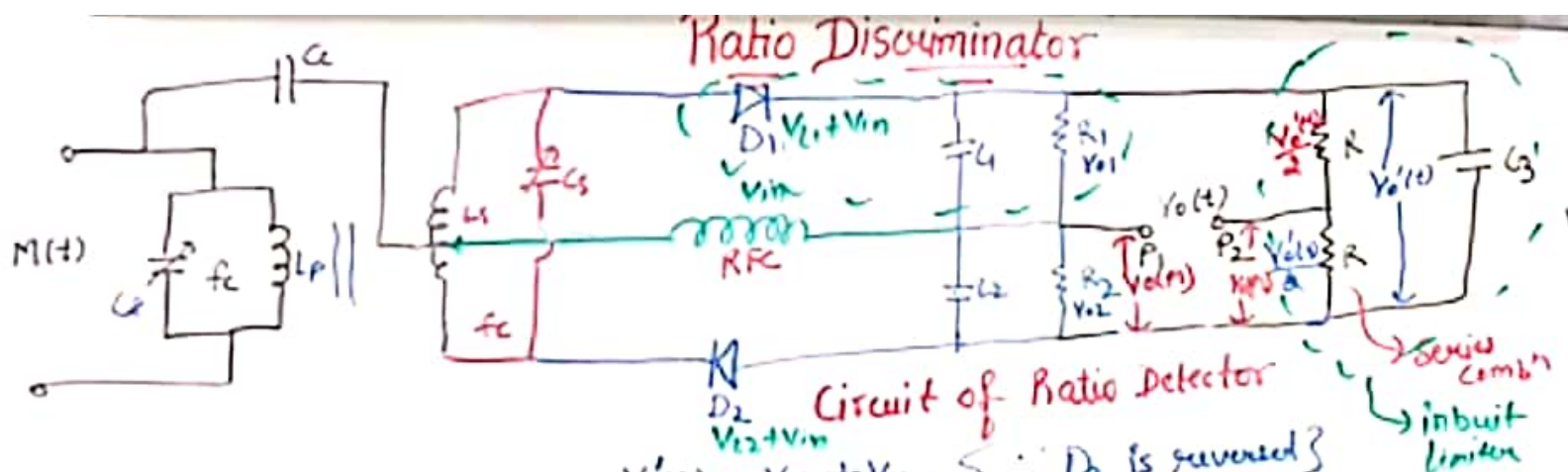

$$V_0'(t) = V_{01} + V_{02} \quad \because D_2 \text{ is reversed}$$

$$V_0(t) = V_0(P_1) - V_0(P_2)$$

$$= V_{02} - \frac{V_0'(t)}{2} = V_{02} - \frac{V_{01} + V_{02}}{2}$$

$$V_0(t) = \frac{V_{02} - V_{01}}{2}$$


$\frac{V_{01}}{V_{02}} \rightarrow$ Ratio changes according to V .
 \therefore Ratio Detector

Advantages:-

- ① Less affected by noise due to inbuilt limiter.
- ② Simple circuit.
- ③ Larger Bandwidth
- ④ High linearity.


Disadvantages:-

- ① Not be implemented over IC

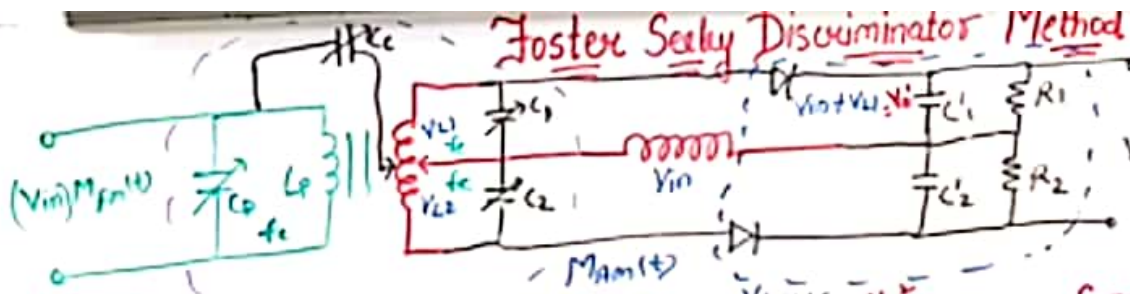

Advantages of coupling capacitor


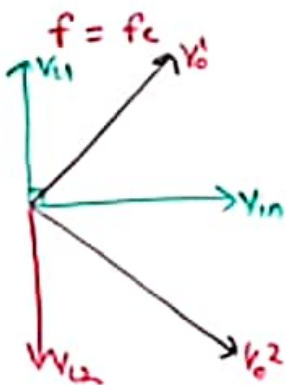
- Block the DC from primary to secondary
- couple primary to center tapped inductor.



$$|V_0'| = |V_0''|$$

$$|V_0'| - |V_0''| = 0$$

when $f = f_c$
 $V_0(t) = 0$

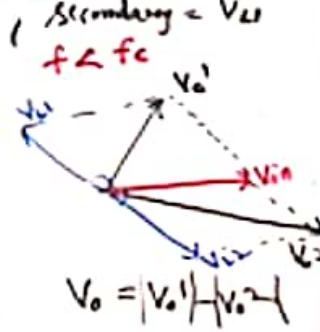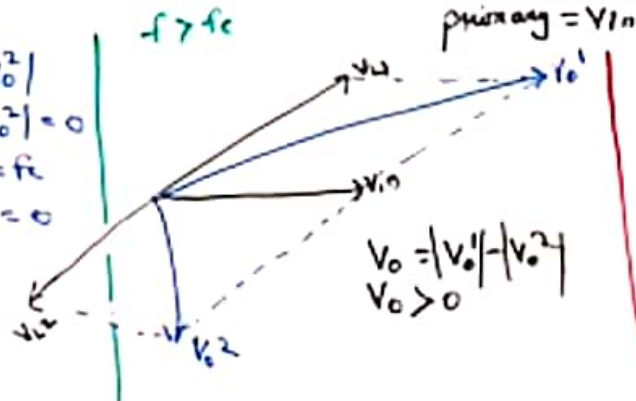

$f = f_c \Rightarrow$ the phase b/w primary & secondary $\neq 90^\circ$

$f > f_c \Rightarrow$ the phase b/w primary & secondary $< 90^\circ$

$f < f_c \Rightarrow$ the phase b/w primary & secondary $> 90^\circ$


primary = V_{in} , secondary = V_{L1}

$$V_0 = |V_0'| - |V_0''|$$

$$V_0 > 0$$

$$V_0 = |V_0'| - |V_0''|$$

Block Diagram of PLL

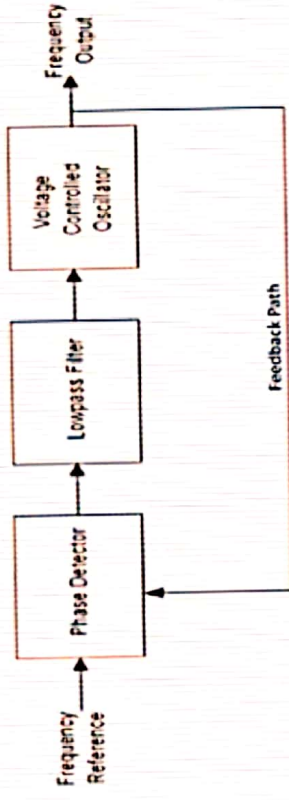

Phase Detector

- A phase detector is basically a comparator that compares the input frequency f_{in} with feedback frequency f_{out} .
- Comparing the input frequency & output frequency it provides a error signal which is basically a Dc voltage.
- The loop is locked when these two signals are of the same frequency and have a fixed phase difference.
- Basically Phase Detector works as an Ex-OR gate.

Voltage Controlled Oscillator (VCO)

- Voltage-controlled oscillator generates frequency controlled by input voltage.
- The dc level output of a low-pass filter is applied as control signal to the voltage-controlled oscillator (VCO).
- The VCO frequency is adjusted till it becomes equal to the frequency of the input signal.
- During this adjustment, PLL goes through three stages-free running, capture and phase lock.

Low Pass Filter

- Low-pass filter is used to remove high frequency components and noise from the output of the phase detector.
- Low Pass Filter provides a steady dc level voltage which becomes the input of VCO.

Stages of PLL Operation

- **Free Running Stage:** When no input is applied at the phase detector, then due to VCO, PLL works in Free Running Stage. The output frequency of this stage is dependent on the free running frequency of VCO.
- **Capture Stage:** When a input frequency is applied at the phase detector, then due to feedback mechanism PLL tries to track the output with respect to input. This stage is called Capture Stage.

Stages of PLL Operation

- **Phase Locked State:** Due to feedback mechanism, the frequency comparison stops as soon as the output frequency become equal to the input frequency. This stage is called Phase Locked State.