

## Lecture 01

Electronics is study of flow of electrons.

There are active and passive elements / devices in the circuit.

Elements that release energy / power are active elements.

e.g.: capacitor.

Elements that consume energy / power are passive elements.

e.g.: Resistor

### Atomic Structure

No. of  $n^o$  = No. of nucleons (Mass no.) - No. of protons (atomic No.)

$e^-$  revolve in orbit/shell no. 'n' =  $2n^2$ .

If valence  $e^-$  i.e.  $VE = 4$ , then it is semiconductor.

$VE < 4$ , then it is conductor

$VE > 4$ , then it is insulator

e.g.: Si(14),  $VE = 4$ , It is semiconductor

$N$ ,  $VE = 5$ , It is insulator.

$Al$ ,  $VE = 3$ , It is conductor.

Categorisation based on valence  $e^-$  ( $VE$ )


### Based on free $e^-$

Conductor — Highest no. of free  $e^-$ .

Semi Conductor — very less no. of free  $e^-$  at room temperature.

Insulators — 0 free  $e^-$  at room temperature.


### Energy Band in solids

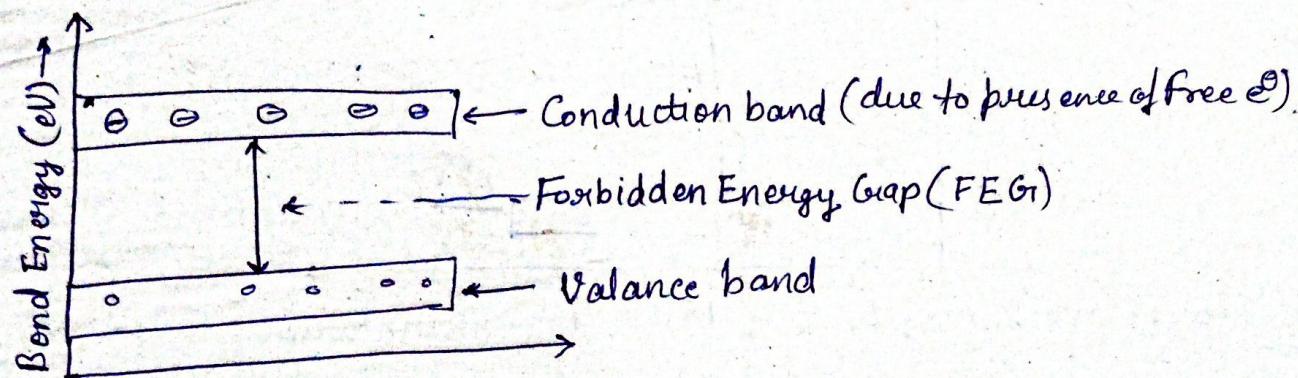

$$1 \text{ eV} = q \times V = 1.6 \times 10^{-19} \text{ C} \times 1 \text{ V} = 1.6 \times 10^{-19} \text{ J.}$$




$$FEG_i = 1.1 \text{ eV}$$

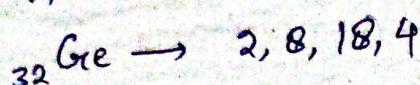

$$FEG_i = 0.72 \text{ eV}$$
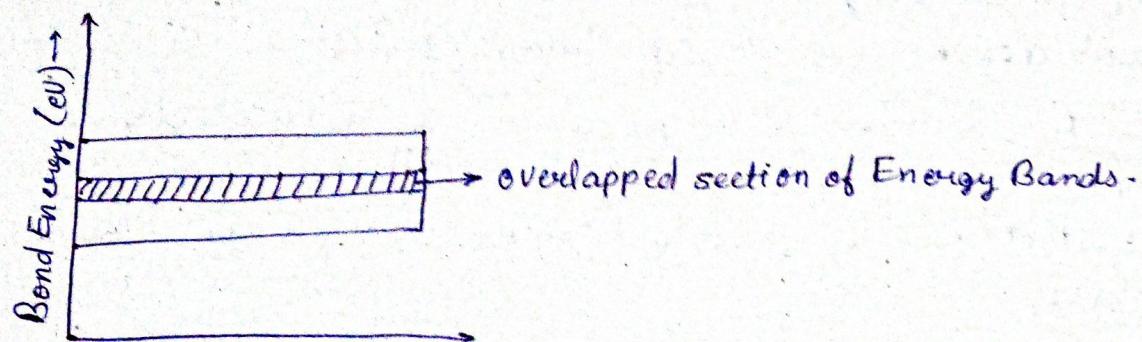
## Energy Band in Conductors


Conduction Band and Valance Band overlaps in conductor.



Forbidden Energy Gap is 0 in conductors.
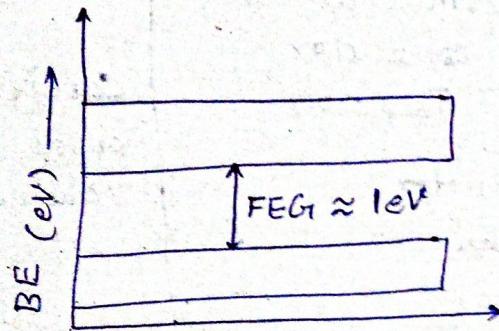
## Energy Band in Semi Conductor


Conduction Band and Valance Band are closer  $\approx 1\text{ eV}$  FEG<sub>i</sub>



Obviously, Forbidden Energy Gap = 1 eV in Semiconductors.
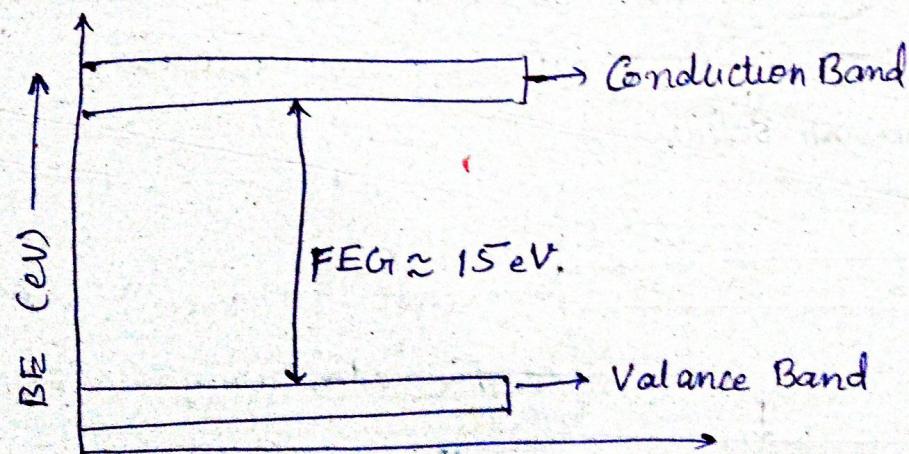
## Energy Band in Insulators

Conduction Band and Valance Band are far away.



Forbidden Energy Gap is 15 eV in insulators.

The Energy possessed by Free  $e^-$ (s) is Conduction Band.

The Energy possessed by Valence  $e^-$ (s) is Valance Band.

## Lecture 02

Semiconductors are the materials whose conductivity lies in between that of conductors and insulators.

It has -ve temperature coefficient of Resistance i.e. With  $T$  in temp. Resistance  $\downarrow$ . Its conductivity can also be changed.

e.g.  $_{14}^{30}\text{Si}$ ,  $_{32}^{64}\text{Ge}$ .

$E_g$  denotes FEG i.e. Forbidden Energy Gap.

$E_g$  of Ge = 0.72 eV;  $E_g$  of Si = 1.1 eV.

Covalent Bond is present in Germanium and Silicon.

### Effect of Temperature on Semiconductor


- (1) At absolute zero i.e. 0 K, Semiconductor behaves as Insulator due to absence of covalent bond.
- (2) Above absolute zero,  $e^\ominus(s)$  move from VB to CB resulting in formation of holes (positively charged carrier).

Holes current and  $e^\ominus(s)$  current b/w Conduction Band and Valence Band takes place.

The direction of Holes current and  $e^\ominus(s)$  current is always quite opposite.
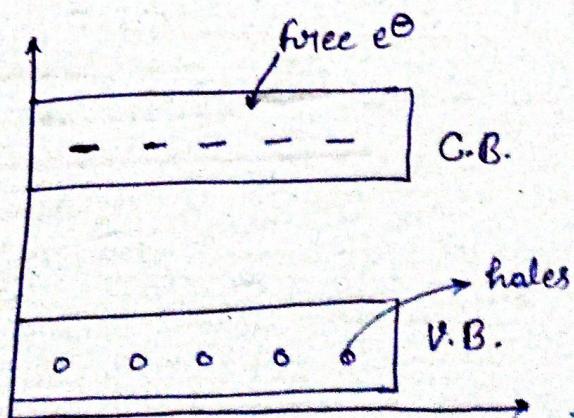
### Intrinsic Semiconductor (Pure Semiconductor)

The no. of holes in V.B and no. of free  $e^\ominus$  in C.B. are equal in pure semiconductors.




Extrinsic Semiconductor is also known as Impure or doped Semiconductor.

Pure Semiconductor + Dopeants (Impurities)  $\rightarrow$  Extrinsic Semiconductor

There are two types of Extrinsic Semiconductor —


(I) n-type Semiconductor In this semiconductor, Pentavalent Dopeants are doped and  $e^-$  (S) are Majority carriers.

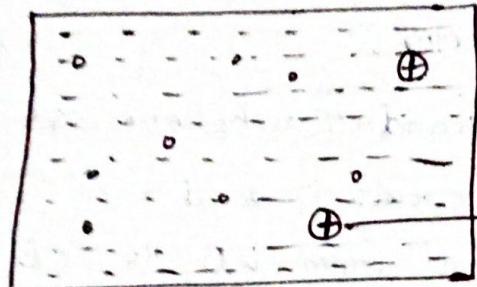(II) p-type semiconductor In this semiconductor, Trivalent Dopeants are doped and Holes are majority carriers.



n-type

Fixed Donor/ Pentavalent Ions.

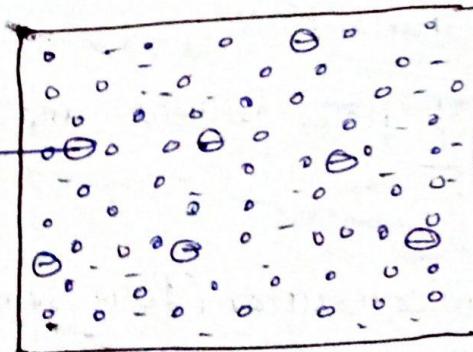


Fixed/ static Acceptor Ions

p-type

## Lecture 03

PN Junction is a diode made by junction at P-type and N-side to P-side. Due to absence of free carriers, depletion region is formed and its boundaries act as barrier for movement of carriers.


Acceptors

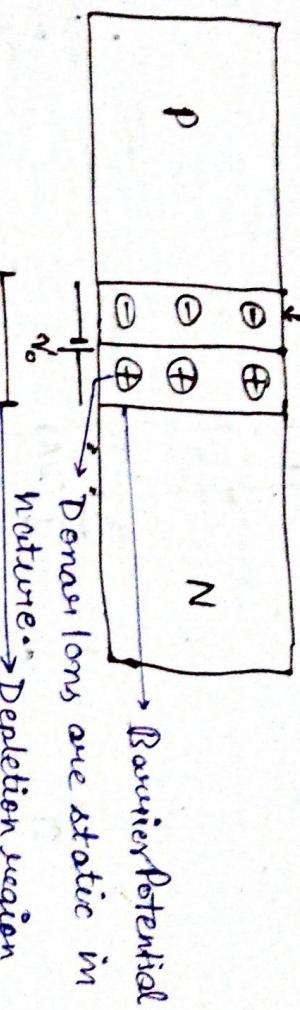

$$V_o(\text{acc}) = 0.3 \text{ V} \quad \text{and} \quad V_o(\text{CSI}) = 0.7 \text{ V}$$


### External Biasing

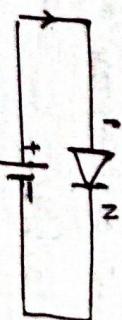
(i) Forward Biasing The external Potential must be greater than Built-in Potential for forward Biasing. In F.B., the depletion region less and finally vanishes.



In it, P side is connected to +ve terminal and N side is connected to -ve terminal of battery.

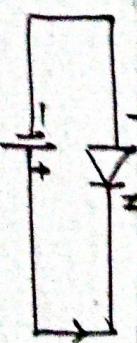(ii) Reverse Biasing In forward-opposite i.e. Reverse Biasing, P side is connected to -ve terminal and N side is connected to +ve terminal of external Voltage source. The depletion region increases as  $\vec{E}$  are in same direction resulting no movement of free carriers.  $\therefore I_D = 0$ . Reverse saturation current due to minority carriers comes into picture in reverse Biasing.



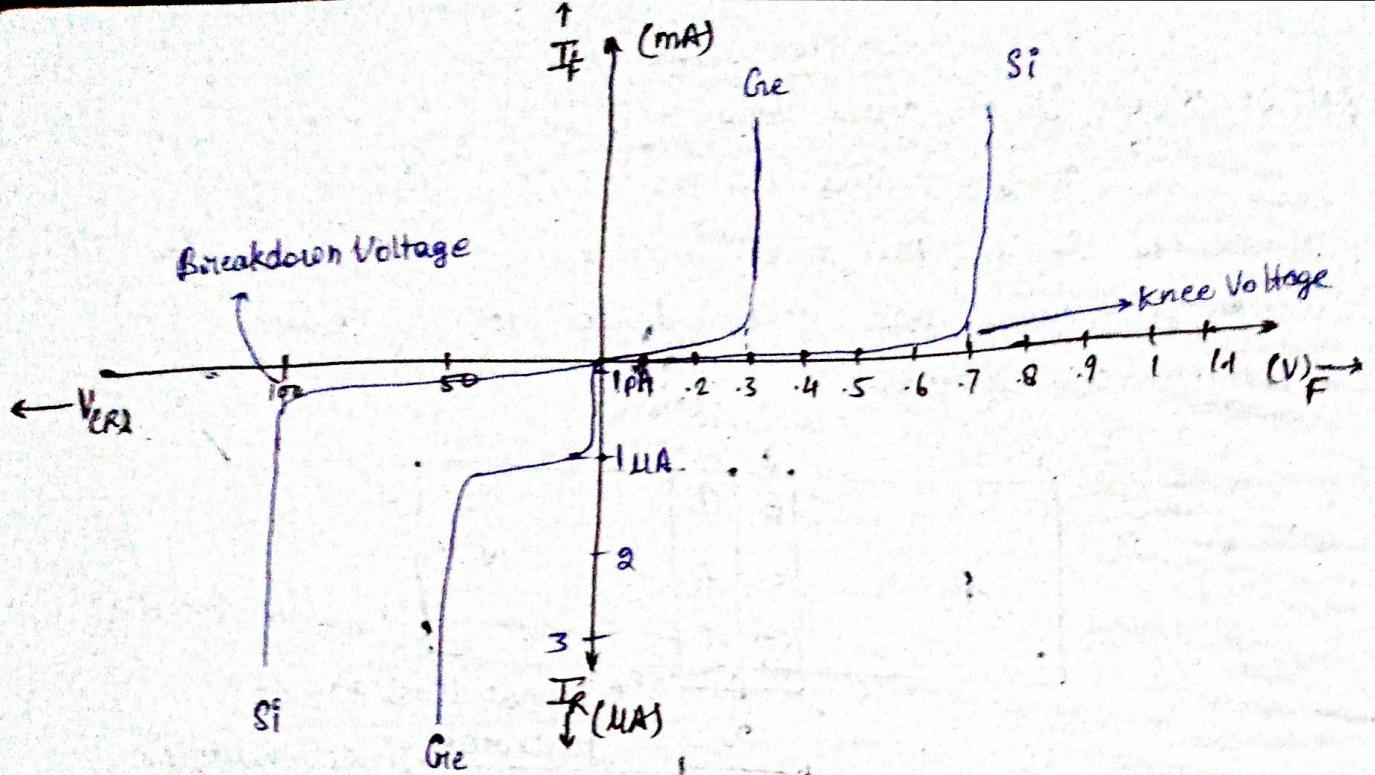

V-I characteristic of a P-N Junction diode

$$I_D = I_0 (e^{V_D / n V_T} - 1); \quad \eta(\text{Ge}) = 1 \quad \text{and} \quad \eta(\text{Si}) = 2$$

$$V_T = \frac{k_B T}{Q} \quad (\text{Volt equivalent of Temperature}) \approx 26 \text{ mV at } 300 \text{ K.}$$

$I_D$  is diode current and  $V_D$  is voltage applied to diode.  $I_0$  is reverse saturation current or Reverse leakage current.

In Forward Bias,  $I_D \approx I_0 e^{V_D / n V_T}$ .

In Reverse Bias,  $I_D \approx I_0$ .

Note: Ge, Si are single crystal semiconductors while Gra is compound semiconductor.

	Knee V (v)	$I_0$
Ge	0.3	10 pA
Si	0.7	10 pA
Gra	1.2	5 pA

Temperature dependence of V-I characteristic

In forward Bias, V-I characteristic shifts towards left at a rate of  $2.5 \text{ mV}/^\circ\text{C}$   $\uparrow$  in temp.

In Reverse Bias,  $I_0$  doubles with  $10^\circ\text{C}$  rise in temp., the breakdown voltage also  $\uparrow$ .

## Lecture 04

Semiconductor Diode is the diode made up of semiconductor materials.

e.g. PN Junction diode



### Properties

- (I) It conducts in only one direction and opposes in another.
- (II) In ideal conditions, Forward Biased diodes behaves as short circuit while Reverse Biased diodes behaves as open circuit.
- (III) During F.B.,  $V_m = V_{out}$ , during R.B.,  $V_{out} = 0$ .
- (IV) Forward Resistance ( $R_F$ ) is negligible in diodes.
- (V) Under ideal conditions, Reverse resistance is very high  $\approx \infty$ .
- (VI) For Germanium,  $\frac{\text{AC reverse Resistance}}{\text{AC forward Resistance}} = 4 \times 10^4$ .

For Silicon,

$$\frac{r_s}{r_f} = 1 \times 10^6.$$

### Resistance in diodes


#### (I) Forward Resistance

- (a) AC forward Resistance ( $r_f$ ) =  $\Delta V_F / \Delta I_F$
- (b) DC forward Resistance ( $R_f$ ) =  $V_F / I_F$


#### (II) Reverse Resistance

- (a) AC Reverse Resistance ( $r_r$ )
- (b) DC Reverse Resistance.

Equivalent circuit of PN Junction diode

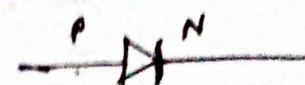

#### (I) Approximate model

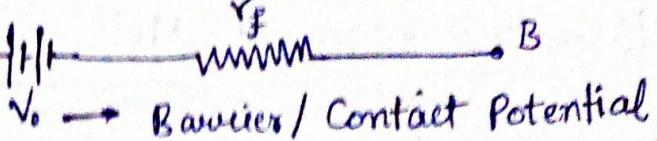

#### (II) Simplified model




#### (III) Ideal model




## Lecture 05

### Load Line Analysis

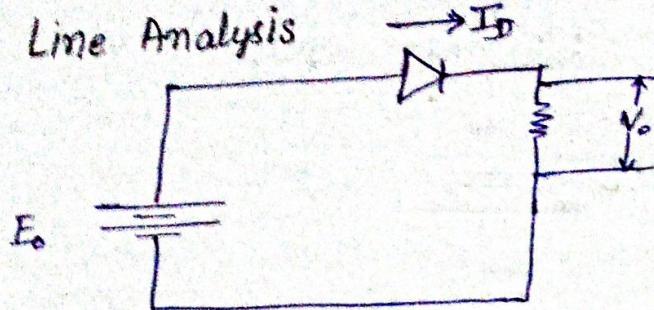

According to KVL,  $E_o = V_D + I_D R$ .

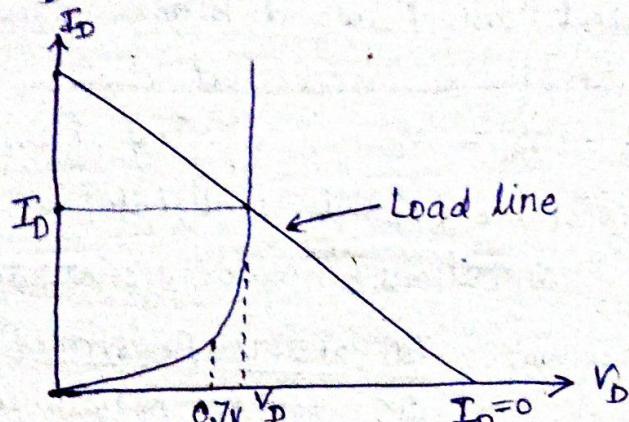


Depending on  $R$ , the slope of line varies,  $V_D = E$  so it is  $k/a$  load line.

**Rectifier** converts A.C. signal to D.C. signal.


There are two types of Half wave and full wave-

Half wave Rectifier

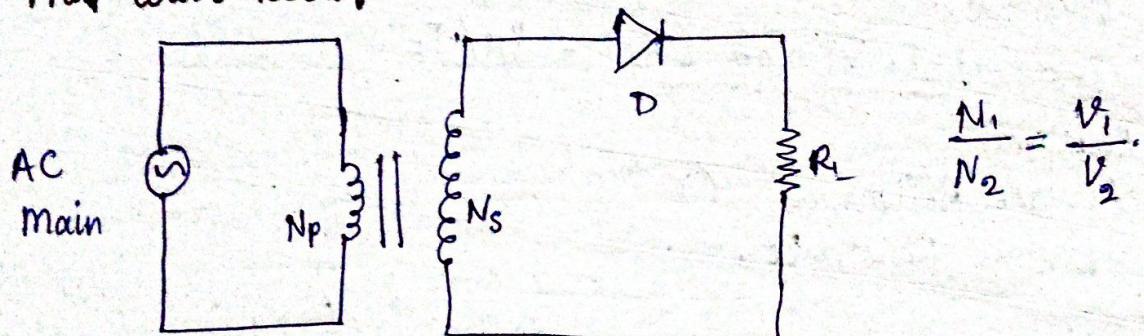

$$\frac{N_1}{N_2} = \frac{V_1}{V_2}$$

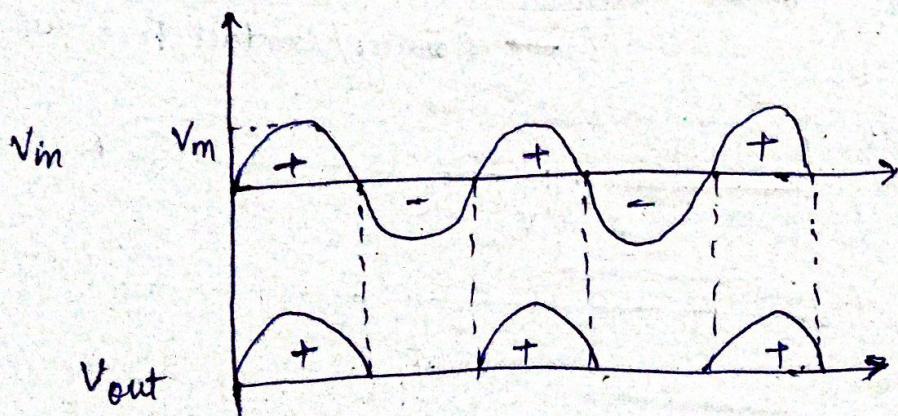Phasor diagram of Half wave rectifier for an ideal diode



$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_o^2 d\theta} = \sqrt{\frac{1}{2\pi} \left[ \int_0^\pi I_m^2 \sin^2 \theta d\theta + \int_\pi^{2\pi} 0 d\theta \right]} \\ = \sqrt{\frac{I_m^2}{2\pi} \int_0^\pi \frac{1 - \cos 2\theta}{2} d\theta} = \sqrt{\frac{I_m^2}{4\pi} \left| \theta - \frac{\sin 2\theta}{2} \right|_0^\pi}$$

$$I_{rms} = I_m/2.$$

For a Half wave rectifier,  $I_{rms} = I_m/2$ ,  $V_{rms} = V_m/2$ .

$$I_{d.c.} = \frac{\int_0^\pi i_o d\theta}{2\pi} = \frac{I_m}{\pi}, \quad V_{d.c.} = V_m/\pi.$$

Efficiency of a Half wave Rectifier -

$$\eta = \frac{\text{output power}}{\text{input power}} = \frac{(I_m/\pi) \times R_L}{(I_m/2)^2 \times (R_L + r_f)} = \frac{4}{\pi^2} \frac{R_L}{(R_L + r_f)}.$$

$$\therefore \eta = \frac{4}{\pi^2} \frac{1}{\left(1 + \frac{r_f}{R_L}\right)} \approx \frac{4}{\pi^2}.$$

$$\text{H.W.R's } \eta_{max} = 4/\pi^2 \approx 0.406 = 0.406 \times 100 = 40.6\%.$$

under ideal condition, i.e. if it is maximum,  $V_{out} = V_{in}$

$$\frac{V_{rms}}{V_{dc}} = \text{Form factor} \approx 1.57 = \frac{V_m/\pi}{V_m/2} = \frac{V_m/2}{V_m/\pi} = \pi/2.$$

$$I_{rms} = I_m/2, \quad I_{dc} = I_m/\pi. \quad f_{out} = f_{in} \quad (T_{in} = T_{out})$$

$$\eta = .406.$$

Aim of rectifier is to convert A.C. signal to Pulsating D.C. signal which after being filtered gives pure d.c. signal. It is interesting to note  $V_{rms} > V_{d.c.}$

## Lecture 06

Ques  
50 m  
Main



Transformer is used either to  $\frac{1}{\sqrt{2}}$  input A.C. voltage and prevent electrical shocks.  $V_m = V_{m \text{ max}} \cdot \theta = \omega t$

Ripple factor =  $\frac{\text{r.m.s. value of ac component}}{\text{d.c. value of d.c. output}} \cdot \frac{(I_m)_{\text{ac}}}{I_{\text{dc}}}$

$$\frac{(I_m)_{\text{ac}}}{I_{\text{dc}}} = \sqrt{\frac{(I_m)^2 - I_{\text{dc}}^2}{I_{\text{dc}}^2}} = \sqrt{\left(\frac{I_m}{I_{\text{dc}}}\right)^2 - 1} \approx 1.91 \text{ for HWR.}$$


if Ripple factor is 0, a.c. component in output = 0.

$$V_m = V_{m \text{ max}} \theta.$$

### Full Wave Rectifier (FWR)

- Centre tapped
- Bridge tapped
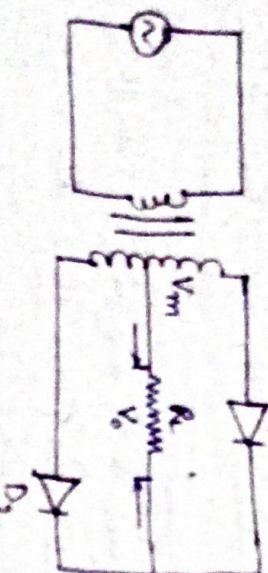
#### (a) Centre Tapped Full Wave Rectifier



$$\text{Efficiency, } \eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{(I_{\text{dc}})^2 \times R_L}{(I_m)^2 (r_f + r_L)}$$

$$= \frac{(2I_m/\sqrt{2})^2 \times R_L}{(I_m/R_L)^2 (r_f + r_L)} = \frac{2 \times 400}{(1+r_f/R_L)} = \frac{0.012}{(1+r_f/R_L)}$$

$$\eta \approx 0.012 = 0.12 \%$$

$$\eta_{\text{max}} = 0.12 \%$$

Peak inverse voltage (PIV) =  $2V_m$ . PIV is present during


Reverse bias only.

$$\text{Ripple factor} = \frac{(I_m)_{\text{ac}}}{I_{\text{dc}}} = \sqrt{\left(\frac{I_m}{I_{\text{dc}}}\right)^2 - 1} \approx 0.482$$

lowerripple factor, lower the a.c. component and better Rectifier Circuit.

## Lecture 07

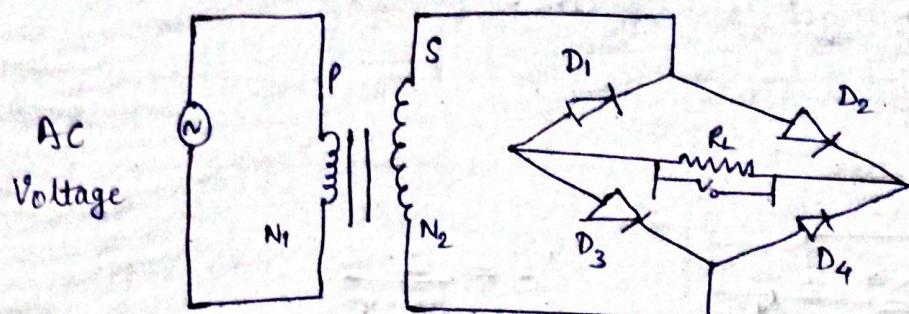
### (2) Bridge Tapped Full Wave Rectifier



$$V_i = V_m \sin \omega t = V_m \sin \theta.$$

**Working:** During the Half cycle of input current,  $D_2$  and  $D_3$  are in forward Bias while  $D_1$  and  $D_4$  are in Reverse Bias.

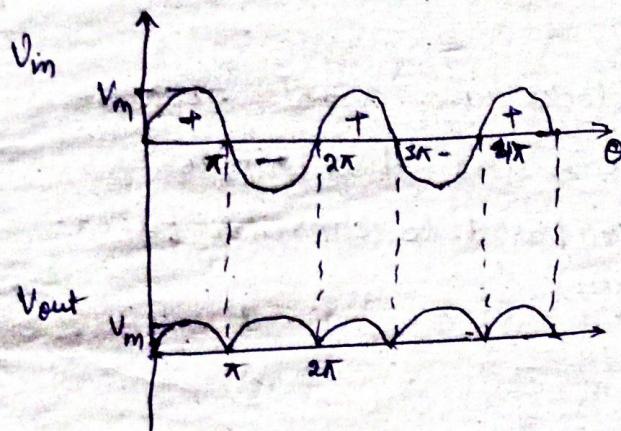During -ve Half cycle of input current,  $D_1$  and  $D_4$  are in Forward Bias while  $D_2$ ,  $D_3$  are in Reverse Bias.



$$I_{rms} = I_m / \sqrt{2}$$

$$V_{rms} = V_m / \sqrt{2}$$

$$I_{dc} = 2I_m / \pi$$

$$V_{dc} = 2V_m / \pi$$

$$V_{out} = 2V_{in}$$

$$PIV = V_m.$$

$$\text{Ripple factor} = \frac{(I_{rms})_{dc}}{I_{dc}} = 0.482 \quad \eta = \frac{P_{out}}{P_{in}} = .812 \Rightarrow \eta_{max} = 81.2\%$$


	HWR	CTFWR	BTFWR
No. of Diodes	1	2	4
Transformer	No	C-Tapped Transformer	No
$I_{rms}$	$I_m / 2$	$I_m / \sqrt{2}$	$I_m / \sqrt{2}$
$I_{dc}$	$I_m / \pi$	$2I_m / \pi$	$2I_m / \pi$
PIV	$V_m$	$2V_m$	$V_m$
Ripple factor	1.21	.482	.482
$\eta_{max}$	40.6%	81.2%	81.2%
$V_{out}$	$V_{in}$	$2V_{in}$	$2V_{in}$

## Lecture 08


Output of rectifier is pulsating d.c. and by using filter circuit, we can get pure d.c.

Types of filter circuit

(I) Capacitor filter

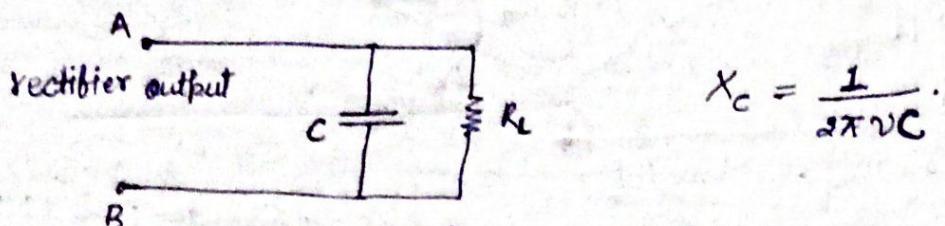


(II) Choke filter circuit

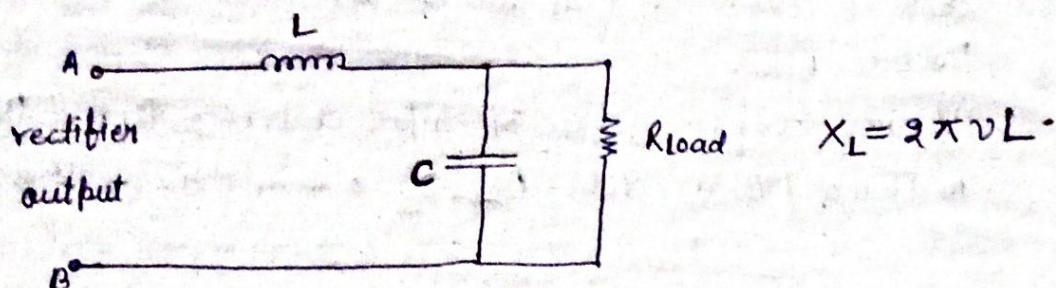


Inductor passes d.c. signal and blocks a.c. signal because  $X_L = 0$  (d.c.)  $X_C = \infty$  (a.c.) and thus ripple is reduced in higher extent compared to capacitor filter.

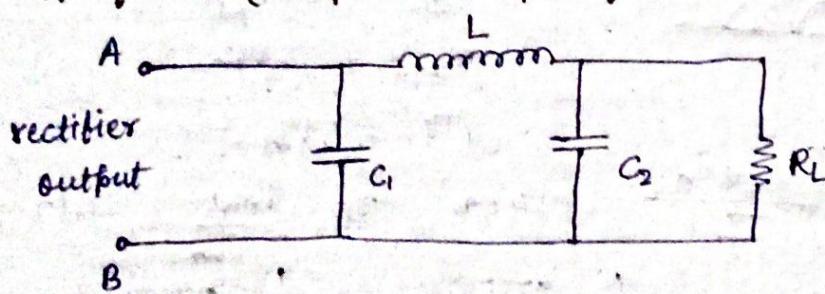(III)  $\pi$ -filter (Capacitor input filter)



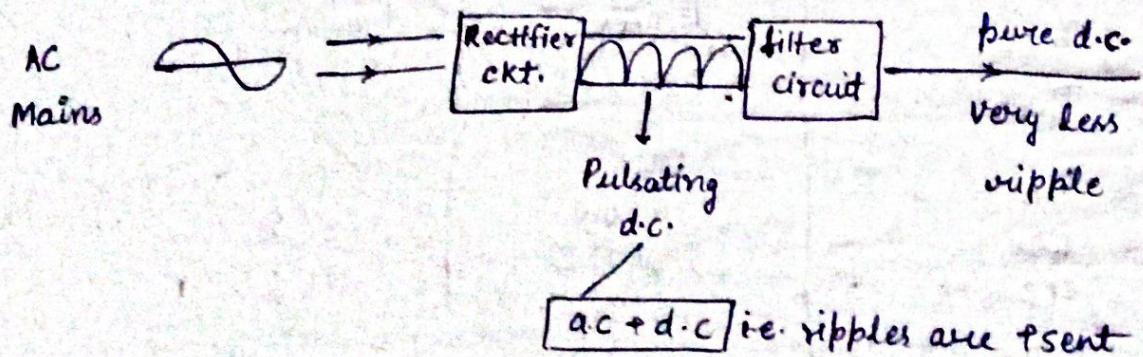In this case, ripple is reduced at the highest extent.




## Lecture 09

Clipper circuits are those circuit which 'clip' some portions of input waveform without disturbing the remaining part of the waveform.


### Types

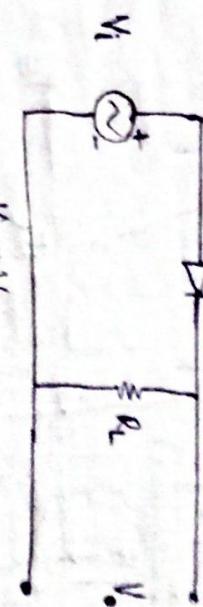(i) Series clippers (Simplest form of clipper circuit)



$$V_o = V_m.$$

(ii) Parallel clipper

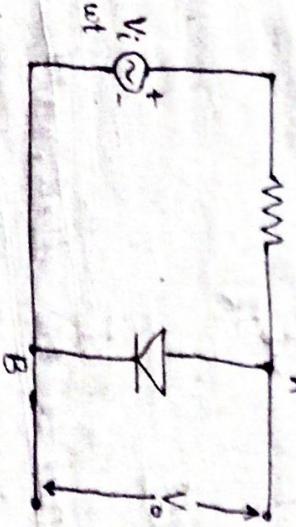


$$V_o = V_h - V_k = 0 \quad [\text{in forward}]$$

$$\text{As. } V_h = V_k$$

$$\text{But } V_o = -V_m \quad [\text{in reverse}]$$

So +ve part is clipped.

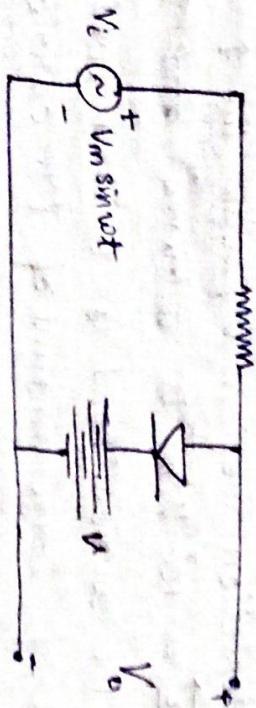
By applying some external D.C. bias, we can clip a specific part of input waveform.



During +ve half cycle,  $V_o = V$ . During -ve half cycle,  $V_o = V_i = -V_m$ .
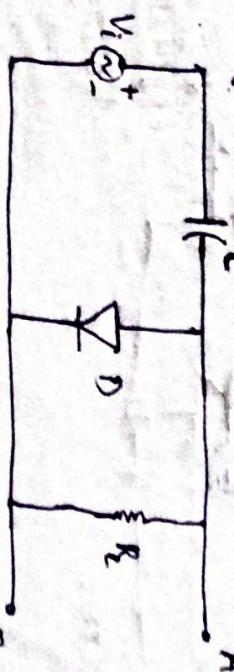
### Clamper Circuits

It shifts the d.c. level to a different d.c. level without distorting input waveform.




$$V_o = 0 \quad \text{for +ve Half cycle}$$

$$\text{But for -ve Half cycle}$$

$$V_o = (-V) + (-V) = -2V$$
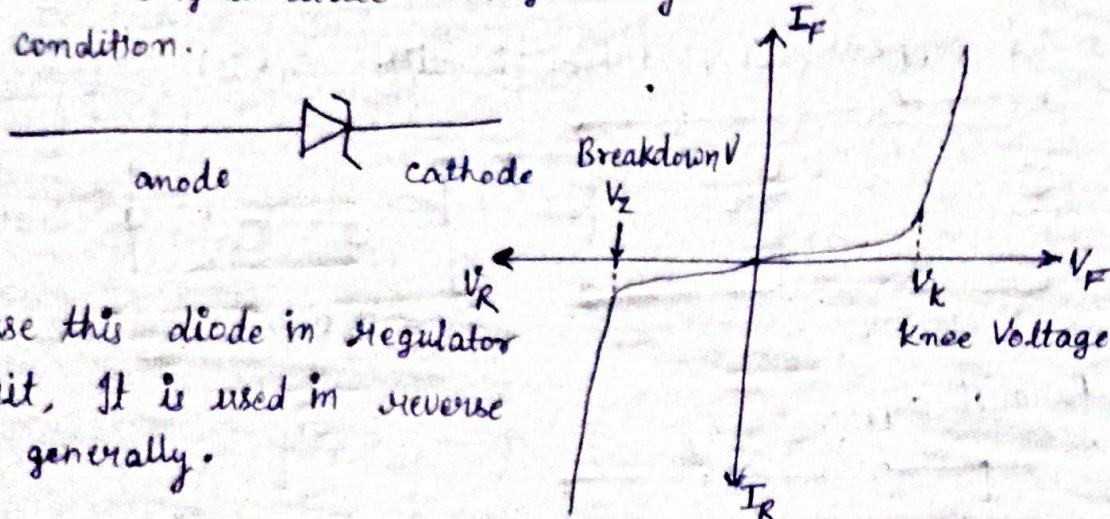
## Lecture 10

A fixed d.c supply can be got using voltage regulator. Concentration of doping level of impurity is very large in zener Diode. It is also a PN Junction diode and special crystal diode that generally works in reverse bias condition.



To use this diode in regulator circuit, it is used in reverse bias generally.

### Reverse Bias Breakdown Mechanism

#### (i) Avalanche effect


For less doped semiconductor. Due to this effect, a large amount of current is observed just after the breakdown due to presence of large no. of free charge carrier.

#### (ii) Zener Breakdown effect (due to heavily doped Si)

The depth of depletion region  $\downarrow$  with the  $\uparrow$  in doping level.  $E = 10^7 \text{ V/m}$  is achieved and Due to Very high  $E$ , the covalent bond is broken which leads in creation of large amount of free carriers.

### Application of zener diode

#### (i) for making regulator circuit.

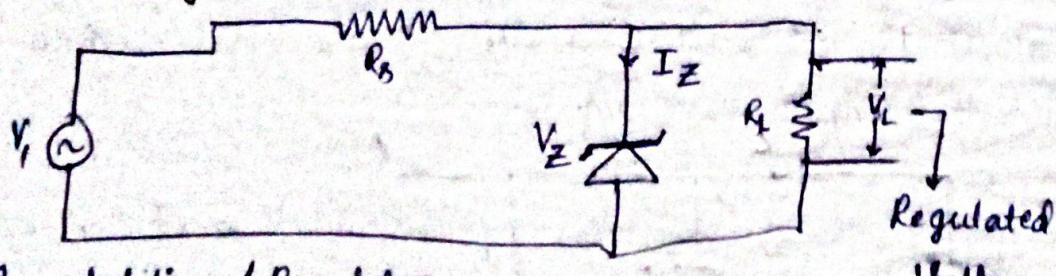

In stabilizer / Regulators :

Regulated  
Voltage

Case 1 → If  $V_{AB} = V_L \geq V_Z$ , then Diode is in 'on' condition means diode is replaced by voltage source.

Case 2 → If  $V_{AB} = V_L \leq V_Z$ , then Diode is in 'off' state means, diode is replaced by open.

During 'ON' state,  $I_R = I_Z + I_L$  [ $V_{AB} = V_L \geq V_Z$ ]  
 $\Rightarrow I_Z = I_R - I_L$ .

$$I_R = \frac{V_R}{R} = \frac{V_I - V_L}{R} \Rightarrow I_2 = \frac{V_I - V_L}{R} - \frac{V_L}{R_L}$$

$$I_L = \frac{V_L}{R_L}$$

$$P_Z = V_Z I_Z$$

$$P_Z < P_{Z\max}$$