


$$q(0^+) = \frac{42}{11} \text{ Coulomb}$$

$$V_1(0^+) = 5 + \frac{42}{11} = \frac{97}{11} \text{ V}$$

$$V_2(0^+) = 0 + \frac{42}{11} \times \frac{1}{2} = \frac{21}{11} \text{ V}$$

$$V_3(0^+) = -2 + \frac{42}{11} \times \frac{1}{3} = -\frac{8}{11} \text{ V}$$

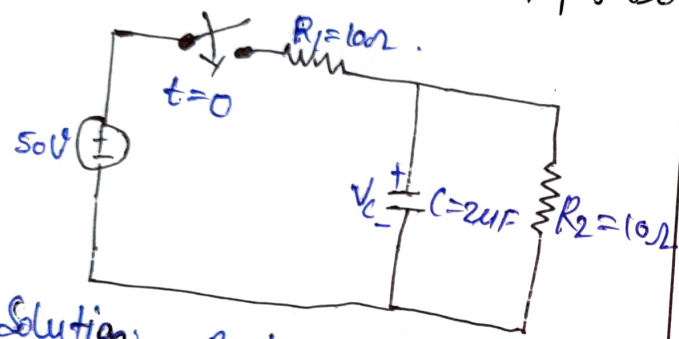Question: - In figure, the switch is closed at $t=0$. Find the current i and capacitor voltage V_c , for $t > 0$.



Solution: - By KVL, we can write,
 $10(i_1 + i_2) + 0.01 \frac{di_1}{dt} + 5i_1 - 100 = 0 \rightarrow (1)$
 and $10(i_1 + i_2) + 5i_2 - 100 = 0 \rightarrow (2)$
 putting i_2 from eqn (2) in eqn (1), we get -

$$10 \left[i_1 + \frac{100 - 10i_1}{15} \right] + 0.01 \frac{di_1}{dt} + 5i_1 - 100 = 0$$

$$\text{or, } \frac{di_1}{dt} + 833i_1 = 3333$$

The solution of this equation is given by -

$$i_1 = i_{th} + i_{tp}$$

$$i_{th} = K e^{-833t} \text{ A}$$

$$i_{tp} = \frac{3333}{833} = 4.0 \text{ A}$$

$$i_1 = K e^{-833t} + 4$$

Consider current passes through R_2 is i_1 .

By KVL, we can write,

$$R_1 \cdot i + \frac{1}{C} \int (i - i_1) dt - 50 = 0 \rightarrow (1)$$

and $R_2 \cdot i_1 - \frac{1}{C} \int (i - i_1) dt = 0 \rightarrow (2)$

On differentiation, we have.

$$R_1 \frac{di}{dt} + \frac{1}{C} (i - i_1) = 0 \rightarrow (3)$$

and $R_2 \frac{di_1}{dt} - \frac{1}{C} (i - i_1) = 0 \rightarrow (4)$

Step 1: - Calculation of i .

putting i_1 from eqn (3) in eqn (4), we get,

$$R_2 \frac{d}{dt} \left(R_1 C \frac{di}{dt} + i \right) - \frac{1}{C} \left[i - \left(R_1 C \frac{di}{dt} + i \right) \right] = 0$$

$$\text{or, } R_1 R_2 C \frac{d^2 i}{dt^2} + R_2 \frac{di}{dt} - \frac{i}{C} + R_1 \frac{di}{dt} + \frac{i}{C} = 0$$

$$\text{or, } R_1 R_2 C \frac{d^2 i}{dt^2} + (R_1 + R_2) \frac{di}{dt} = 0 \rightarrow (5)$$

putting given values of R_1, R_2 and C , then we get

$$(10)(10)(2 \times 10^{-6}) \frac{d^2 i}{dt^2} + (10 + 10) \frac{di}{dt} = 0$$

$$\text{or, } \frac{d^2 i}{dt^2} + 105 \frac{di}{dt} = 0 \rightarrow (6)$$

The auxiliary eqⁿ is given by

$$m^2 + 10^5 m = 0$$

$$m = 0, -10^5$$

Therefore, the solution of eqⁿ ⑥ is given by

$$i = K_1 e^0 + K_2 e^{-10^5 t} \rightarrow (7)$$

Step II:- calculation of i_1 .

From eqⁿ ④, we have

$$i_1 = R_1 C \frac{di}{dt} + i \rightarrow (8)$$

putting i from eqⁿ ⑦ in eqⁿ ⑧, we get -

$$\dot{i}_1 = 10 \times 2 \times 10^{-6} \frac{d}{dt} (K_1 + K_2 e^{-10^5 t}) + K_1 + K_2 e^{-10^5 t}$$

$$= 2 \times 10^{-5} [-10^5 K_2 e^{-10^5 t}] + K_1 + K_2 e^{-10^5 t}$$

$$i_1 = K_1 - K_2 e^{-10^5 t} \rightarrow (9)$$

Step III:- calculation of V_c ,

we have

$$V_c = \frac{1}{C} \int_{-\infty}^t (i - i_1) dt = R_2 i_1 \rightarrow (10)$$

From eqⁿ ⑨ and ⑩, we have

$$V_c = 10 (K_1 - K_2 e^{-10^5 t}) \rightarrow (11)$$

Step IV:- calculation of K_1 and K_2 .

we have $V_c(0^-) = 0$

As $t \rightarrow \infty$, the capacitor becomes open circuited, leaving 20V in series with the 50V, i.e.

$$i(\infty) = \frac{50}{20} = 2.5 \text{ A}$$

$$V_c(\infty) = \text{Voltage across } 10\Omega$$

$$= 10 \times 2.5 = 25 \text{ V}$$

Now for,

$V_c(0^-) = 0$, from eqⁿ ⑪, we have

$$25 = 10 (K_1 - K_2 e^0)$$

$$25 = 10 (K_1 - 0)$$

$$\boxed{K_1 = 2.5}$$

Therefore, the current is given by eqⁿ ⑦, after putting K_1 and K_2 as -


$$i = 2.5 (1 + e^{-10^5 t}) \text{ A}$$

and V_c is given by eqⁿ ⑪, after putting K_1 and K_2 as -

$$V_c = 10 (2.5 - 2.5 e^{-10^5 t})$$

$$\boxed{V_c = 25 (1 - e^{-10^5 t}) \text{ V}}$$

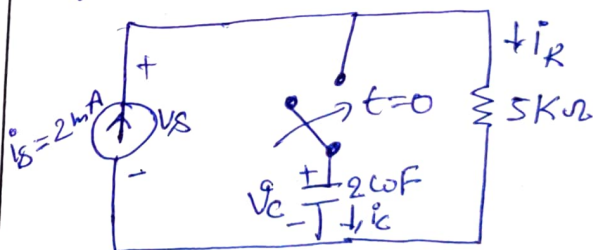Question:- In figure, the switch is closed at $t=0$. The capacitor has no charge for $t < 0$. Find i_R , i_c , V_c and V_s for all instants if $I_S = 2 \text{ mA}$.



Solution:- Step I:- To obtain initial condition.

For $t < 0$, the circuit becomes as shown in figure, in this case capacitor behaves as open circuited.

For $t < 0$, $i_R = 2 \text{ mA}$, $i_c = 0$, $V_c = 0$,

$$V_s = 2 \times 10^{-3} \times 5 \times 10^3 = 10 \text{ V}$$


Step II:- To obtain i_R , i_c , V_c and V_s for $t > 0$.
after switching, the circuit becomes

As shown in figure (b)

We have

$$i_R + i_C = 2 \times 10^{-3}$$

$$i_S = 2 \text{ mA}$$

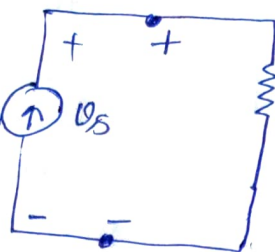


By KVL, we can write

$$R i_R - \frac{1}{C} \int_{-\infty}^t i_C dt = 0$$

$$R i_R - \frac{1}{C} \int_{-\infty}^t (2 \times 10^{-3} - i_R) dt = 0$$

on differentiation, we get
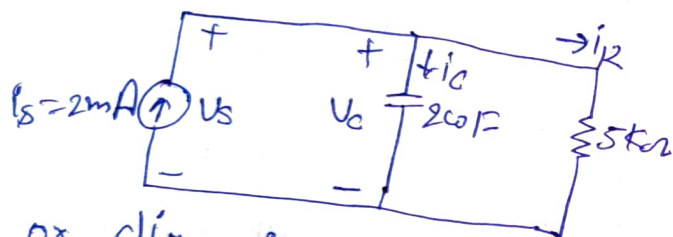
$$R \frac{di_R}{dt} - \frac{1}{C} (2 \times 10^{-3} - i_R) = 0$$



$$\text{or, } \frac{di_R}{dt} + \frac{i_R}{RC} = \frac{2 \times 10^{-3}}{RC}$$

The solution of this eqⁿ is given by -

$$i_R = i_{R1} + i_{R2}$$

$$\text{where, } i_{R1} = K e^{-t/RC}$$

$$i_{R2} = \frac{\frac{2 \times 10^{-3}}{RC}}{\frac{1}{RC}} = 2 \times 10^{-3}$$

$$i_R = K e^{-t/RC} + 2 \times 10^{-3} \rightarrow (2)$$

For calculation of K using initial condition.

We have, $V_C(0^-) = 0$ (initial condition)

We know that,

$$V_C = \frac{1}{C} \int_{-\infty}^t i_C dt$$

$$= V_C(0^-) + \frac{1}{C} \int_0^t i_C dt$$

$$V_C = \frac{1}{C} \int_0^t i_C dt \rightarrow (3)$$

From eqⁿ (1), (2) and (3) we have

$$V_C = \frac{1}{C} \int_0^t (-K e^{-t/RC}) dt$$

$$= RK [e^{-t/RC}]_0^t = RK (e^{-t/RC} - 1)$$

$$\text{or, } V_C = RK (e^{-t/RC} - 1) \rightarrow (4)$$

As $t \rightarrow \infty$, $V_C(\infty) = R i_R(\infty)$ (since at steady state condition capacitor behaves as open circuited).

$$\therefore 5 \times 10^3 \times i_R(\infty) = 5 \times 10^3 \times K (e^{-\infty} - 1)$$

From eqⁿ (2), we have -

$$i_R(\infty) = K e^{-\infty} + 2 \times 10^{-3} = 2 \times 10^{-3} \text{ A}$$

$$5 \times 10^3 \times 2 \times 10^{-3} = 5 \times 10^3 \times K (-1)$$

$$\text{or, } K = -2 \times 10^{-3}$$

putting the value of K in eqⁿ (2), we get -

$$i_R = 2 \times 10^{-3} (1 - e^{-t/5 \times 10^3 \times 2 \times 10^{-6}})$$

$$i_R = 2 \times 10^{-3} (1 - e^{-100t}) \text{ A} \rightarrow (5)$$

now, $i_R(0^+) = 0 \text{ A}$, $i_R(\infty) = 2 \text{ mA}$.

For i_C ; putting the value of K from eqⁿ (5) in eqⁿ (1), we get -

$$i_C = 2 \times 10^{-3} - 2 \times 10^{-3} (1 - e^{-100t})$$

$$\text{or, } i_C = 2 \times 10^{-3} e^{-100t} \text{ A}$$

$$i_C(0^+) = 2 \text{ mA}, i_C(\infty) = 0 \text{ A}$$

For V_C ; Putting $K = -2 \times 10^{-3}$ in eqⁿ (4), we get -

$$V_C = -2 \times 10^{-3} \times 5 \times 10^3 (e^{-100t} - 1)$$

$$\text{or, } V_C = 10 (1 - e^{-100t}) \text{ V}$$

$$\text{now, } V_C(0^+) = 0 \text{ V}, V_C(\infty) = 10 \text{ V}$$

for V_s ; From circuit diagram, we have -


$V_s = V_c = \text{Voltage across resistor of } 5k\Omega$

$$V_s = 10(1 - e^{100t}) \text{ V}$$

now, $V_s(0^+) = 0 \text{ V}$, $V_s(\infty) = 10 \text{ V}$

Maximum power transfer Theorem:

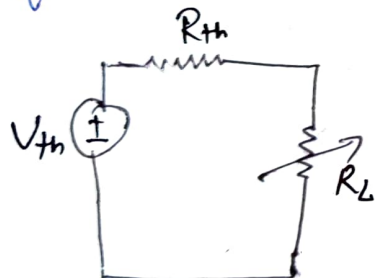According to the maximum power transfer theorem, the condition for maximum power flow through load resistor R_L can be achieved when the load resistor equals the thevenin's equivalent resistance of the circuit.



(i) power through R_L -

$$P = I_L^2 R_L \rightarrow \textcircled{i}$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} \quad (\text{Thevenin's theorem})$$

$$P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L \rightarrow \textcircled{ii}$$

differentiate the above eqⁿ w.r.t R_L and equating it to zero.

$$\frac{dP}{dR_L} = \frac{V_{th}^2}{(R_{th} + R_L)^4} \left[(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L) \right]$$

$$R_{th} - R_L = 0$$

$$\therefore \boxed{R_L = R_{th}} \rightarrow \textcircled{iii}$$

this is the required condition for max power flow.


putting the value of $R_L = R_{th}$ in eqⁿ (ii)

$$P_{max} = \frac{V_{th}^2}{(R_{th} + R_{th})^2} \cdot R_{th}$$

$$P_{max} = \frac{V_{th}^2}{4 R_{th}} \cdot R_{th}$$


$$\boxed{P_{max} = \frac{V_{th}^2}{4 R_{th}}}$$

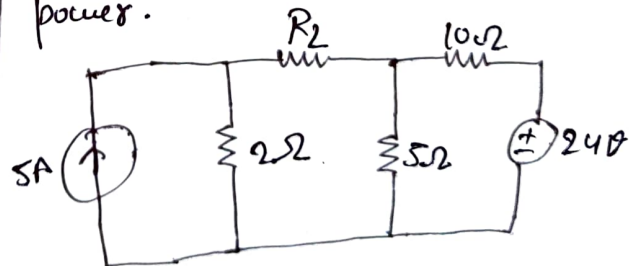Question: - In the given network find the value of R_L which will absorb the maximum power from the source. Also find the maximum power.



Solved: - $R_L = ?$

For V_{th} , removing R_L -

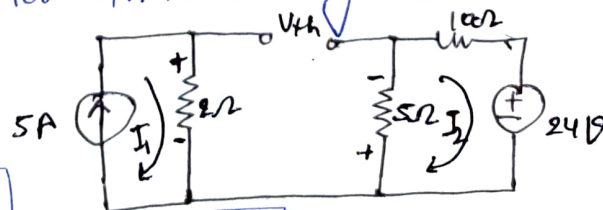


$$\boxed{I_1 = 5 \text{ A}}$$

applying KVL in mesh (2) -

$$-15I_2 = 24$$

$$I_2 = \frac{-24}{15}$$


$$I_2 = -1.6 \text{ A}$$

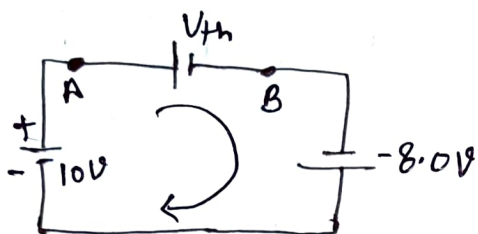

$$-V_{th} - 8 + 10 = 0$$

$$V_{th} = 2 \text{ V}$$

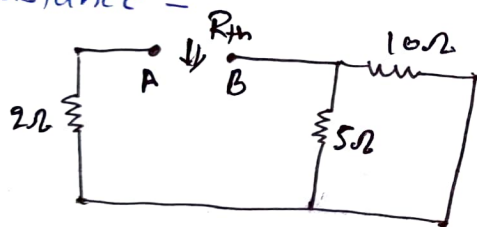Remove R_L & replace all the active sources by their internal resistance -



$$R_{th} = 5.33 \Omega$$

$$(i) \quad R_L = R_{th} = 5.33 \Omega \text{ for maximum power flow -}$$

$$(ii) \quad P_{max} = \frac{V_{th}^2}{4R_{th}} \\ = \frac{2^2}{4 \times 5.33} \\ = \frac{1}{10.66}$$

$$P_{max} = 0.187 \text{ W}$$

Question:- Find the Value of R_L in given network. Also find the maximum power in R_L .


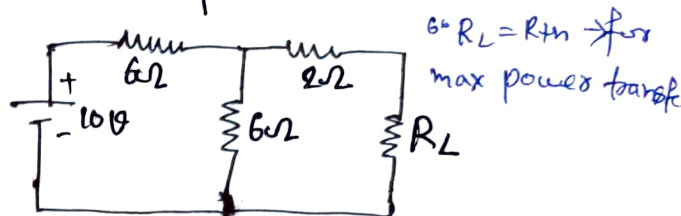


Figure - DC network ckt.

Solved:- for V_{th}

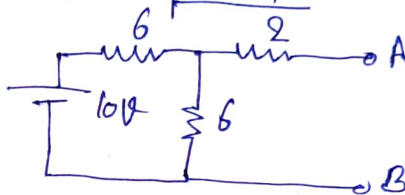

$$6I + 6I - 10 = 0$$


$$12I = 10$$

$$I = \frac{10}{12} = \frac{5}{6} \text{ A}$$

$$V_{th} = 10 - 6 \times \frac{5}{6} = 5 \text{ V}$$


$$V_{th} = 5 \text{ V}$$

for R_{th}

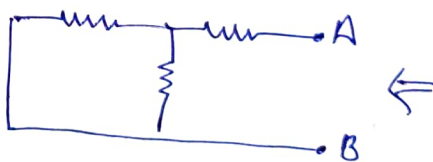

$$R_{th} = 6/6 + 2 = 5 \Omega$$

Thaenin's ckt diagram \rightarrow

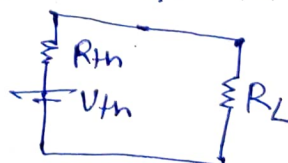

for maximum power -

$$R_L = R_{th}$$

$$R_L = 5 \Omega$$



$$P_{max} = I_L^2 \cdot R_L$$

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$P_{max} = \left(\frac{5}{5+5} \right)^2 \times 5 = \frac{25}{204} \times 5 = 1.25 \text{ W}$$

Millman's Theorem:-

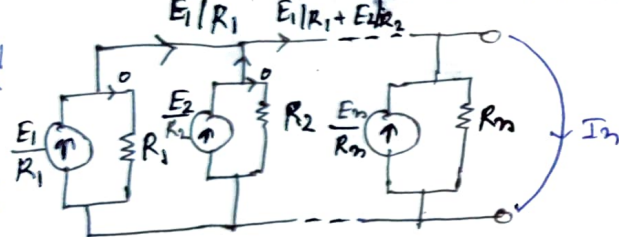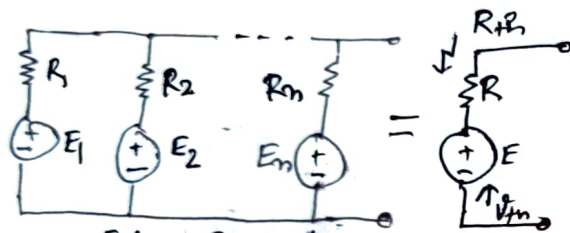"If n voltage sources with voltages $E_1, E_2, E_3, \dots, E_n$ and internal resistance $R_1, R_2, R_3, \dots, R_n$ are connected in parallel, then these voltage source can be replaced by a single voltage source E in series with resistance R ."



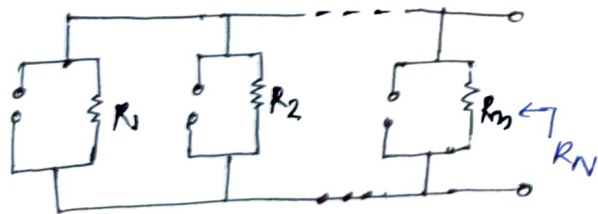
$$I_N = \frac{E_1}{R_1} + \frac{E_2}{R_2} + \dots + \frac{E_n}{R_n}$$




$$R_N = R_1 \parallel R_2 \parallel \dots \parallel R_n$$
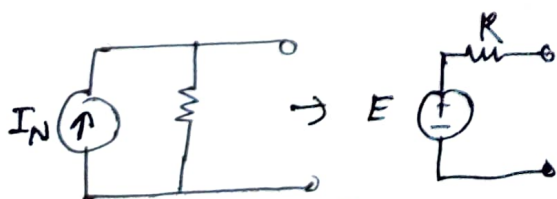
$$\frac{1}{R_N} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$



$$E = I_N R_N = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \dots + \frac{E_n}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$
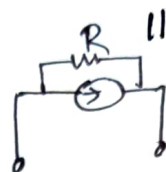
$$E = \frac{\sum_{i=1}^n E_i R_i}{\sum_{i=1}^n R_i}, R = R_n$$




$$I = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

$$I = \frac{\sum_{i=1}^n I_i R_i}{\sum_{i=1}^n R_i}$$


$$R = R_1 + R_2 + \dots + R_n$$

$$R = \sum_{i=1}^n R_i$$

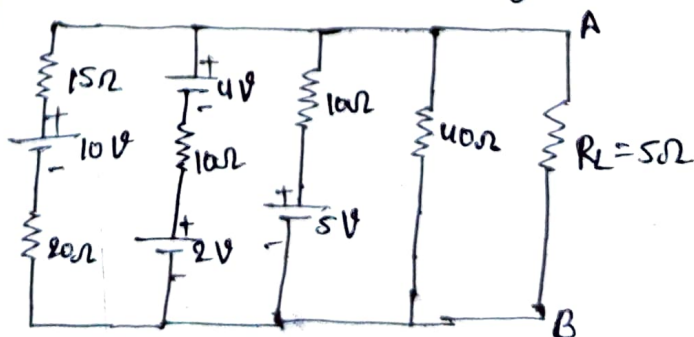Question:- Using millman's theorem, calculate current through 5Ω resistor.



P-16

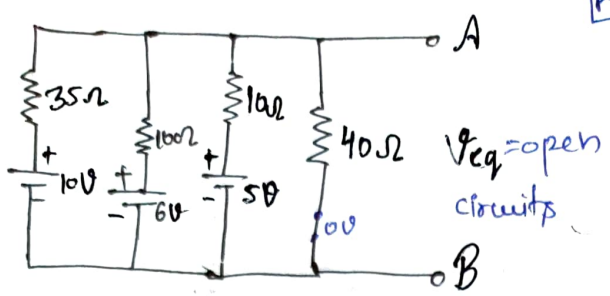

$$V_{eq} = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

$$= \frac{\frac{10}{35} + \frac{6}{10} + \frac{5}{6} + \frac{0}{40}}{\frac{1}{35} + \frac{1}{10} + \frac{1}{6} + \frac{1}{40}}$$

$$= \frac{1.3857}{0.253}$$

$$= 5.48V$$

$$\frac{1}{R_{eq}} = \frac{1}{35} + \frac{1}{10} + \frac{1}{6} + \frac{1}{40}$$


$$R_{eq} = \frac{1}{\frac{1}{35} + \frac{1}{10} + \frac{1}{6} + \frac{1}{40}} = \frac{1}{0.253}$$

$$R_{eq} = 3.94\Omega$$


$$I_L = \frac{5.48}{3.94 + 5} = 0.61A$$

$$I_L = 610mA$$

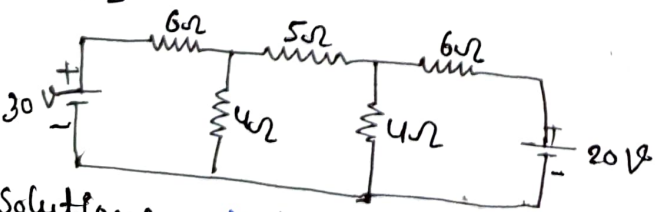Question:- Find I_L in 5Ω resistance or R_L .



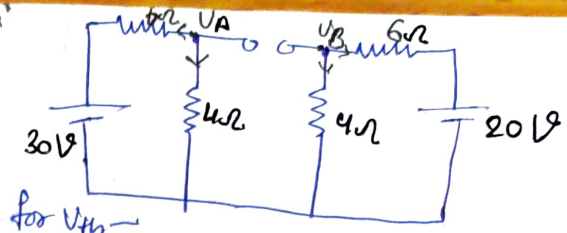Solution:- find $I_L = ?$, $R_L = 5\Omega$.
 $\therefore I_L = \frac{V_{th}}{R_{th} + R_L}$



for V_{th} -

$$\frac{V_A - 30}{6} + \frac{V_A - 0}{4} = 0$$

$$\frac{2V_A - 60 + 3V_A}{12} = 0$$

$$5V_A = 60$$

$$V_A = 12V$$

$$\Rightarrow \frac{V_B - 20}{6} + \frac{V_B - 0}{4} = 0$$

$$\Rightarrow \frac{2V_B - 40}{12} + 3A = 0$$


$$5V_B = 40$$

$$V_B = 8V$$


$$V_{th} = V_A - V_B$$

$$V_{th} = 12 - 8 = 4V$$

for R_{th} -

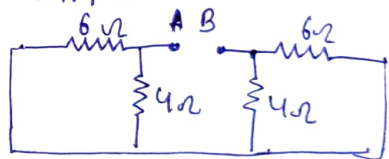


$$6||4 \Rightarrow \frac{6 \times 4}{6 + 4} = \frac{24}{10} = 2.4$$

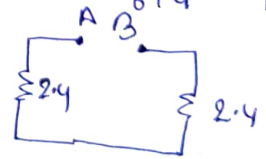

$$R_{th} = 4.8\Omega$$



Thevenin's equivalent ckt.

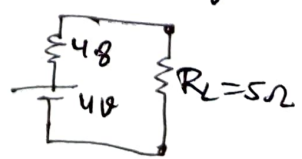


$$I_L = \frac{4}{(4.8 + 5)} = \frac{4}{9.8}$$

$$I_L = 0.004A$$

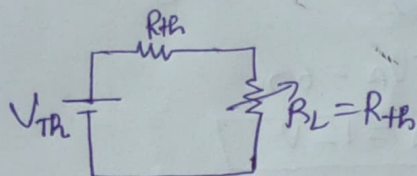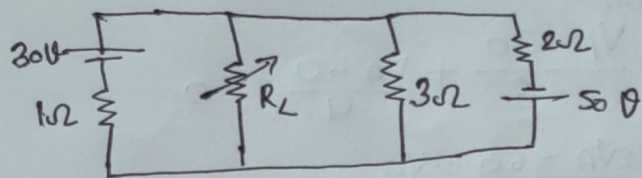Q1 find the value of resistance R_L for maximum power transfer calculate maximum power.



Find $V_{th} \rightarrow$

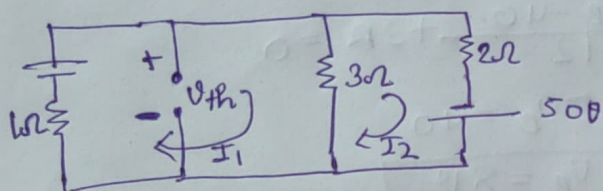

Apply KVL to mesh 1,

$$4I_1 - 3I_2 = 30$$

Apply KVL to mesh 2,

$$-3I_1 + 5I_2 = 50$$

$$I_1 = 27.27A ; I_2 = 2636A$$


$$-I_1 + 30 - V_{th} = 0$$

$$-27.27 + 30 = V_{th}$$

$$2.73V = V_{th}$$

$$V_{th} = 2.73V$$

Find $R_{th} \rightarrow$

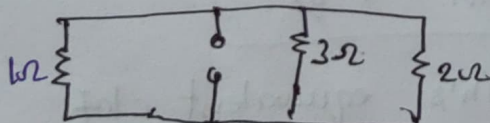

$$R_{th} = \left(\frac{1}{1} + \frac{1}{3} + \frac{1}{2} \right)^{-1}$$


$$R_{th} = 0.5454\Omega$$

$$I_L = \frac{2.73}{2(0.5454)}$$

$$= 2.502A$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(2.73)^2}{4 \times 0.5454} = 3.4162W$$

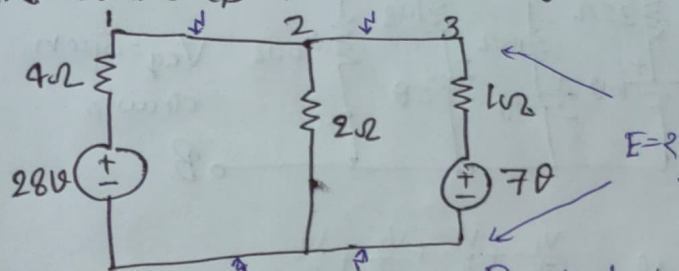Question: Find the voltage across all the branches in the below given ckt.



Solution: $E_1 = 28V$; $R_1 = 4\Omega$

$$E_2 = 0V$$
 ; $R_2 = 2\Omega$


$$E_3 = 7V$$
 ; $R_3 = 10\Omega$

$$E = \frac{\sum_{i=1}^n E_i G_i}{\sum_{i=1}^n G_i} \Rightarrow E = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$E = \frac{\frac{28}{4} + \frac{0}{2} + \frac{7}{10}}{\frac{1}{4} + \frac{1}{2} + \frac{1}{10}}$$

$$E = 8V$$

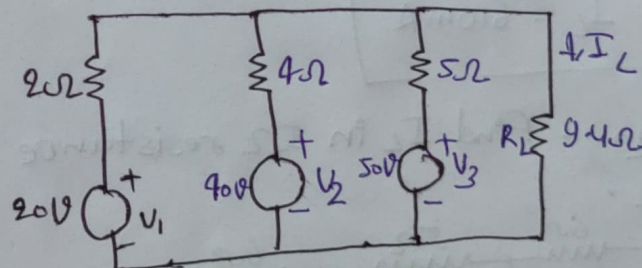Question: Use millman's theorem to find current I_L through resistor R_L for the network shown below.




$$V_{eq} = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{20}{2} + \frac{40}{4} + \frac{50}{5}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{5}}$$

$$V_{eq} = 31.57$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{5}} = 1.0326\Omega$$

$$R_{eq} = 1.0326\Omega$$

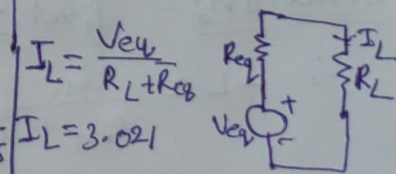

$$I_L = \frac{V_{eq}}{R_L + R_{eq}}$$

$$I_L = 3.021$$

$$I_L = 3.021A$$