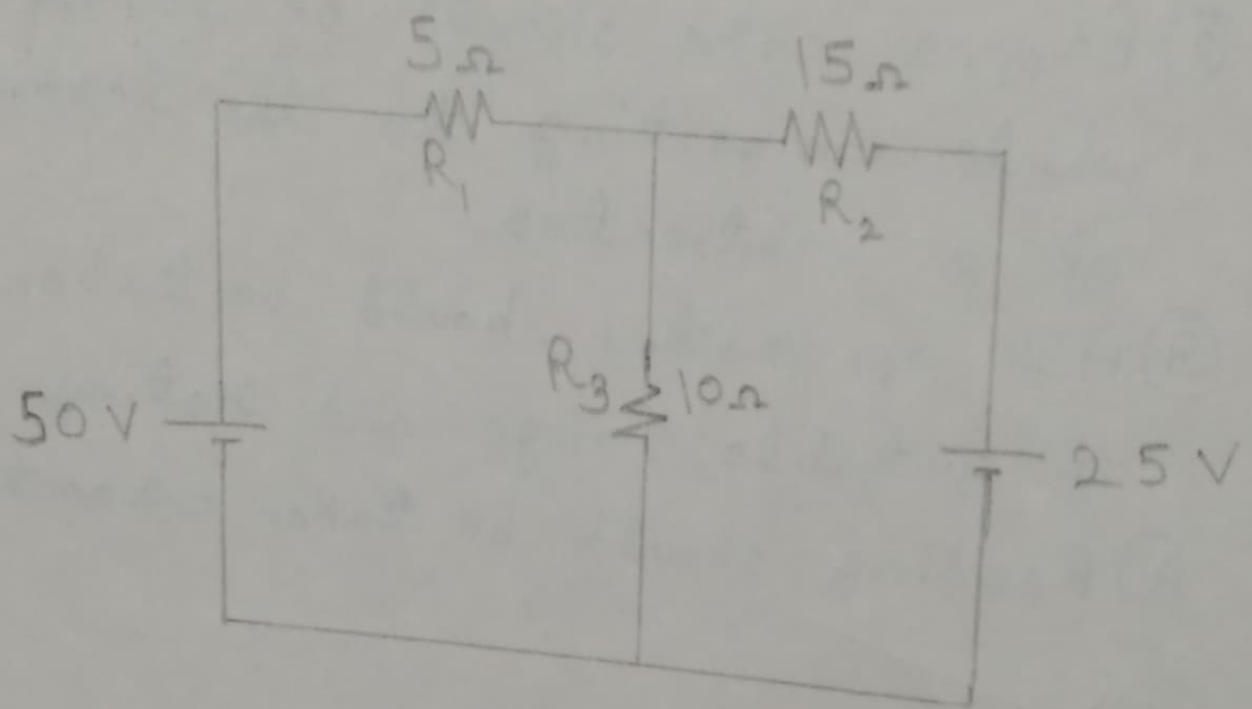


Circuit Diagram:-



TUTORIAL / PRACTICAL NO.

Experiment No.-3

Object :- Verification of Kirchhoff's Law.

Apparatus :-

• A.C. Supply	0-30 V	1
• Ammeters	0-2 A	3
• Voltmeters	0-150 V	1
• Rheostat	20 Ω	3

Theory :-

Kirchhoff's Voltage Law (KVL) :- In a closed circuit the algebraic sum of voltage is zero. If V is the supply voltage, I is the current flowing through elements of resistance R_1, R_2, R_3 .

$$V - I(R_1 + R_2 + R_3) = 0$$

Kirchhoff's Current Law (KCL) :- At any

junction the current entering the junction is equal to current going out to the junction.

$$I = I_1 + I_2$$

Observation Table :-
KVL :-

S.No.	Supply Voltage (V)	V_1 (V)	V_2 (V)	V_3 (V)	Result
1	50 V	18.18 V	0 V	31.82 V	50 V
2	25 V	0 V	-6.82 V	31.82 V	25 V

KCL :-

S.No.	V_{source} (V)	I_1	I_2	I_3
1	50	-4.54	2.72	1.82
2	75	-6.82	4.09	2.73
3	100	-9.09	5.45	3.64

KVL Reading :-

S.No.	V_{source1} (V)	V_{source2} (V)	V_1 (V)	V_2 (V)	V_3 (V)
1	15 V	25 V	2.27	12.27	12.73
2	15 V	0 V	6.82	8.18	8.18

TUTORIAL / PRACTICAL NO.

Formula used:-

$$\Delta V_{\text{Loop}} = 0$$

$$\sum I = 0$$

Calculation:-

Verification of KVL:-

In loop 1,

$$-15 + V_1 + V_3 = 0$$

$$-15 + 2.27 + 12.73 = 0$$

$$\therefore \text{L.H.S} = \text{R.H.S.}$$

In loop 2,

$$25 - V_3 - V_2 = 0$$

$$25 - 12.73 - 12.27 = 0$$

$$\therefore \text{L.H.S} = \text{R.H.S}$$

$$\therefore \Delta V_{\text{Loop}} = 0$$

Verification of KCL:-

$$\sum I = 0$$

$$I_1 + I_2 + I_3 = 0$$

$$-4.54 + 2.72 + 1.82 = 0$$

$$\therefore \text{L.H.S.} = \text{R.H.S.}$$

$$\therefore \sum I = 0$$


Hence Verified.

TORIAL / PRACTICAL NO.

Result:- By observing the calculation it is verified that sum of potential in a closed loop is equal to 0 and sum of current entering and going out from the junction is equal to 0.

Precautions:-

- ① All the connections should be tight.
- ② All devices should be checked they are working properly or not before connecting to the circuit.
- ③ Voltmeter is always connected in parallel with the resistor.
- ④ Ammeter is always connected in series with the resistor.

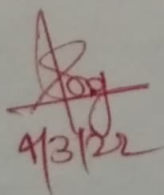
4/3/22