
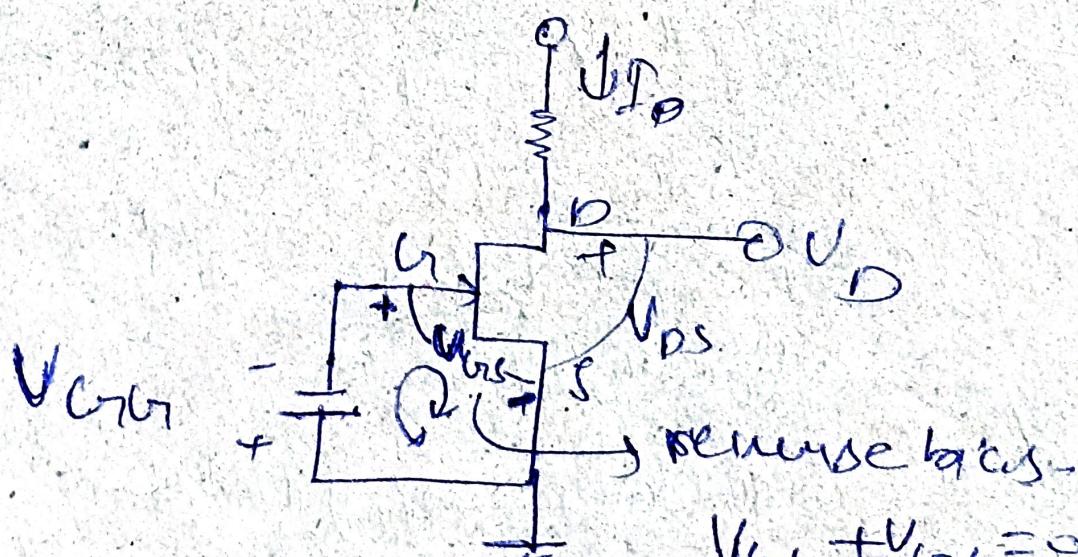


#

## Biasing Offset

- 1) fixed bias circuit
- 2) Voltage divider circuit { oscillates
- 3) Self bias circuit  $\rightarrow$  off

- 1) fixed bias circuit

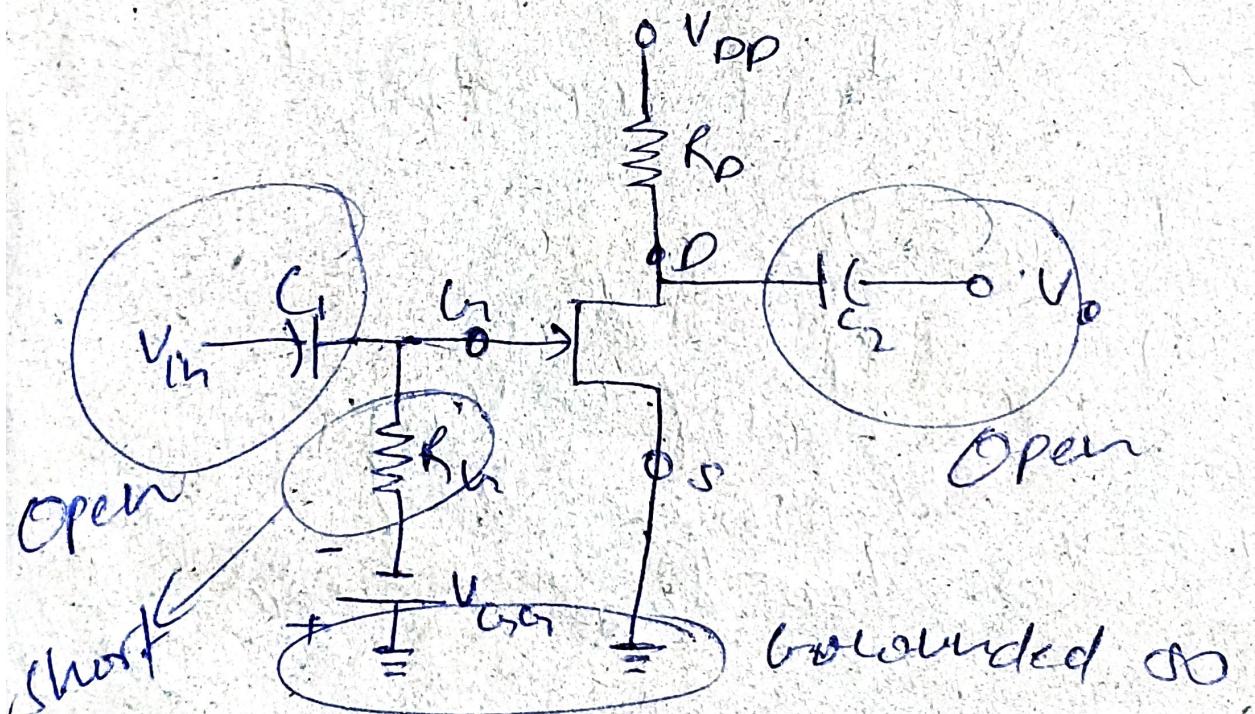

$$V_{BSR} + V_{inS} = 0$$

$$V_{BSR} = -V_{inS} \quad \text{①}$$

$$V_{GDS} = -V_{GSQ} \quad (1)$$

$$\textcircled{#} \quad I_D = I_{DSS} \left( 1 - \frac{V_{GDS}}{V_P} \right)^2 \quad (1)$$

\# KVL at o/p

$$\begin{aligned} V_{DD} - I_D R_D - V_o &= 0 \\ \boxed{V_o = V_{DD} - I_D R_D} \end{aligned}$$

$$V_o = V_{DS} = V_{DD} - I_D R_D$$

\#\#\# i)  $V_{GDS} = -V_{GSQ}$

ii)  $I_{DQ} = I_{DSS} \left( 1 - \frac{V_{GSQ}}{V_P} \right)^2$   
any quiescent point

iii)  $V_{DSQ} = V_{DD} - I_D R_D \quad \text{Question Point}$

Given  $V_{DD} = 16V$ ,  $R_D = 2k\Omega$

$$\begin{aligned} V_{GDS} &\approx 4V & V_{GSQ} &= -V_{GSQ} \\ I_{DSS} &= 20 \text{ mA} & &= -4V \\ V_P &\approx 8V & \end{aligned}$$

Find  $V_{GSQ}$ ,  $I_DQ$ ,  $V_{DSQ}$

iv)  $V_D$

$$\text{Q2} \quad i) V_{GDSQ} = -V_{GSQ} = \boxed{-9 \text{ Volt} \Rightarrow V_{GSQ}}$$

$$I_{DQ} = 20 \times 10^3 \times \left(1 - \frac{(-9)}{6}\right)^2$$

$$20 \times 10^3 \left(1 - \frac{1}{2}\right)^2$$

$$\frac{20 \times 10^3}{\frac{1}{4}} = 5 \text{ mA}$$

$$iii) V_{DSQ} = 16 - 5 \text{ mA} \times 2 \times 10^3 = 10 \rightarrow 5 \times 10^3 \times 2 \times 10^3$$

$$16 - 10 = 6 \text{ Volt}$$


$$\boxed{V_{DSQ} = 6 \text{ Volt}}$$

$$iv) V_D = V_D - V_S \rightarrow 0 \quad \text{source grounded}$$

$$V_D = V_{DS} + V_S \rightarrow 0$$

$$\boxed{V_D = .6 \text{ V}}$$



Concept

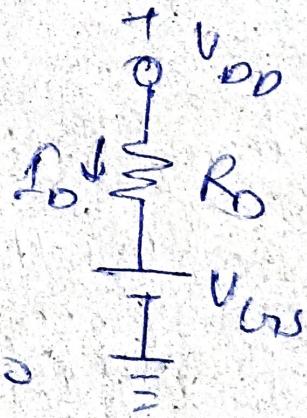

$$V_{DD} - I_D R_D \neq V_{DS} = 0$$

i) Fixed Bias Current

ii) Voltage divider circuit:

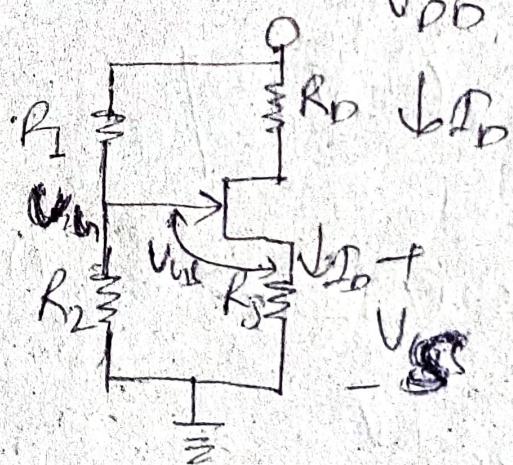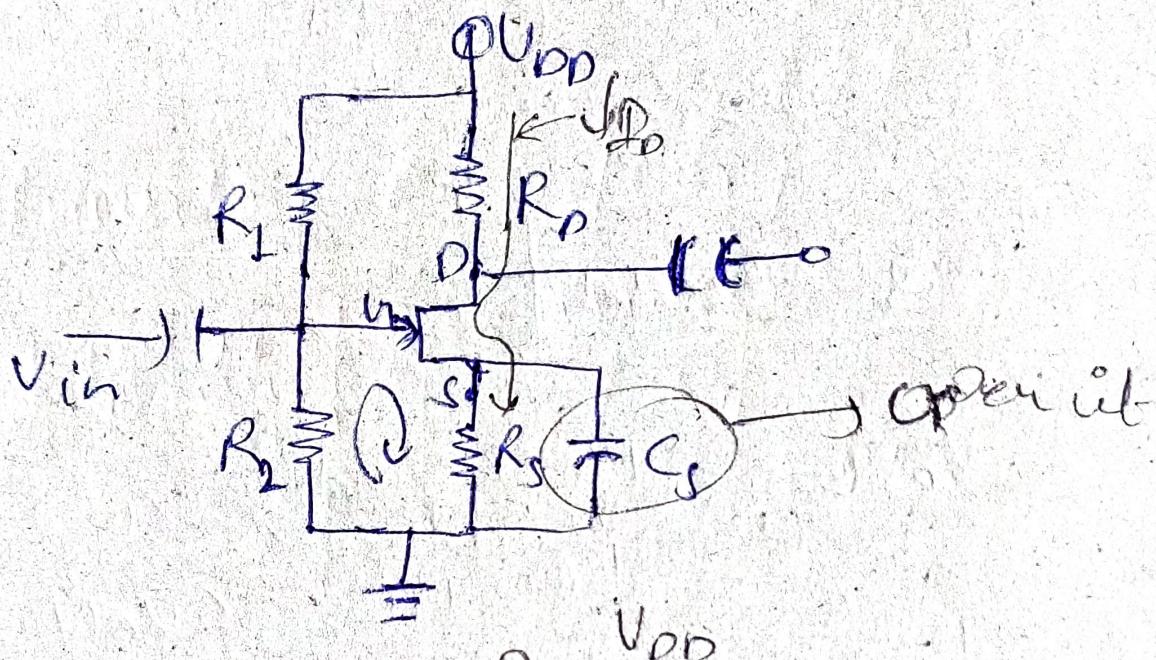

$$V_S = I_D R_S$$

i)  $V_S = I_D R_S \quad (1)$



ii)  $V_{out} = \frac{R_2}{R_1 + R_2} \times V_{DD} \quad (2)$

iii)  $V_{out} - V_{CDS} - V_S = 0$

$$V_{CDS} = V_G - V_S \quad (3)$$


# UNIT - 8

## Operational Amplifier

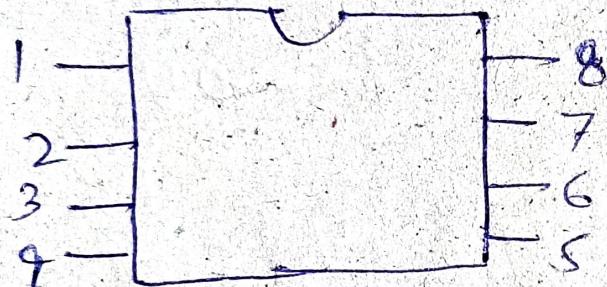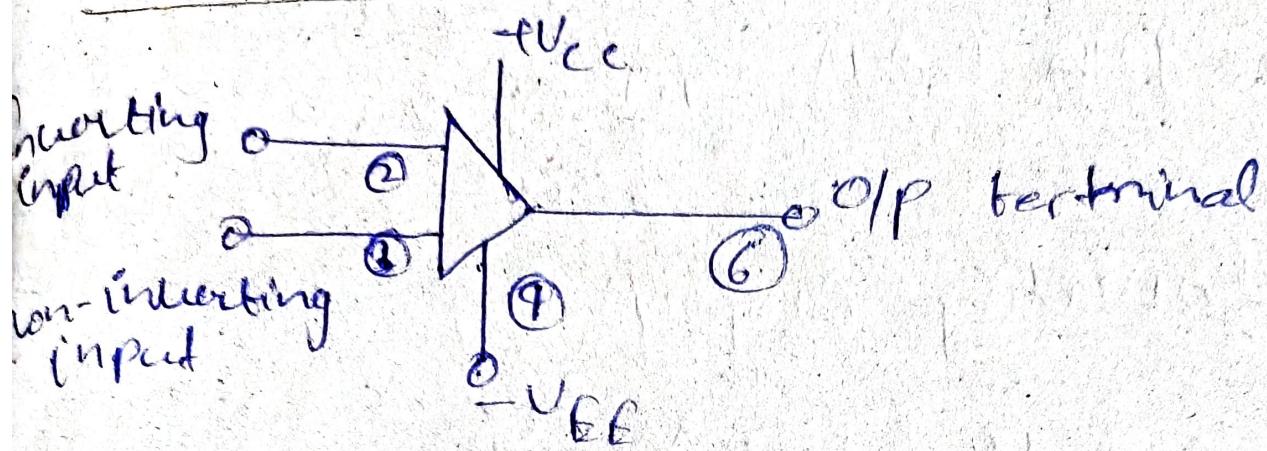


Cases:

i) Inverting

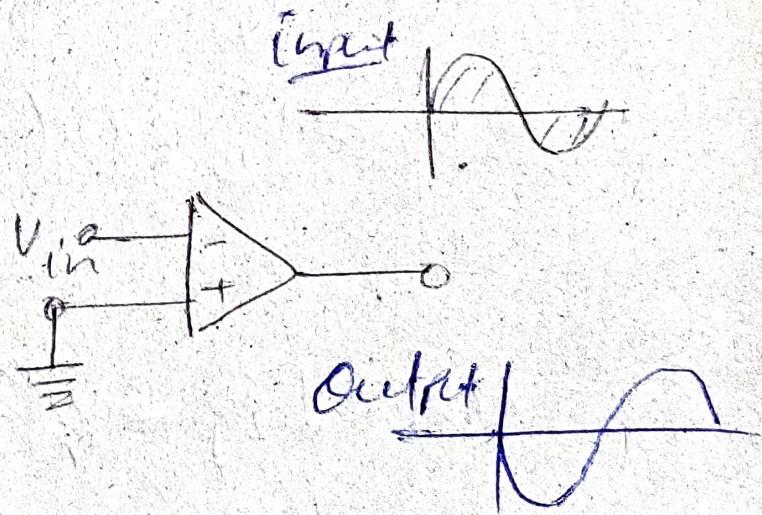


ii) non-inverting

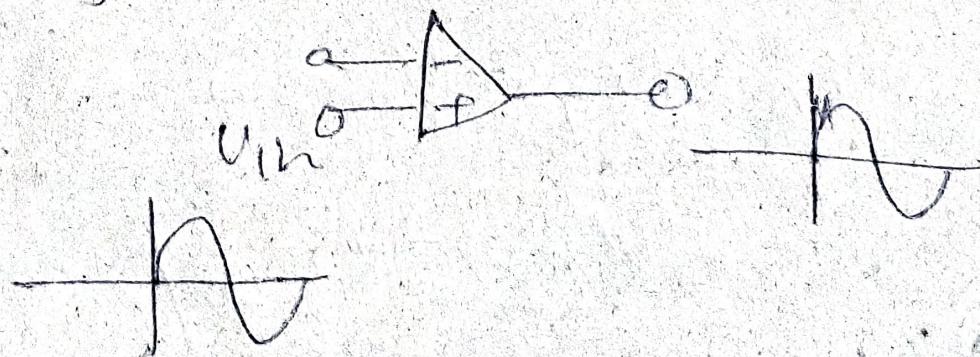

Ques. In Ideal differential amp  
- find i) differential gain ( $A_d$ ) ii) common mode gain ( $A_c$ )

### i) Inverting Amplifier:

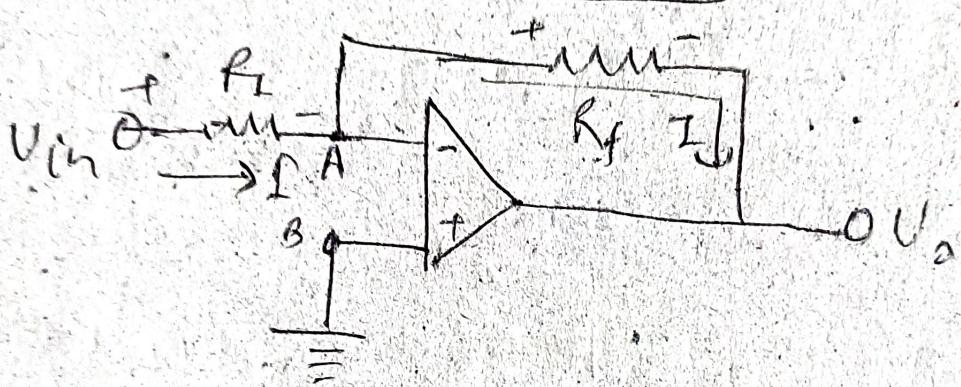

$$V_B = 0$$

$V_A = V_B = 0$  (by virtual ground effect)

$$V_{in} - I R_1 - V_A = 0$$

$$\boxed{V_{in} = I R_1}$$

$$V_A - I R_f - V_o = 0$$


$$\boxed{V_o = -I R_f}$$

$$A_{\text{gain}} = \frac{V_o}{V_{\text{in}}} = -\frac{\text{I}R_f}{\text{I}R}$$

$$A_{\text{gain}} = \frac{V_o}{V_{\text{in}}} = -\frac{R_f}{R_L}$$

$$V_o = \frac{-R_f}{R_L} (V_{\text{in}})$$

(e) Non-Inverting amplifier:

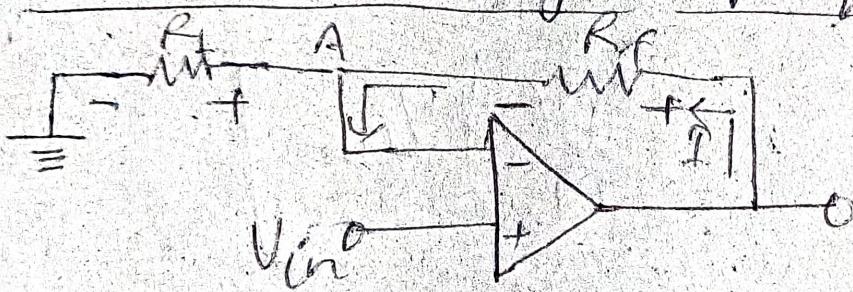

$$V_B = V_{\text{in}}$$

$$V_A = V_B = V_{\text{in}}$$

$$V_A + \text{I}R_f - V_o = 0$$

$$V_o = V_A + \text{I}R_f = V_{\text{in}} + \text{I}R_f \quad (1)$$

$$V_A - \text{I}R_L = 0$$

$$V_A = \text{I}R_L \Rightarrow V_{\text{in}} = \text{I}R_L \quad (2)$$

$$\text{train} = \frac{V_o}{V_{in}} = \frac{V_{in} + DR_f}{DR_f}$$

$$\therefore \frac{DR_1 + DR_f}{DR_f}$$

Train 2:  $L + \frac{R_f}{R_1}$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$