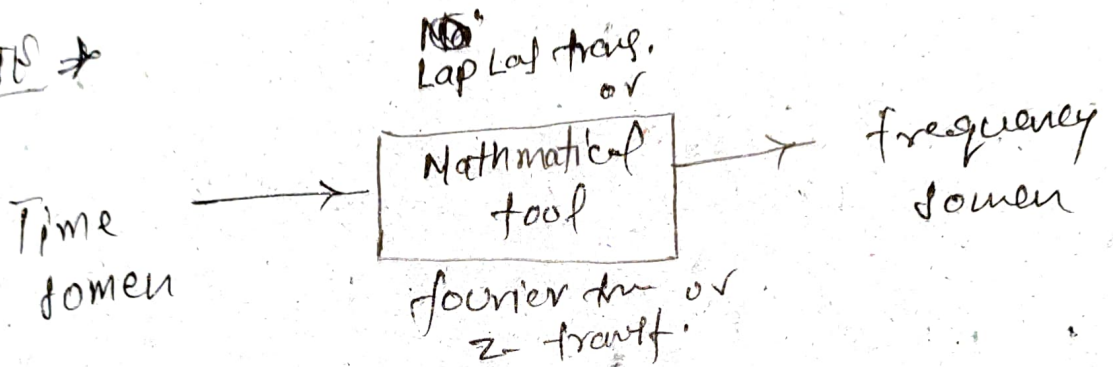


Network Analysis

Signal \rightarrow in EC it represent time varying voltage, current or electromagnetic wave that carries info.

NOTE \rightarrow



Type \downarrow

① Periodic \rightarrow A signal that repeat its value at a regular interval of time.

$$x(t) = x(t + T_0)$$

where $T_0 \rightarrow$ Period

If a signal does not satisfy above eqn called non periodic.

② Continuous and discrete signal \rightarrow Continuous time signal or analog signal are defined for every value of time for a continuous interval.

Ex - sine wave, cosine, triangular.

Discrete time function, are sampled version of continuous time function.

In such function, the independent variable is in discrete form.

$$x(n) = 5^n$$

where $n = 0, 1, 2, \dots$

even function or (symmetrical)

A signal is said to be even function if inversion of time axis does not change its amplitude.

functions are symmetrical about vertical axis.

$$x(-t) = x(t)$$

A signal is said to be odd if it is negative of its reflection

$$x(-t) = -x(t)$$

In such signal inversion of time axis invert amplitude of signal.

Deterministic and random signals -
 Deterministic are those signal which define
 completely a specified function of time.

Whenever a random signal contains uncertain
 information about their values.

Ex - noise.

Complex freq. \rightarrow A freq. which depend on
 "s" which control the magnitude of signal
 and "w" which control rotation of signal.

$$X(t) = X_m e^{st}$$

where $S = \sigma + j\omega$

$\sigma \rightarrow$ real part of s known as neper freq.
 $\omega \rightarrow$ radian freq.

$$X(t) = X_m \cdot e^{\sigma t} \cdot e^{j\omega t}$$


$$= X_m e^{\sigma t} [\cos \omega t + j \sin \omega t]$$

Case - 1 - when $\omega = 0$ & σ has certain value
 then real part

$$X(t) = X_m \cdot e^{\sigma t}$$


$$S = \sigma$$

(i) $\sigma > 0$

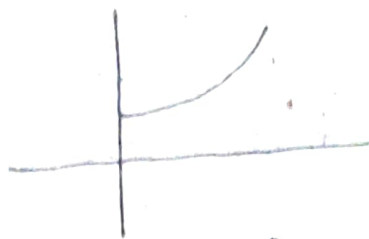


Exponential incr.

(ii) $\sigma < 0$

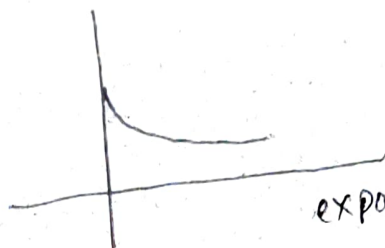

exponential decr.

(iii) $\sigma = 0$

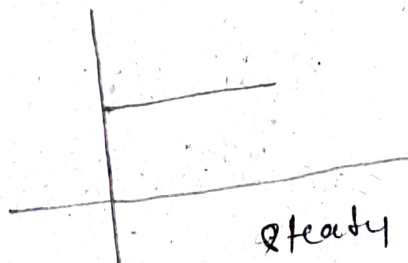

steady state curve

Case 2-

when $\sigma = 0$ & ω has some circular value
then real part

$$X(t) = X_m \cos(\omega t)$$

and imaginary part

$$Y(t) = X_m \sin(\omega t)$$

so sinusoidal steady state curve is obtained.

Case - 3

when both have real value
real part

$$X(t) = X_m e^{\sigma t} \cos(\omega t)$$

Im.

$$Y(t) = X_m e^{\sigma t} \sin(\omega t)$$

(i) when $\sigma > 0$

real part




Imaginary




(ii)

when $\sigma < 0$

Real part

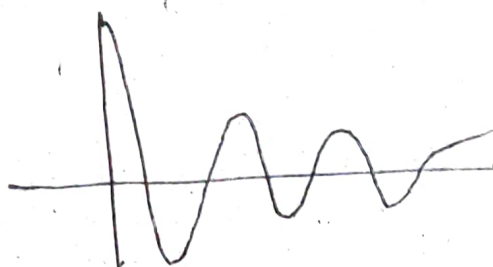


Imaginary part

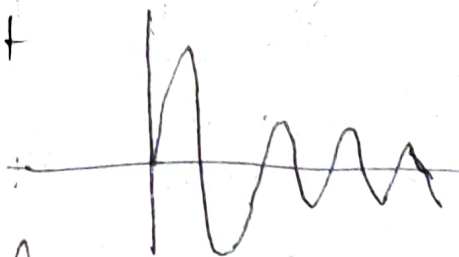

Standard test signal


Unit step signal
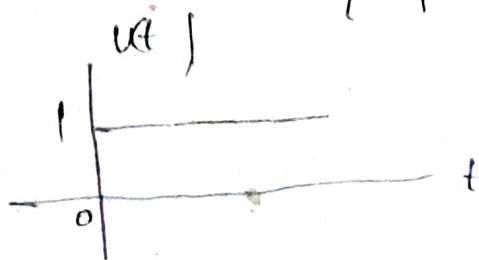
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$



Ramp signal *
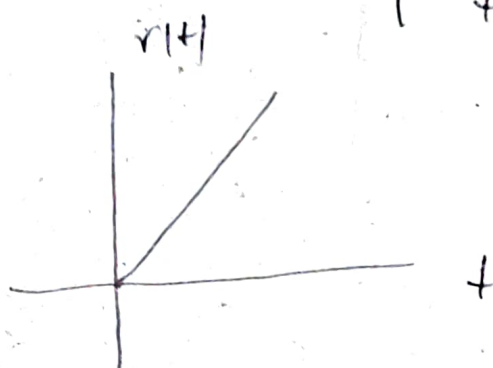
$$r(t) = \begin{cases} 0, & t < 0 \\ t, & t \geq 0 \end{cases}$$



Impulse signal


$$\delta(t) = \begin{cases} 0 & t \neq 0 \\ 1 & t = 0 \end{cases}$$

the ideal impulse is the impulse that is zero every where but at origin it is infinitely high, the area of impulse is finite.

Unit impulse signal is mostly used where the area of unit impulse signal is 1.

~~the area~~
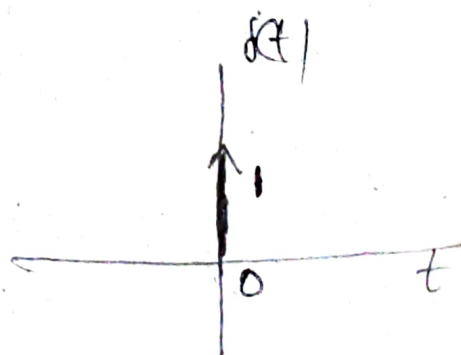
$$\int_{-\infty}^{\infty} \delta(t) \cdot t \, dt = 1$$



Network : Electrical network is an interconnection of electrical element such as resistor, inductor, capacitor

Network element \rightarrow

① Active element : ~~electrical~~ element which are capable of generating electrical energy called Active element.

② Passive element : those element which consume energy and having tendency to change the form of Applied energy into other form of energy.

Ex of ① - voltage and current source, op. amps, transistor.

Ex of ② - resistor, capacitor, inductor.

③ Unilateral : those element in which direction of current passes through them is changed. then properties of circuit also changed.

Ex - diode, transistor.

④ Bilateral : ~~and~~ those element in which direction of current passes do not change the properties of circuit. resistor, conductor, capacitor.

⑤ Lumped \Rightarrow networks in which all the network elements are physically representable & known as lumped network.

Ex - Resistor, inductor, capacitor.

Distributed - networks in which the circuit element can not be physically representable for analysis.

Ex - transmission line.

transient behaviour of a Networks \Rightarrow

transient condition \Rightarrow

① steady state condition \Rightarrow

After transient period, the circuit response reach its stable value and such condition is called steady state condition.

transient period \Rightarrow when change occurs in any networks for a very short duration of time circuit response changes rapidly it may contain peak of very high amplitude, this period of time is known as transient period.

Initial condition of circuit & the behaviour of any electrical circuit can be examined using differential eqⁿ.

these eqⁿ are given value of voltage current or derivative of these quantity w.r.t time

$t(0^-) \Rightarrow$ the time instant at which network is not yet change but about to be changed.

$t(0^+) \Rightarrow$ instant at which the condition of network is just changed.

• Resistor

$$V = IR$$

- Linear time independent eqⁿ.

- Current through resistor changes instantaneously if applied voltage changes.



• Capacitor

$$i = C \frac{dv}{dt}$$

fully charge capacitor behave like open circuit.

Capacitor does not allow sudden change in ~~current~~ voltage.

Inductor *

$$V = L \cdot \frac{di}{dt}$$


Does not allow sudden change in current.
fully charge inductor behave like short circuit
so no effect of sudden change in current
on inductor.

Maximum power transfer theorem *

DC voltage source will deliver max power to
variable load when load resistance is
equal to source resistance.

AC voltage source will deliver max power to
the variable complex load when load
impedance is equal to complex conjugate
of source impedance.

Proof *

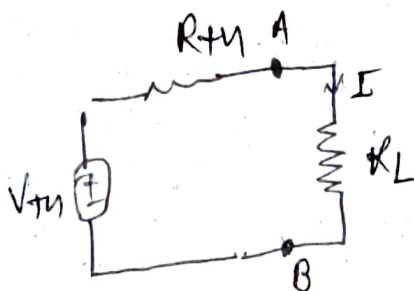

$$P_L = I^2 R_L$$

$$I = \frac{V_{th}}{R_{th} + R_L} \quad (\text{Thevenin theorem})$$

$$P_L = \left(\frac{V+V_1}{R_{th}+R_L} \right)^2 R_L$$

for max or min first ~~derivative~~ derivative will be zero.

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$\boxed{R_L = R_{th}}$$

→ Value of Max power transfer.

Put $R_L = R_{th}$ & $P_L = P_{max}$

$$P_L = \left(\frac{V+V_1}{R_{th}+R_L} \right)^2 R_L$$

⇒

$$\boxed{P_{max} = \frac{V+V_1^2}{4R_L}}$$

* Efficiency of Max power

$$\eta_{max} = \frac{P_{max}}{P_S}$$

$$P_S = I^2 (R_{th} + R_L)$$

$$\therefore R_{th} = R_L$$

$$\Rightarrow P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$$\Rightarrow P_s = \frac{V_{th}^2}{2R_{th}}$$

$$\eta = \frac{1}{2} = 50\% \quad \underline{\text{Ans.}}$$


MILLMAN'S THEOREM \Rightarrow

through the Application of Millman's theorem any parallel voltage sources can be reduced to one.

Step 1 \Rightarrow ①. Convert all voltage sources to current source.

② Combine parallel current source.

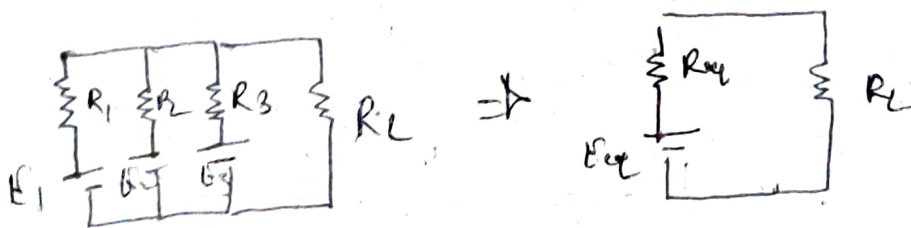③ Convert the resulting current source to a voltage source





$$E_{eq} = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \dots + \frac{E_n}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

for AC Network \Rightarrow

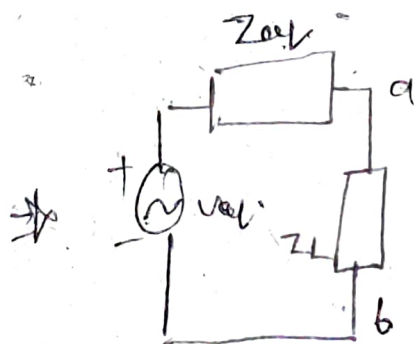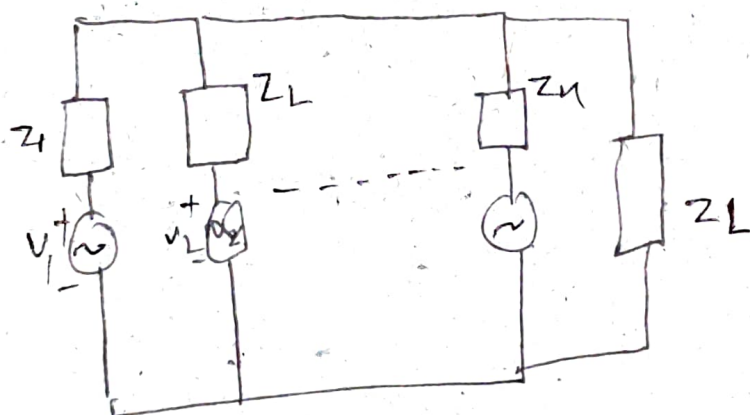if n number of voltage sources $V_1, V_2, V_3, \dots, V_n$ having internal impedances $Z_1, Z_2, Z_3, \dots, Z_n$ are connected in parallel across load Z_L .



$$V_{eq} = \frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \dots + \frac{V_n}{Z_n}$$

$$\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}}$$