

Assignment No.-5

(1) Define the following :

- a) Peak Value or Amplitude
- b) Root Mean Square (RMS) Value
- c) Average Value
- d) Form Factor
- (e) Peak factor
- f) Instantaneous Value
- (g) Phase angle
- h) Time period
- (i) Frequency
- j) Amp Phase difference

(2) What do you understand by 'phase lag' and 'phase lead' ? Explain with the help of an example.

(3) For a sinusoidal voltage wave $v(t) = V_0 \sin \omega t$, derive the expression for the following :

- a) RMS voltage
- (b) Average Voltage
- c) Form Factor
- (d) Peak factor

4) Write short notes on following :

- a) Power factor
- b) Q-factor of a coil
- c) Active Power
- d) Reactive Power
- e) Apparent Power
- f) Power Triangle
- g) Impedance Triangle

5) Explain and derive the expression of current in 1- ϕ AC circuits for the following cases:

- a) Resistive circuit
- b) Purely Inductive circuit
- c) Purely capacitive circuit
- f) R-L circuit
- g) R-C circuit
- h) R-L-C series circuit